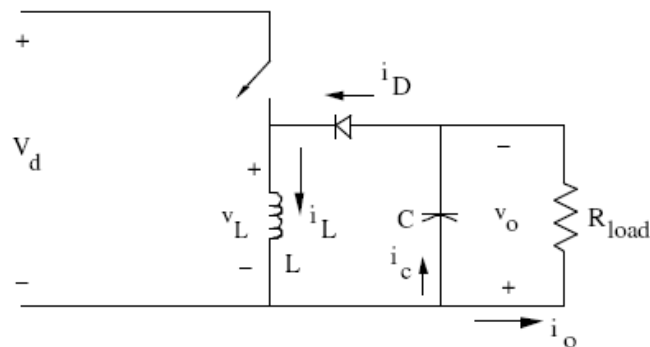


LAB 06

Step-down/Up dc-dc (Buck-Boost) Converter



Nominal Values:

- $V_d = 8.5 \text{ V}$
- $L = 10 \mu\text{H}$
- $rL = 10 \text{ m}\Omega$
- $C = 100 \mu\text{F}$
- $R_{\text{load}} = 8 \Omega$
- $f_s = 100 \text{ kHz}$
- switch duty ratio $D = 0.75$

Problems

1. In steady state, obtain the following waveforms using Buck-Boost:
 - (a) v_L and i_L
 - (b) v_o , i_o and i_c .
- 2.

Increase the load resistance to 80Ω . Obtain v_L and i_L waveforms in the discontinuous conduction mode [Hint: use $V(o) = 28 \text{ V}$ and $I_L(0) = 0$]. Check if the results agree with the analytical calculations.

$$V_o = D V_d \sqrt{\frac{I_{oB,\max}}{I_o}} \qquad I_{oB,\max} = \frac{T_s V_o}{2L}$$

3. Calculate a analytical D

$$D = \frac{V_o}{V_d} \sqrt{\frac{I_o}{I_{oB,\max}}}$$

so that V_o is kept constant to the same value as in continuous mode and check to see if results agree with the analytical calculations.

4. Obtain the peak-to-peak ripple in the output voltage and check to see if results agree with the analytical calculations.

5. Calculate the rms value of the current through the output capacitor as a ratio of the average load current I_o