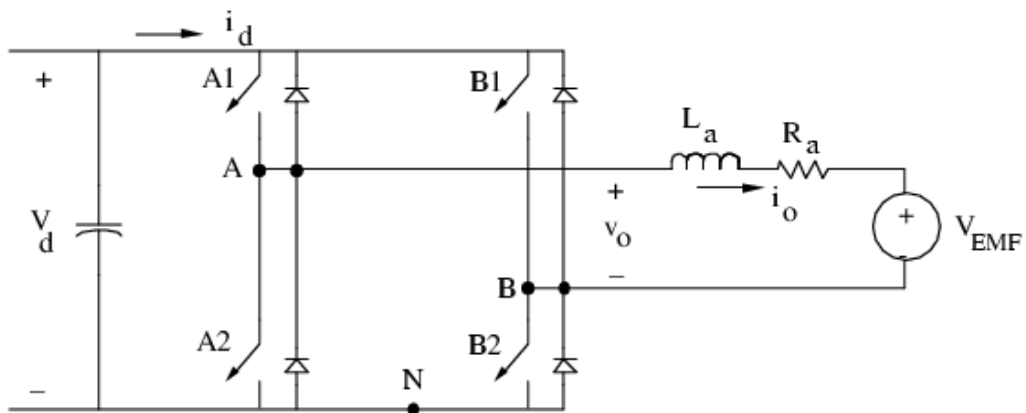


## LAB 07

### Full-Bridge, Bipolar-Switching dc-dc Converter



Nominal Values:  $V_d = 200 \text{ V}$   
 $V_{EMF} = 79.5 \text{ V}$   
 $R_a = 0.37 \Omega$   
 $L_a = 1.5 \text{ mH}$   
 $I_o(\text{avg}) = 10 \text{ A}$   
 $f_s = 20 \text{ kHz}$   
duty-ratio  $D_1$  of  $T_{A1}$  and  $T_{B2} = 0.708$   
( $\therefore v_{\text{control}} = 0.416 \text{ V}$  with  $\hat{V}_{\text{tri}} = 1.0 \text{ V}$ )

1. Obtain the following waveforms
  - (a)  $v_{oA}$ ,  $v_{oB}$
  - (b)  $v_o$ ,  $i_o$
2. Obtain average  $V_o$  and compare with analytical expression
3. Obtain peak-to-peak ripple in  $i_o$  and compare with analytical expression
4. Obtain average value  $I_d$  and compare with analytical expression