

$$i = \frac{(V_i - V_-)}{R_1} = \frac{V_- - V_o}{R_2}$$

$$V_- = -V_o/A$$

$$i = \frac{(V_i + V_o/A)}{R_1} = \frac{(-V_o/A - V_o)}{R_2}$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{R_2}{R_1} \frac{1}{1 + (1 + R_2/R_1)/A} \approx -\frac{R_2}{R_1} \quad (A \gg 1)$$

R_1	R_2	A	V_o/V_i
10 k Ω	100 k Ω	100	-9.009
10 k Ω	100 k Ω	10 ⁴	-9.989
10 k Ω	100 k Ω	10 ⁶	-9.9999
10 k Ω	100 k Ω	∞	-10


$V_o/V_i = -\frac{10A}{A+11}$



2) $A \rightarrow \infty$, $\frac{V_o}{V_i} = 1 + \frac{R_2}{R_1} = 1 + \frac{10^4}{10^4} = 2$

(a)

$$\left. \begin{array}{l} \text{mínimo: } 1 + \frac{0.95 \cdot 10^4}{1.05 \cdot 10^4} = 1.905 \\ \text{máximo: } 1 + \frac{1.05 \cdot 10^4}{0.95 \cdot 10^4} = 2.105 \end{array} \right\} 2 \pm 5\%$$

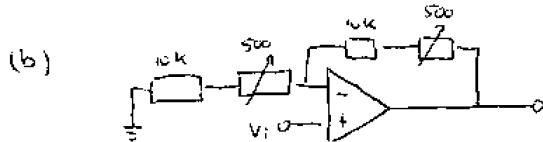Stat.: $R_2 (\pm 5\%), R_1 (\pm 5\%) \cdot \frac{R_2/R_1 (\pm \sqrt{2} 5\%) }{1 + R_2/R_1} (\pm \frac{1}{\sqrt{2}} 5\% = 3.5\%)$



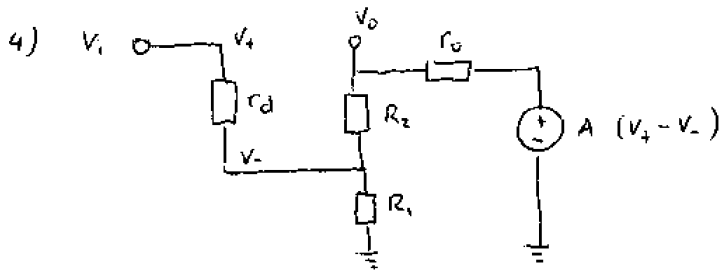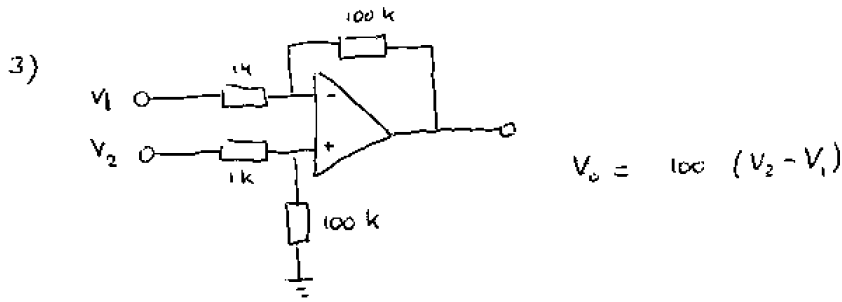

(*) $r_o \ll R_1, R_2$

$$V_o = A (V_+ - V_-) = A (V_i - V_-)$$

(*) $r_d \gg R_1$


$$V_- = \frac{R_1}{R_1 + R_2} V_o = \beta V_o \quad (\beta = \frac{R_1}{R_1 + R_2})$$

(a) $V_o = A (V_i - \beta V_o) \Rightarrow \frac{V_o}{V_i} = \frac{A}{1 + A\beta}$

$$V_- = \beta V_o = \frac{A\beta}{1 + A\beta} V_i$$

$$I_i = (V_+ - V_-) / r_d = (V_i - \frac{A\beta}{1 + A\beta} V_i) / r_d = \frac{1}{r_d} \cdot \frac{1}{1 + A\beta} V_i$$

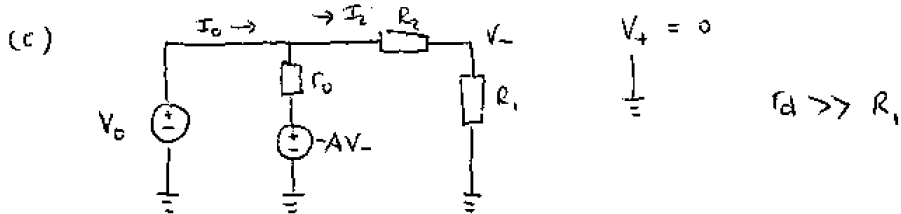(b) $R_i = \frac{V_i}{I_i} = r_d (1 + A\beta)$



$$V_o = I_2 (R_1 + R_2) \quad \textcircled{I} \quad I_2 = V_o / (R_1 + R_2)$$

$$e \quad V_o = -A V_- + (I_o - I_2) r_o \quad \textcircled{II}$$

$$V_- = R_1 I_2 \quad \textcircled{III}$$

③ em ② :

$$V_o = -A R_1 I_2 + (I_o - I_2) r_o$$

$$= I_o r_o - I_2 (r_o + A R_1) \quad \textcircled{IV}$$


① em ④

$$V_o = I_o r_o - V_o \frac{(r_o + A R_1)}{R_1 + R_2}$$

$$V_o \left(1 + \frac{r_o + A R_1}{R_1 + R_2} \right) = I_o r_o$$

$$\beta = R_1 / (R_1 + R_2)$$
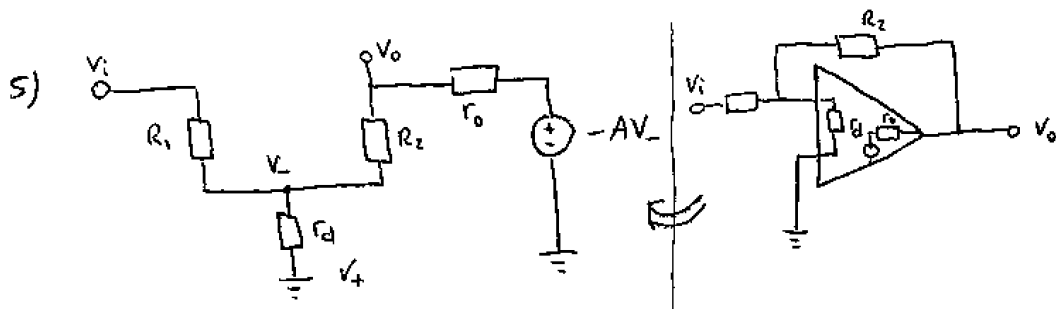
$$R_{out} = \frac{V_o}{I_o} = \frac{r_o}{1 + \frac{r_o + A R_1}{R_1 + R_2}} \approx r_o \frac{1}{1 + A \beta}$$



(a) $r_d \gg R_1, R_2$

$$V_- = V_o \frac{R_1}{R_1 + R_2} + V_i \frac{R_2}{R_1 + R_2} \quad \left(\beta = \frac{R_1}{R_1 + R_2} \right)$$

$$= V_o \beta + V_i (1 - \beta)$$

$$V_o = -A V_- \quad (r_o \ll R_2)$$

$$= -A (V_o \beta + V_i (1 - \beta))$$

$$V_o + A \beta V_o \approx A (\beta - 1) V_i$$

$$(1 + AB)V_o = A(\beta - 1)V_i$$

$$\text{ganho: } \frac{V_o}{V_i} = \frac{(\beta - 1)A}{1 + AB} \quad \left(A \rightarrow \infty, \frac{V_o}{V_i} \rightarrow -\frac{R_2}{R_1} \right)$$

$$(b) \quad I_i = (V_i - V_-) / R_1 \quad \left(\begin{array}{l} V_- = -V_o / A \\ = -\frac{(\beta - 1)}{1 + AB} V_i \end{array} \right)$$

$$I_i = \frac{1}{R_1} \left(V_i + \frac{\beta - 1}{1 + AB} V_i \right)$$

$$= \frac{V_i}{R_1} \left(1 + \frac{\beta - 1}{1 + AB} \right)$$

$$\frac{V_i}{I_i} = \frac{1 + AB}{AB + \beta} R_1 \approx R_1$$

(c) igual a 4c