
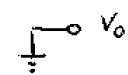



1) Solução 1 : 


Solução 2 : $A \frac{d^2 V(t)}{dt^2} = -B V(t)$

$$V = -\frac{B}{A} \iint V(t) dt^2$$

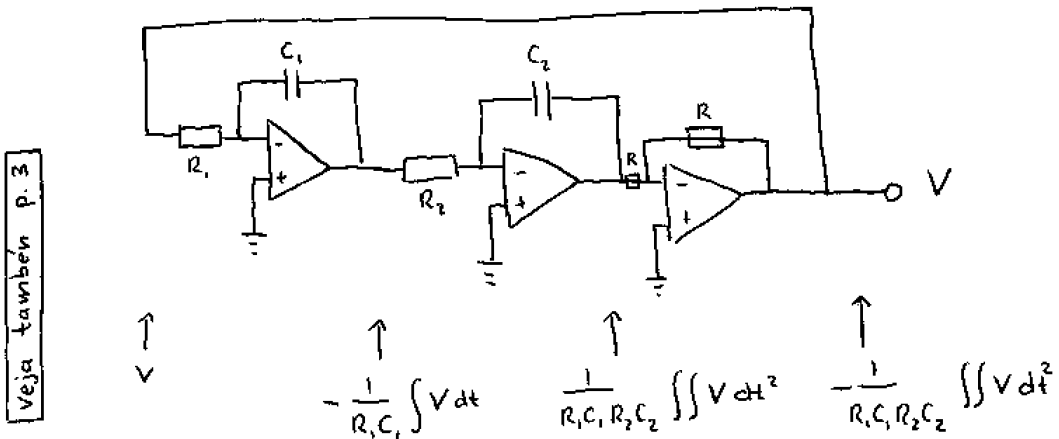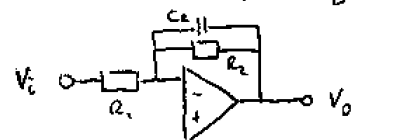

$$R_1 C_1 R_2 C_2 = \frac{A}{B} = 3.6 \cdot 10^7 \text{ s}^2$$

2)  $\left| \frac{V_o}{V_i} \right| = \frac{R_2}{R_1} \frac{1}{\sqrt{1 + \omega^2 (R_2 C_2)^2}} = 100 \text{ (DC)}$ $\omega=0$

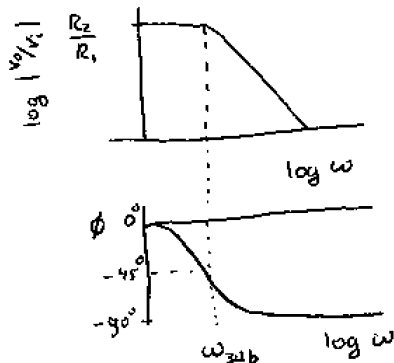

$$\omega_{3db} : \omega^2 (R_2 C_2)^2 = 1$$

$$f_{3db} : f = \frac{1}{2\pi R_2 C_2} = \frac{1}{2\pi \cdot 10^5 \cdot 10^{-10}}$$



$$= 15.9 \text{ kHz}$$

$$(= 10^5 \text{ rad/s})$$

| V_i | ω | $\left \frac{V_o}{V_i} \right $ | ϕ |
|-----------------|----------|----------------------------------|---------------|
| $\sin \omega t$ | 10^4 | 99.50 | -5.7° |
| | 10^5 | 70.71 | -45° |
| | 10^6 | 9.95 | -84.3° |

$$\phi = \arctg(-\omega R_2 C_2)$$

3)

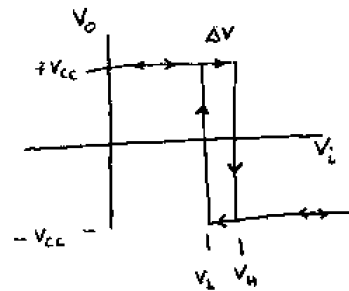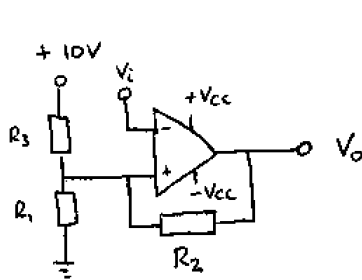

$$+V_{cc} = +10V$$

$$-V_{cc} = -10V$$

$$V_H = \frac{R_1}{R_1 + R_3} (+10V) = +5V \Rightarrow R_1 = R_3 = 1k\Omega$$

$$\Delta V = 2V_{cc} \cdot \frac{R_1 // R_3}{R_2 + R_1 // R_3} = 2V$$


Veja também p. 3

$$\frac{R_1 // R_3}{R_2 + R_1 // R_3} = 0.1 \Rightarrow \frac{0.5k}{R_2 + 0.5k} = 0.1$$

$$\Rightarrow R_2 = 4.5k\Omega$$

(p. 231 of Horowitz & Hill)

4)

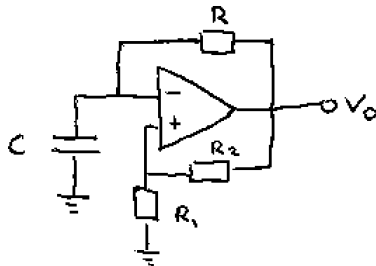

(p. 695 of Bogart)

$$\beta = \frac{R_1}{R_1 + R_2}$$

$$T = 2RC \ln\left(\frac{1+\beta}{1-\beta}\right) \text{ s.}$$

$$f = 1 \text{ kHz} \Rightarrow T = 1 \text{ ms}$$


$$\text{exemplo: } R_1 = R_2 = 1k\Omega, \beta = 0.5$$

$$2RC \ln(3) = 10^{-3}$$

$$RC = \frac{1}{2 \ln 3} 10^{-3}$$

$$R = 1k\Omega \Rightarrow C = 0.46 \mu\text{F}$$

1) Solução 3


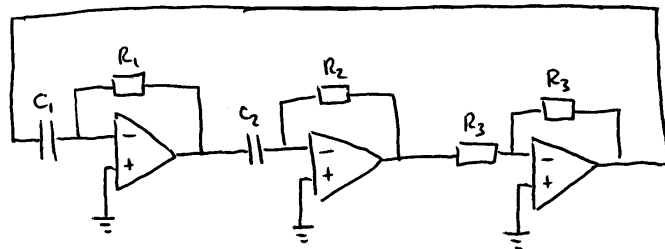


$$\begin{array}{cccc} \uparrow & \uparrow & \uparrow & \uparrow \\ V(t) & -R_1 C_1 \frac{dV(t)}{dt} & R_1 C_1 R_2 C_2 \frac{d^2 V(t)}{dt^2} & -R_1 C_1 R_2 C_2 \frac{d^3 V(t)}{dt^3} \end{array}$$

$$A \frac{d^2 V(t)}{dt^2} + B V(t) = 0 \Rightarrow V(t) = -\frac{A}{B} \frac{d^2 V(t)}{dt^2}$$


$$\frac{A}{B} = R_1 C_1 R_2 C_2 = 3.6 \cdot 10^7 \text{ s}^2$$

3)

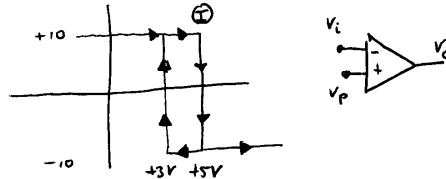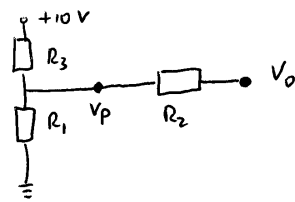

$$\textcircled{I} \quad V_0 = +10 \text{ V}, \quad V_p = +5 \text{ V} \Rightarrow R_1 = R_2 \parallel R_3 \Rightarrow \frac{1}{R_1} = \frac{1}{R_2} + \frac{1}{R_3}$$
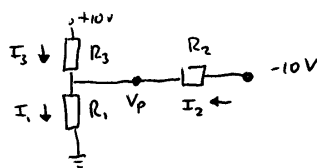
$$\textcircled{II} \quad V_0 = -10 \text{ V}, \quad V_p = +3 \text{ V} \Rightarrow$$



$$I_1 = I_2 + I_3$$

$$\frac{V_p}{R_1} = \frac{-10 - V_p}{R_2} + \frac{10 - V_p}{R_3} \Rightarrow \text{com } (V_p = 3)$$

$$\Rightarrow 3 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = 10 \left(\frac{1}{R_3} - \frac{1}{R_2} \right)$$

Solução: $R_2 = 1 \text{ k}\Omega \Rightarrow R_3 = 250 \Omega, R_1 = 200 \Omega$
↑ escolha