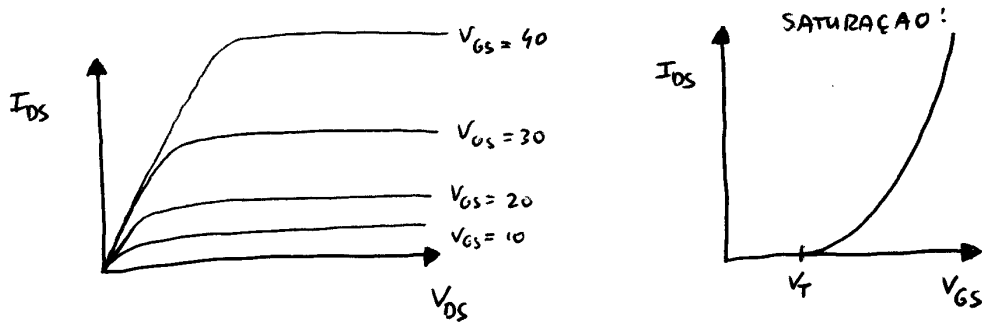


① saturação : $V_{DS} \geq V_{GS} - V_T$

② satur. : $I_{DS} = \frac{1}{2} \mu_N C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$

③ linear : $I_{DS} = \mu_N C_{ox} \frac{W}{L} (V_{GS} - V_T) V_{DS}$



1a : $R_D = ?$ $V_D = \pm 1V \Rightarrow$ polarização $V_D = 0V$

$I_D = 0.1mA \Rightarrow R_D = \frac{V_{DD} - V_D}{I_D} = 50 k\Omega$

$R_S = ?$: $V_S = ?$: saturação : $I_{DS} = \frac{1}{2} \mu_N C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$

$0.1 mA = \frac{1}{2} 0.4 mA (V_G - V_S - V_T)^2$

$0.5 = (V_S + V_T)^2$

$V_S = -1 - \sqrt{0.5} = -1.7V$

$R_S = \frac{V_S - V_{SS}}{0.1 mA} = 33 k\Omega$

$R_G = 10 M\Omega$ (escolha)

verifique se temos saturação : $V_{DS} \geq V_{GS} - V_T ?$

$V_D = 0V$ $0 - (-1.7) \geq 0 - (-1.7) - 1$?


minimo $V_D = -1V$ $-1 - (-1.7) \geq 0 - (-1.7) - 1$?

1b : ① $g_m \equiv \frac{\partial I_{DS}}{\partial V_{GS}}$ em saturação (veja eq. ②) :

$g_m = \frac{1}{2} \mu_N C_{ox} \frac{W}{L} 2 (V_{GS} - V_T) = \frac{2 I_{DS}}{(V_{GS} - V_T)}$


$$g_m = \frac{2I_{D_S}}{(V_{GS} - V_T)} = \frac{2 \cdot 0.1 \text{ mA}}{1.7 \text{ V} - 1 \text{ V}} = 2.85 \cdot 10^{-3} \text{ A/V}$$
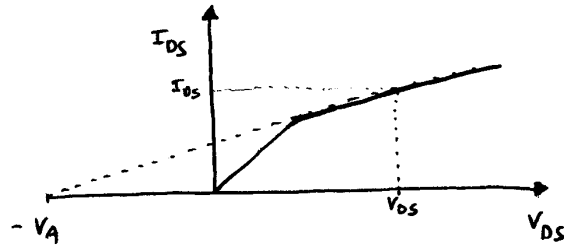
$$\textcircled{c} \quad \frac{1}{r_o} \equiv \frac{\partial I_{D_S}}{\partial V_{D_S}}$$



$$\frac{1}{r_o} = \frac{I_{D_S}}{V_{D_S} + V_A} = \frac{0.1 \text{ mA}}{1.7 \text{ V} + 40 \text{ V}} \Rightarrow r_o = 417 \text{ k}\Omega$$

1c: modelo pequenos sinais

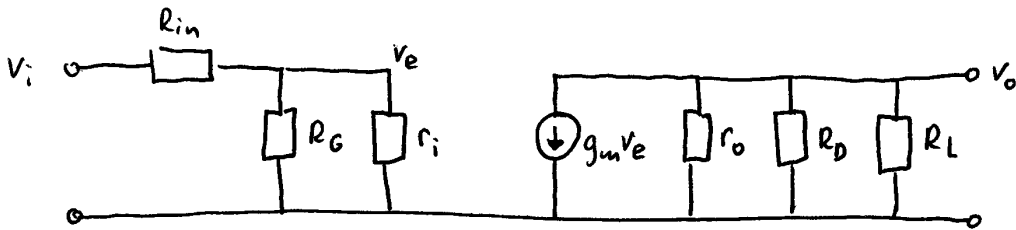


$$v_e = \frac{R_G \parallel r_i}{R_G \parallel r_i + R_{in}} \cdot v_i$$


$$V_o = g_m v_e (r_o \parallel R_D \parallel R_L) v_i = g_m \frac{R_G \parallel r_i}{R_G \parallel r_i + R_{in}} (r_o \parallel R_D \parallel R_L) v_i$$

$$\Rightarrow \frac{V_o}{V_i} = 2.85 \cdot 10^{-3} \cdot \frac{5 \text{ M}}{5 \text{ M} + 1 \text{ M}} (417 \text{ k} \parallel 50 \text{ k} \parallel 40 \text{ k}) = 50 \text{ V/V}$$

2:

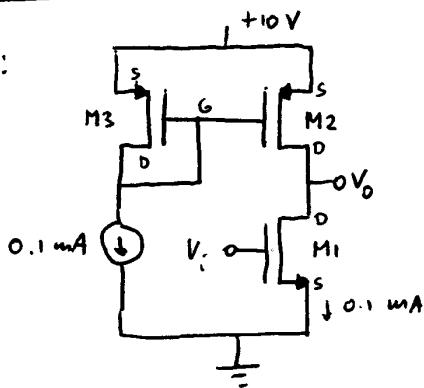

modelo pequenos sinais:

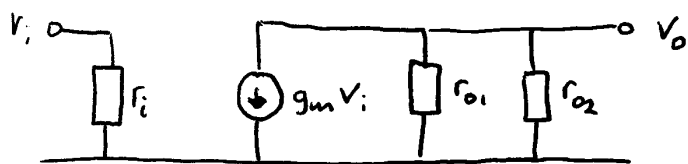

$$\text{M3: } V_{SG} = V_{SD} \Rightarrow$$

$$V_{SD} > V_{SG} - |V_T| \text{ sempre} \Rightarrow \text{saturação}$$

$$g_m = \frac{2 I_{DS}}{V_{GS} - V_T} = \frac{2 \cdot 0.1 \text{ mA}}{-1 \text{ V}} = -2 \cdot 10^{-4} \text{ A/V}$$

$$r_{o1} = \frac{V_{DS} + V_A}{0.1 \text{ mA}} \approx \frac{V_A}{0.1 \text{ mA}} = \frac{100 \text{ V}}{0.1 \text{ mA}} = 1 \text{ M}\Omega$$

$$r_{o2} = r_{o1} = 1 \text{ M}\Omega$$

$$\frac{v_o}{v_i} = g_m (r_{o1} \parallel r_{o2}) = (-2 \cdot 10^{-4} \text{ A/V}) \cdot (500 \text{ k}\Omega) = -100 \text{ V/V}$$

2b: M2 : saturação quando $V_{SD2} \geq V_{SG2} - |V_{T2}|$

$$10 - V_{D2} \geq 10 - V_{G2} - |V_{T2}|$$

$$V_{D2} \leq V_{G2} + 1 \text{ V} \quad V_G = 0$$

$$V_{D2} \leq 1 \text{ V}$$


M1 : saturação quando $V_{DS1} \geq V_{GS1} - V_T$

$$V_{D1} \geq V_{G1} - 1 \text{ V}$$

$$V_{D1} \geq -1 \text{ V}$$

$$v_o = V_{D1} = V_{D2} \Rightarrow -1 \text{ V} < v_o < 1 \text{ V}$$

2c :

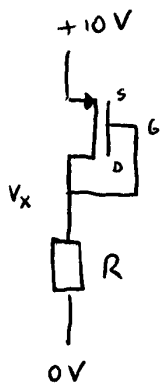

$$\textcircled{I} : I_{SD} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_T|)^2$$

$$I_{SD} = \frac{1}{2} \cdot 10 (\mu\text{A/V}^2) \cdot \frac{100 \mu\text{m}}{10 \mu\text{m}} \cdot (10 - v_x - 1)^2$$

$$= 50 \cdot (9 - v_x)^2 \mu\text{A} = 0.1 \text{ mA}$$

$$\textcircled{II} : I_{SD} = \frac{v_x}{R} \Rightarrow v_x \approx g v$$

$$R = \frac{v_x}{I_{SD}} = \frac{g v}{0.1 \text{ mA}} = 90 \text{ k}\Omega$$