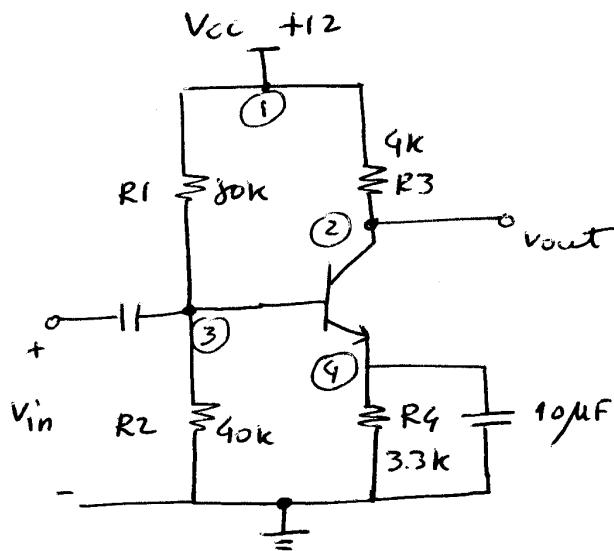



1)



1a) circuito equivalente thevenin

$$V(3) = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{40k}{80k + 40k} \times 12 = 4V$$
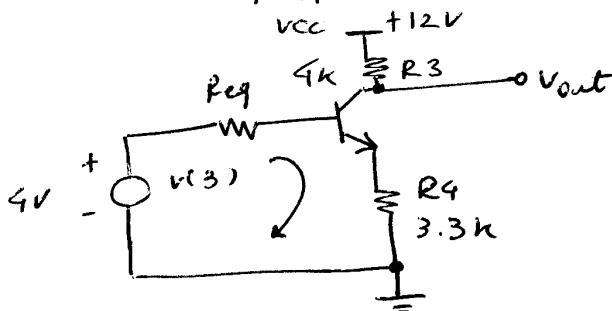
$$R_{eq} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{40k \times 80k}{40k + 80k} = 26.7k \Omega$$



Pela lei das malhas

$$V(3) = R_{eq} I_B + V_{BE} + I_E R_4$$

$$V(3) = R_{eq} I_B + V_{BE} + (\beta + 1) I_B R_4$$

logo

$$I_B = \frac{V(3) - V_{BE}}{R_{eq} + (\beta + 1) R_4} = \frac{4 - 0.7}{26.7 \times 10^3 + 251 \times 3.3 \times 10^3} = 3.86 \mu A$$

$$V(4) = I_E R_4$$

$$= (\beta + 1) I_B \times R_4$$

$$= 251 \times 3.86 \times 10^{-6} \times 3.3 \times 10^3 = 3.2 \text{ V}$$

$$V(2) = V_{CC} - I_C R_3$$

$$= 12 - 250 \times 3.86 \times 10^{-6} \times 4 \times 10^3$$

$$= 8.14 \text{ V}$$

logo

$$V(1) = 12 \text{ V}$$

$$I_B = 3.86 \mu\text{A}$$

$$V(2) = 8.14 \text{ V}$$

$$I_C = 0.965 \text{ mA}$$

$$V(3) = 4 \text{ V}$$

$$I_E = 0.969 \text{ mA}$$

$$V(4) = 3.2 \text{ V}$$

15)


$$\frac{1}{r_\pi} = \frac{\partial I_B}{\partial V_{BE}} = \frac{I_B}{V_T}$$

$$\text{logo } r_\pi = \frac{V_T}{I_B} = \frac{25 \text{ mV}}{3.86 \mu\text{A}} = 6477 \Omega$$

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T} = \beta \frac{I_B}{V_T} = \frac{I_C}{r_\pi} = 0.0386 \text{ A/V}$$

$$\frac{1}{r_o} = \frac{\partial I_C}{\partial V_{CE}} = \frac{I_C}{V_A} \quad \text{logo } r_o = \frac{V_A}{I_C} = \frac{70}{250 \times 3.86 \times 10^{-6}} = 72539 \Omega$$

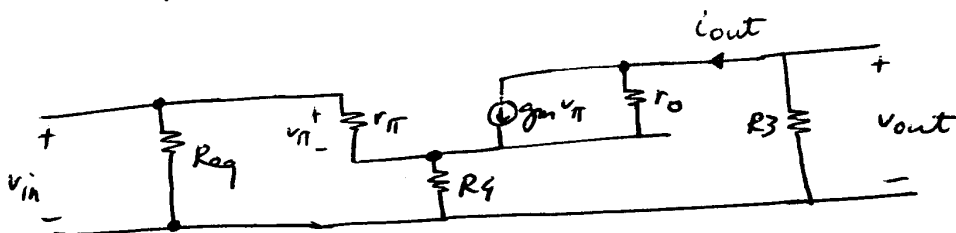16) circuito equivalente para pequenos sinais



$$v_{in} = v_{\pi} + R_4 i_{out}$$

$$v_{out} = -R_3 i_{out} = (i_{out} - g_m v_{\pi}) r_o + R_4 i_{out}$$

$$\text{logo } (-R_3 - R_4 - r_o) i_{out} = -g_m r_o v_{\pi}$$

$$i_{out} = \frac{g_m r_o v_{\pi}}{R_3 + R_4 + r_o}$$

$$v_{in} = \left[1 + \frac{g_m r_o R_4}{R_3 + R_4 + r_o} \right] v_{\pi}$$

$$v_{out} = -\frac{R_3 g_m r_o}{R_3 + R_4 + r_o} v_{\pi}$$

$$\text{logo } A_V = \frac{v_{out}}{v_{in}} = -\frac{\frac{R_3 g_m r_o}{R_3 + R_4 + r_o}}{1 + \frac{g_m r_o R_4}{R_3 + R_4 + r_o}} = -\frac{R_3 g_m r_o}{R_3 + R_4 + r_o + g_m r_o R_4}$$

$$A_V \approx -\frac{R_3}{R_4}$$

1d) Condensador em paralelo com R_4


logo R_4 equivalente = 0

$$\text{logo } A_V = -\frac{R_3 g_m r_o}{R_3 + r_o} = -(R_3 || r_o) g_m \approx -R_3 g_m$$

(como seria de esperar do circuito equivalente!)



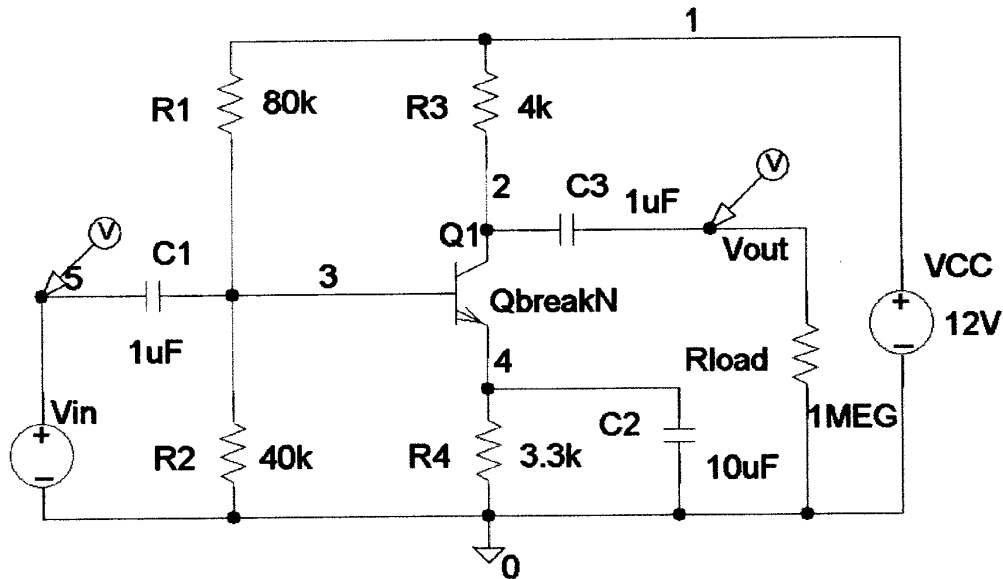1e)
Diagrama esquemático (com condensador)



netlist

* D:\Aulas\electronical\Electrical\fp9\exerc1\Schematic1.sch

* Schematics Netlist *

```
R1      3 1  80k
R2      0 3  40k
R4      0 4  3.3k
C2      0 4  10uF
C1      5 3  1uF
Vin     5 0 DC 0 SIN (0 1MV 1KHZ)
VCC     1 0 DC 12V
Rload   0 Vout 1MEG
R3      2 1  4k
C3      2 Vout 1uF
Q1      2 3 4 QbreakN
```

```
.model QbreakN NPN (BF=250, VAF=70)
```

```
** Analysis setup **
```

```
.tran 0.1ms 3ms
```

```
.OP
```

```
.probe
```

```
.END
```

ponto de polarização


```
****      SMALL SIGNAL BIAS SOLUTION      TEMPERATURE = 27.000 DEG C
```

```
*****
*****
```

ELECTRONICA I FOLHA PROBLEMAS 9

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	12.0000	(2)	8.2158	(3)	3.9049	(4)	
	3.1337						
(5)	0.0000	(Vout)	0.0000				

PROBE (com condensador)

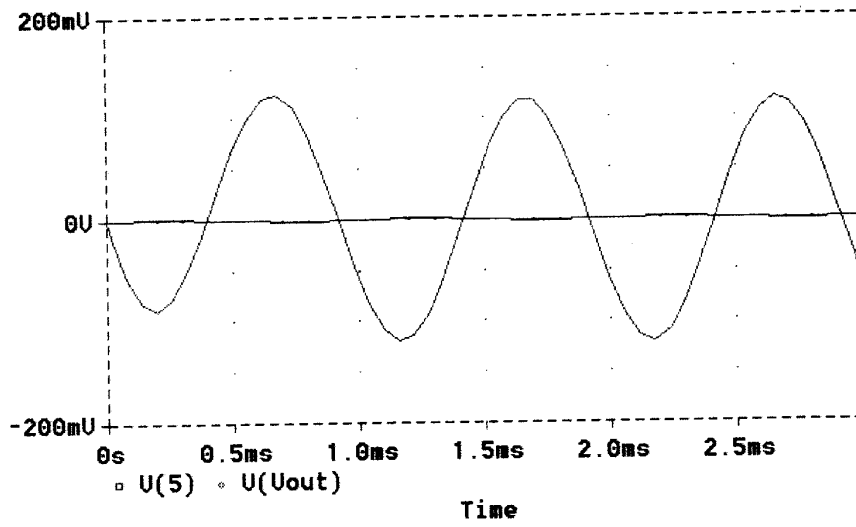

PROBE (sem condensador)

