
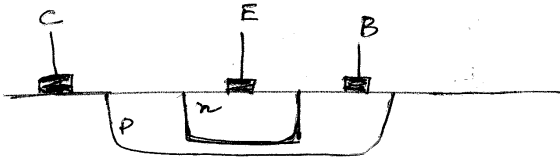


Corte transversal (NPN)

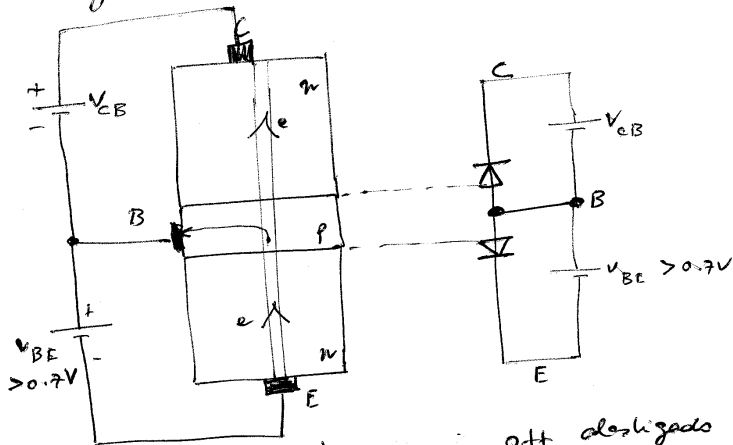

substrato n

diagrama simplificado



- $V_{BE} = 0V$ transistor off desligado
- $V_{BE} > 0.7V$, $V_{CB} > 0$ transistor na zona activa
- $V_{BE} > 0.7V$, $V_{CB} > 0.5V$ transistor saturado

modelo para sinais grandes





$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \quad \text{onde } V_T = \frac{k_B T}{q} \approx 25 \text{ mV para } T = 300 \text{ K}$$

$$I_B = \frac{I_C}{\beta} \quad \text{onde } 50 < \beta < 400$$



$$I_E = I_C + I_B = I_C \left(1 + \frac{1}{\beta}\right) = I_C \left(\frac{\beta + 1}{\beta}\right)$$

ou

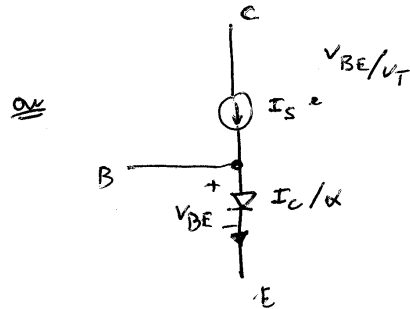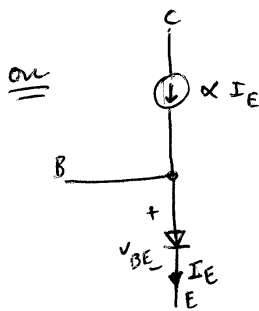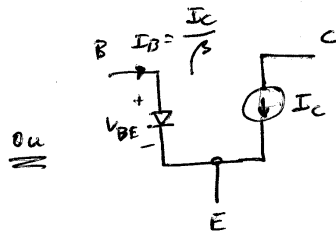
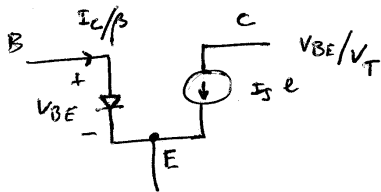
$$I_C = \underbrace{\frac{\beta}{\beta + 1}}_{\alpha} I_E = \alpha I_E \quad \text{com } \alpha \approx 0.99 \text{ se } \beta = 100$$



PNP TRANSISTOR

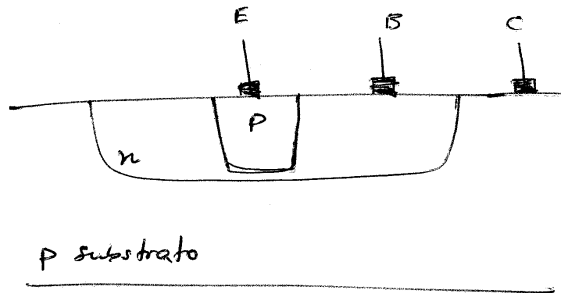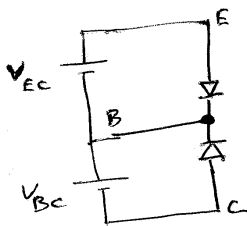


Símbolos para transistores Bipolares

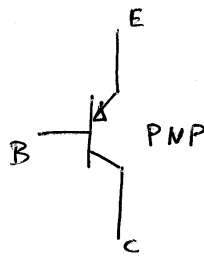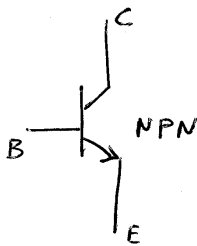

notas

- a "seta" aponta sempre para o material tipo "n"
- a "seta" indica o sentido convencional de corrente

ANÁLISE DC

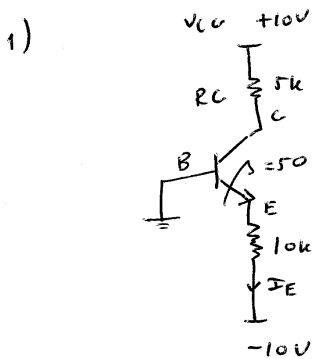

$$I_C = \beta I_B$$

$$I_E = I_C + I_B \\ = (\beta + 1) I_B$$

$$V_E = -0.7 \text{ V}$$

$$I_E = \frac{-0.7 - (-10)}{10 \times 10^3}$$


$$= 0.93 \text{ mA}$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{0.93 \text{ mA}}{51} \approx 18.6 \mu\text{A}$$

$$I_C = \frac{\beta}{\beta + 1} I_E \approx I_E = 0.93 \text{ mA}$$

$$V_C = V_{CC} - R_C \times I_C \\ = 10 - 5 \times 10^3 \times 0.93 \times 10^{-3} \\ = 5.4 \text{ V}$$

2)

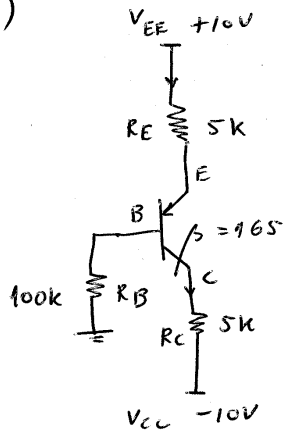

$$V_{EB} = +0.7 \text{ V}$$

$$V_{EE} = R_E \times I_E + V_{EB} + I_B \times R_B$$

$$V_{EE} = (\beta + 1) I_B \times R_E + V_{EB} + I_B R_B$$

$$V_{EE} = [(\beta + 1) R_E + R_B] I_B + V_{EB}$$

$$I_B = \frac{10 - 0.7}{166 \times 5 \times 10^3 + 100 \times 10^3}$$

$$I_B = 1.05 \times 10^{-5} \approx 10 \mu\text{A}$$

$$I_C = \beta I_B = 1.65 \text{ mA}$$

$$V_C = I_C R_C + V_{CC}$$

$$V_C = 1.65 \times 10^{-3} \times 5 \times 10^3 - 10$$


$$= -1.75 \text{ V}$$

$$V_E = V_{EE} - R_E I_E = V_{EE} - R_E \frac{\beta + 1}{\beta} I_C \approx V_{EE} - R_E I_C$$

$$V_E \approx 10 - 5 \times 10^3 \times 1.65 \times 10^{-3} = 1.75 \text{ V}$$

$$V_B = 1.75 - 0.7 = 1.05 \text{ V}$$

3)

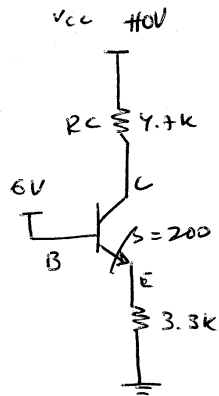

$$V_E = V_B - V_{BE}$$

$$= 6 - 0.7 = 5.3V$$

$$I_E = \frac{5.3}{3.3 \times 10^3} = 1.6 \text{ mA}$$

$$V_C = V_{CC} - R_C I_C$$

$$= 10 - 4.7 \times 10^3 \times 1.6 \times 10^{-3}$$

$$V_C = 2.48V$$

Nota


$$V_{BC} = 6 - 2.48 \approx 3.5V > 0.7V$$

logo a junção V_{BC} está directamente polarizada $V_C = 2.48V$
impossível

$$V_{BC} \approx 0.5V$$

o transistor NÃO está na zona activa mas sim na zona de saturação

4)

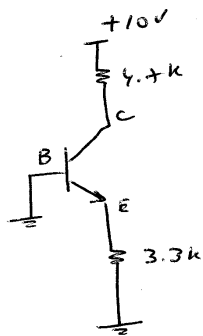


$V_{BE} = 0$ logo o transistor está OFF
desligado


$$I_C = 0, I_E = 0, I_B = 0$$

$$V_C = +10V$$

5)

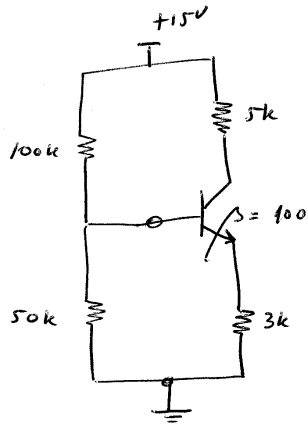

→
teorema de
Thevenin

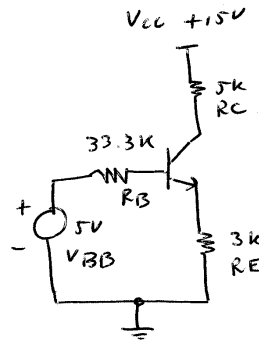

estabilidade da
polarização

$$V_{BB} = R_B I_B + V_{BE} + R_E I_E$$

$$= R_B \frac{I_C}{\beta} + V_{BE} + R_E (\beta + 1) \frac{I_C}{\beta}$$

logo

$$I_C = \frac{(V_{BB} - V_{BE})}{\frac{R_B}{\beta} + R_E} \approx \frac{V_{BB} - V_{BE}}{\frac{R_B}{\beta} + R_E}$$

I_C INSENSÍVEL A V_{BE} , β :

$$V_{BB} \gg V_{BE}$$

$$R_E \gg \frac{R_B}{\beta}$$

$$V_{BD} = R_B I_B + V_{BE} + R_E I_E$$

$$V_{BB} = R_B I_B + V_{BE} + R_E (\beta + 1) I_B$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B + R_E (\beta + 1)}$$

$$I_B = \frac{5 - 0.7}{33.3 \times 10^3 + 3 \times 10^3 \times 101}$$

$$I_B = 12.8 \mu A$$

$$I_C = \beta I_B = 1.28 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 1.29 \text{ mA}$$

$$V_E = R_E I_E = 3 \times 10^3 \times 1.29 \times 10^{-3}$$


$$V_E = 3.87 \text{ V}$$

$$V_C = V_{CC} - R_C I_C$$


$$= 15 - 5 \times 10^3 \times 1.28 \times 10^{-3}$$

$$= 8.6 \text{ V}$$

6)

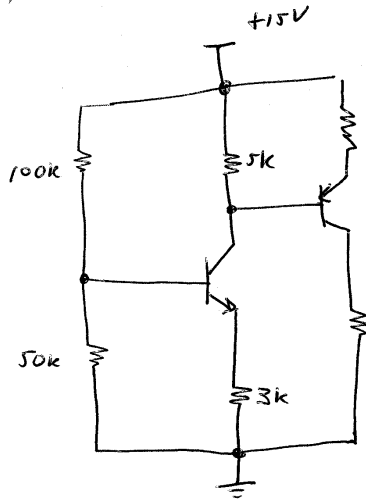

→

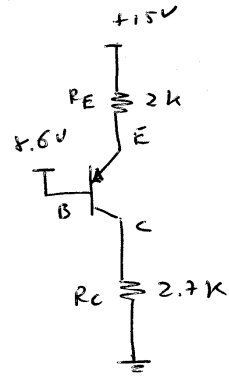

$$V_E = 0.6 + 0.7 = 0.93V$$

$$I_E = \frac{15 - 0.93}{2 \times 10^3} = 2.75 \text{ mA}$$

$$I_C = \frac{\beta}{\beta + 1} I_E = 2.75 \text{ mA}$$

$$V_C = R_C I_C = 2.7 \times 10^3 \times 2.75 \times 10^{-3}$$

$$V_C = 7.43V$$

$$I_D = \frac{I_C}{\beta} = 2.75 \mu\text{A}$$