

OP AMP ideal $v_+ = v_-$ $i_- = i_+ = 0$

$$i_{in} = \frac{v_{in} - v_{out}}{R_3} \quad (1)$$

$$v_- = v_{in} = \frac{R_1}{R_1 + R_2} v_{out}$$

logo $v_{out} = \left(1 + \frac{R_2}{R_1}\right) v_{in}$

Substituindo em (1)


$$i_{in} = \frac{v_{in} - \left(1 + \frac{R_2}{R_1}\right) v_{in}}{R_3}$$

$$i_{in} = -\frac{1}{R_3} \frac{R_2}{R_1} v_{in}$$

logo $R_{in} = \frac{v_{in}}{i_{in}} = -\frac{R_1}{R_2} R_3$

- $R_1 = 10 \text{ k}$
- $R_2 = 5 \text{ k}$
- $R_3 = 1 \text{ k}$

logo $R_{in} = -2 \text{ k } \Omega$

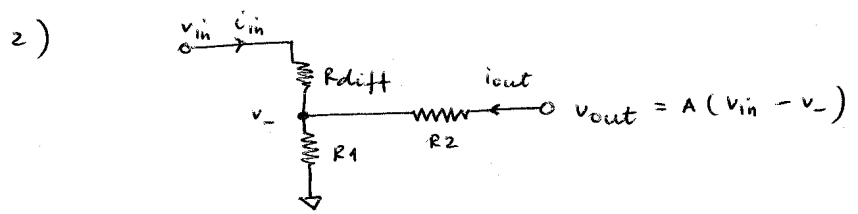

$$v_- = R_1 (i_{in} + i_{out})$$

$$v_- = R_2 \left(\frac{v_{in} - v_-}{R_{diff}} + \frac{v_{out} - v_-}{R_2} \right)$$

$$v_- \left(1 + \frac{R_1}{R_{diff}} + \frac{R_1}{R_2} \right) = \frac{R_1}{R_{diff}} v_{in} + \frac{R_1}{R_2} v_{out}$$

mas $v_- = -\frac{v_{out}}{A} + v_{in}$

substituindo

$$\left(1 + \frac{R_1}{R_2} \right) v_{in} = \left[\frac{1}{A} \left(1 + \frac{R_1}{R_{diff}} + \frac{R_1}{R_2} \right) + \frac{R_1}{R_2} \right] v_{out}$$

logo $A_V = \frac{v_{out}}{v_{in}} = \frac{1 + \frac{R_1}{R_2}}{\frac{1}{A} \left(1 + \frac{R_1}{R_{diff}} + \frac{R_1}{R_2} \right) + \frac{R_1}{R_2}} = \frac{1 + \frac{1}{9}}{10^{-4} \left(1 + 0.9 + \frac{1}{9} \right) + \frac{1}{9}}$

Fazendo $A \rightarrow \infty$

$$A_V = \frac{R_2}{R_1} + 1 = 10$$

$$R_{in} = \frac{v_{in}}{i_{in}}$$

$$v_{in} = R_{diff} i_{in} + R_1 (i_{in} + i_{out}) \quad (1)$$

mas $i_{out} = \frac{A(v_{in} - v_-) - v_-}{R_2}$

mas $v_- = R_1 (i_{in} + i_{out})$

substituindo

$$i_{out} = \frac{A}{R_2} v_{in} - \frac{1}{R_2} (1+A) v_-$$

$$i_{out} = \frac{A}{R_2} v_{in} - \frac{R_1}{R_2} (1+A) (i_{in} + i_{out})$$

$$i_{out} \left(1 + \frac{R_1}{R_2} (1+A) \right) = \frac{A}{R_2} v_{in} - \frac{R_1}{R_2} (1+A) i_{in}$$

logo $i_{out} = \left[\frac{A}{R_2} v_{in} - \frac{R_1}{R_2} i_{in} (1+A) \right] / \left[1 + \frac{R_1}{R_2} (1+A) \right]$

substituindo em (1)

$$v_{in} = \left[R_{diff} + R_1 - \frac{R_1 \frac{R_1}{R_2} (1+A)}{1 + \frac{R_1}{R_2} (1+A)} \right] i_{in} + \frac{\frac{A R_1}{R_2} v_{in}}{1 + \frac{R_1}{R_2} (1+A)}$$

$$\left[1 - \frac{\frac{A R_1}{R_2}}{1 + \frac{R_1}{R_2} (1+A)} \right] v_{in} = \left[R_{diff} + R_1 - \frac{R_1 \frac{R_1}{R_2} (1+A)}{1 + \frac{R_1}{R_2} (1+A)} \right] i_{in}$$


Fazendo $A \rightarrow \infty$ vem

$$v_{in} =$$

3) A saída do OP tem apenas dois valores: +15V e -15V

(i) se $v_{out}(OPAMP) = +15V$ D2 conduz e $V_+ = 0.7V$

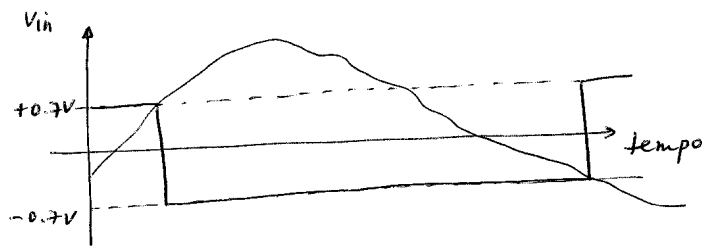(ii) se $v_{out}(OPAMP) = -15V$ D1 conduz e $V_+ = -0.7V$



$$4) I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (v_{GS} - v_T)^2$$

$$\text{mas } v_{GS} = v_G - v_S = 0 - (R_S I_D + v_{SS})$$

$$\text{logo } I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (-R_S I_D - v_{SS} - v_T)^2$$

substituido


$$I_D = \frac{0.5 \times 10^{-3}}{2} (-6 \times 10^3 I_D + 15 - 2)^2$$

$$4 \times 10^3 I_D = (13 - 6 \times 10^3 I_D)^2$$

$$I_D = \begin{cases} 0.017 \text{ A} \rightarrow V_S = 0.017 \times 6 \times 10^3 - 15 = -4.7 \text{ V OK} \\ 0.027 \text{ A} \rightarrow V_S = 0.027 \times 6 \times 10^3 - 15 = +1.7 \text{ V} \\ \text{IMPOSSIBLE} \end{cases}$$

logo $I_D = 17 \text{ mA}$, $V_{GS} = 4.7 \text{ V}$, $V_{DS} = 7.7 \text{ V}$

4b)

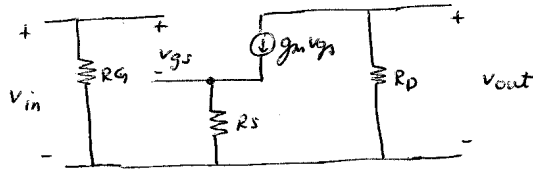

$$v_{out} = -g_m v_{gs} R_D$$

mas $v_{in} = v_{gs} + R_S g_m v_{gs}$

$$v_{in} = (1 + R_S g_m) v_{gs}$$


logo $v_{out} = - \frac{g_m R_D}{1 + R_S g_m} v_{in}$

$$A_V = - \frac{g_m R_D}{1 + R_S g_m} \quad \text{com} \quad g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{2 I_D}{(V_{GS} - V_T)}$$

$$A_V = - \frac{1.26 \times 10^{-3} \times 10^4}{1 + 1.26 \times 10^{-3} \times 6 \times 10^3} = -1.47 \quad g_m = \frac{2 \times 1.7 \times 10^{-3}}{2.7} = 1.26 \times 10^{-3} \text{ A/V}$$

4c) $R_{in} = R_G = 1 \text{ M}\Omega$

4d)

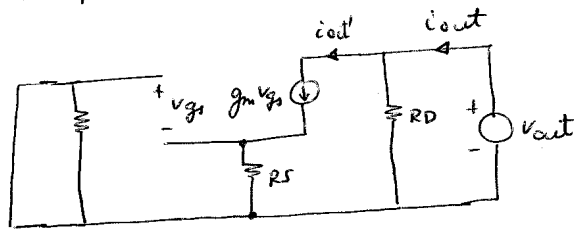

$$R_{out} = R_D \parallel R'_{out}$$

$$\text{com } R'_{out} = \frac{v_{out}}{i_{out}'}$$

$$\text{mas } i_{out}' = g_m v_{gs}$$

$$\text{mas } v_{gs} = -R_S i_{out}'$$

substituindo acima vem

$$i_{out}' = -g_m R_S i_{out}'$$

$$\text{logo } i_{out}' = 0$$

$$\text{logo } R'_{out} = \text{infinito}$$


5a) $V_{B1} = \frac{R_2}{R_1 + R_2} V_{CC} = 12 \text{ V}$

$$V_{E1} = V_{B2} = 11.3 \text{ V} \quad \rightarrow \quad I_{E1} = \frac{V_{E1}}{R_3} = 2 \text{ mA}$$


$$V_{E2} = 10.6 \text{ V} \quad \rightarrow \quad I_{E2} = \frac{V_{E2}}{R_4} = 7 \text{ mA}$$

5a)


1º andar

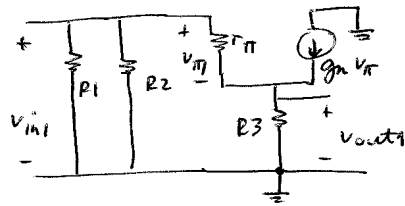

2º andar

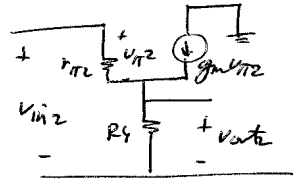

circuito equivalente

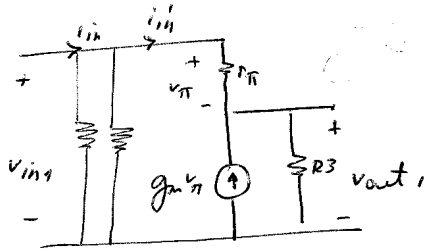

$$v_{out} = R3 (g_m v_{\pi1} + i_{in}')$$

$$\text{mas } i_{in}' = \frac{v_{\pi1}}{r_{\pi}}$$

$$\text{logo } v_{out} = R3 \left(g_m + \frac{1}{r_{\pi}} \right) v_{\pi1}$$

por outro lado

$$v_{in1} = v_{\pi1} + v_{out1}$$

$$\text{logo } v_{\pi1} = (v_{in1} - v_{out1})$$

$$\text{Fica } v_{out1} \left(1 + \frac{R3}{r_{\pi1}} \right) + R3 g_m v_{out1} = \left(R3 g_m + \frac{R3}{r_{\pi}} \right) v_{in1}$$

$$\text{logo } A_{v1} = \frac{v_{out1}}{v_{in1}} = \frac{R3 g_m + \frac{R3}{r_{\pi}}}{1 + R3 g_m + \frac{R3}{r_{\pi}}}$$

$$\text{com } g_m = \frac{\partial I_{C1}}{\partial V_{BE}} = \frac{I_{C1}}{V_T}$$

$$\text{e } r_{\pi} = \frac{V_T}{I_{B1}} = \beta / g_m$$

24.23.09.2009

6

$$A_{v2} = \frac{v_{out2}}{i_{out2}} = \frac{R_4 g_{m2} + \frac{R_4}{r_{\pi 2}}}{1 + R_4 g_{m2} + \frac{R_4}{r_{\pi 2}}}$$

$$\text{com } g_{m2} = \frac{I_{c2}}{V_T}$$

$$\text{e } r_{\pi 2} = \frac{V_T}{I_{B2}} = \frac{\beta}{g_{m2}}$$

5b)

$$R'_{in1} = R_1 \parallel R_2 \parallel R'_{in1}$$

$$R'_{in1} = \frac{v_{in1}}{i'_{in1}}$$

mas $v_{in1} = r_{\pi} i'_{in1} + (i'_{in1} + g_m v_{\pi}) R_3$

$$v_{in1} = r_{\pi} i'_{in1} + (i'_{in1} + g_m r_{\pi} i'_{in1}) R_3$$


$$v_{in1} = (r_{\pi} + R_3 + g_m r_{\pi} R_3) i'_{in1}$$

logo $R'_{in1} = r_{\pi} + (1 + g_m r_{\pi}) R_3$


logo $R_{in1} = R_1 \parallel R_2 \parallel [r_{\pi} + (1 + g_m r_{\pi}) R_3]$

logo $R_{in2} = r_{\pi 2} + (1 + g_{m2} r_{\pi 2}) R_4$

5c)

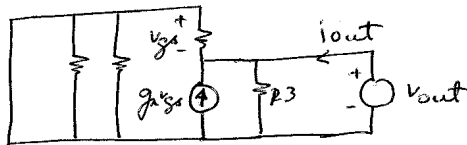


Circuito equivalente

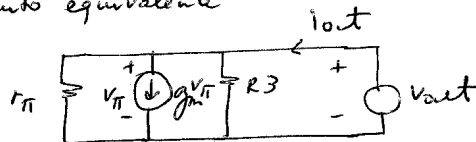

logo $R_{out1} = R_3 \parallel R_{\pi 1} \parallel \frac{1}{g_{m1}}$

logo $R_{out2} = R_4 \parallel r_{\pi 2} \parallel \frac{1}{g_{m2}}$

circuito equivalente total

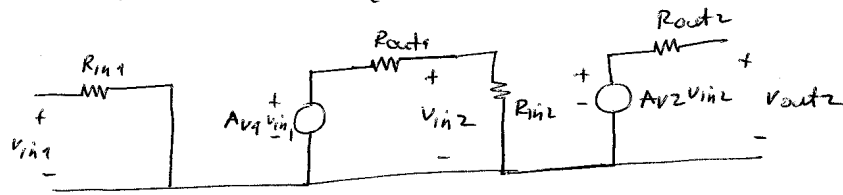

ganho total

$$A_v = A_{v1} \times A_{v2} \times \frac{R_{in2}}{R_{out1} + R_{in2}}$$

Resistência de entrada

$$R_{in} = R_{in1}$$

Resistência de saída

$$R_{out} = R_{out2}$$