

University of Toronto

Final Exam

Date - Dec 13, 2012 (9:30am to 12pm)

Duration: 2.5 hrs

ECE331 — Analog Electronics

Lecturer - D. Johns

ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY

1. Equation sheet is on last page of test.
 2. Unless otherwise stated, use transistor parameters on equation sheet.
 3. Non-programmable calculator allowed; No other aids allowed
 4. Grading indicated by []. Attempt all questions since a blank answer will certainly get 0.
-

Last Name: _____


First Name: _____

Student #: _____

Question	Mark
1	
2	
3	
4	
5	
6	
Total	

(max grade = 36)

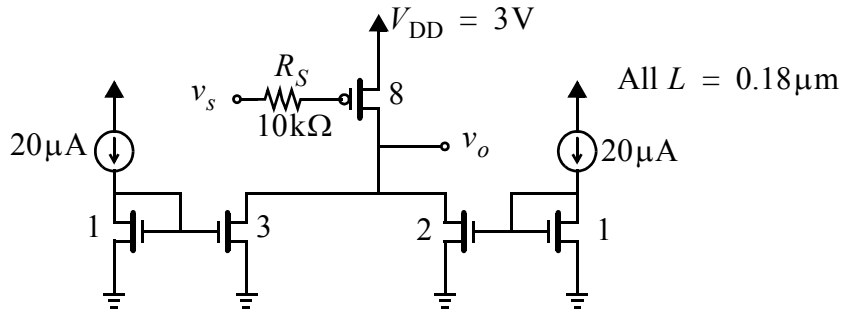[6] **Question 1:** Consider the circuit below where all transistors are in the active region. The numbers beside the transistors indicate the transistor width (in μm).




a) Find the small-signal gain v_o/v_s

$v_o/v_s =$

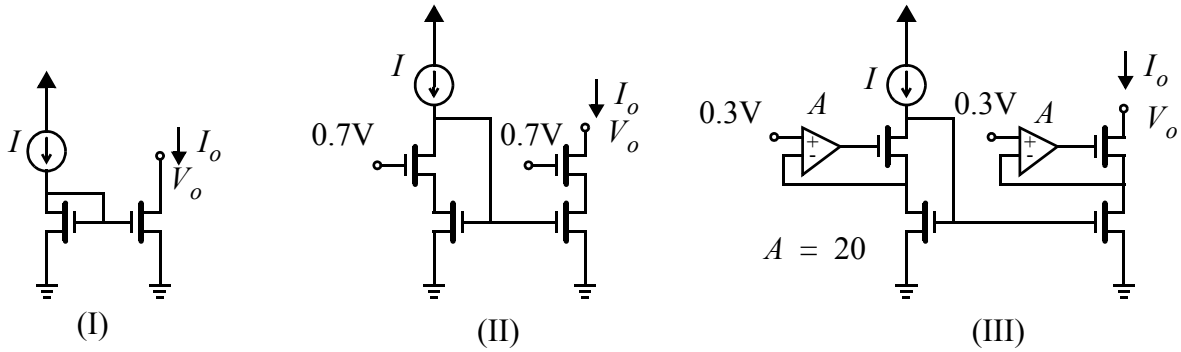b) Estimate the 3db frequency cutoff, f_{3dB} . For C_{db} values assume $V_{db} = 0$.

$f_{3dB} =$

[6] **Question 2:** Consider the 3 current mirrors shown below. For all transistors, $L = 0.18\mu m$, $W = 3\mu m$. Also, $I = 100\mu A$.



a) For the current mirror in (I), estimate the **change** in the output current for an output voltage **change** of $0.5V$. Also, what is the minimum output voltage, $V_{o(\min)}$, while keeping transistors in the active region.

$\Delta I =$
$V_{o(\min)} =$


b) Repeat question a) for the mirror in (II)

$\Delta I =$
$V_{o(\min)} =$

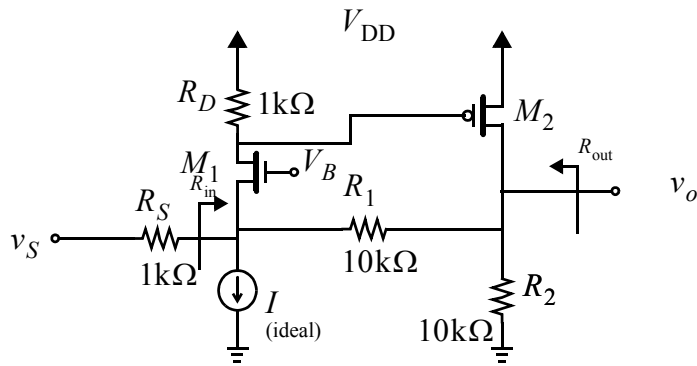c) Repeat question a) for the mirror in (III)

$\Delta I =$
$V_{o(\min)} =$

[6] Question 3: Consider the circuit below.



$$g_{m1} = g_{m2} = 2\text{mA/V}$$

$$r_{o1} = r_{o2} \rightarrow \infty$$


a) Find L , A_{∞} and d .

$L =$
$A_{\infty} =$
$d =$

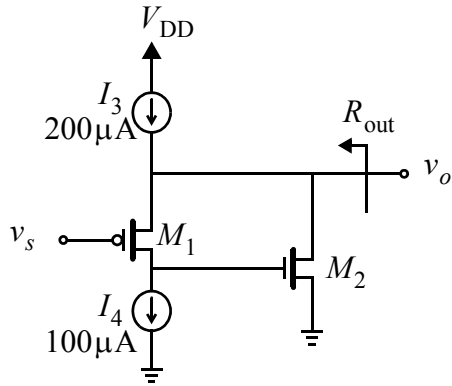b) Find v_o/v_s , R_{in} and R_{out} .

$v_o/v_s =$
$R_{in} =$
$R_{out} =$

[6] **Question 4:** The circuit below is called a “super source follower”. Assume the current sources are realized using single transistors with $L = 0.18\mu\text{m}$ (include their output resistances r_{o3} and r_{o4}).




All $L = 0.18\mu\text{m}$
 All $|V_{ov}| = 200\text{mV}$

Find the value for the output resistance, R_{out} , assuming $g_m r_o \gg 1$.

$R_{out} =$

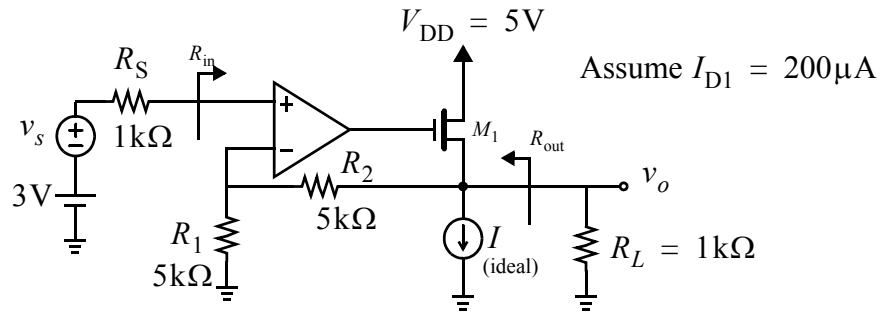[6] **Question 5:** Consider the circuit shown below. For the opamp, $A_o = 40$, $R_{id} = 10\text{k}\Omega$, $R_o = 1\text{k}\Omega$. For M_1 , $V_{ov} = 200\text{mV}$ and $L = 0.18\mu\text{m}$ (include r_o).



a) Find L , A_∞ (assume d is about 0).

$L =$
$A_\infty =$

b) Find v_o/v_s , R_{in} and R_{out} .


$v_o/v_s =$
$R_{in} =$
$R_{out} =$

[6] **Question 6:** Assume an opamp is ideal but has the following open-loop gain and will be used in a non-inverting configuration with 2 resistors.


$$A(s) = \frac{10^4}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})(1 + s/\omega_{p3})} \text{ where } \omega_{p1} = 10^5, \omega_{p2} = 10^7, \omega_{p3} = 10^8.$$

a) Draw the Bode plot for the above open-loop gain (both mag and phase)

Mag

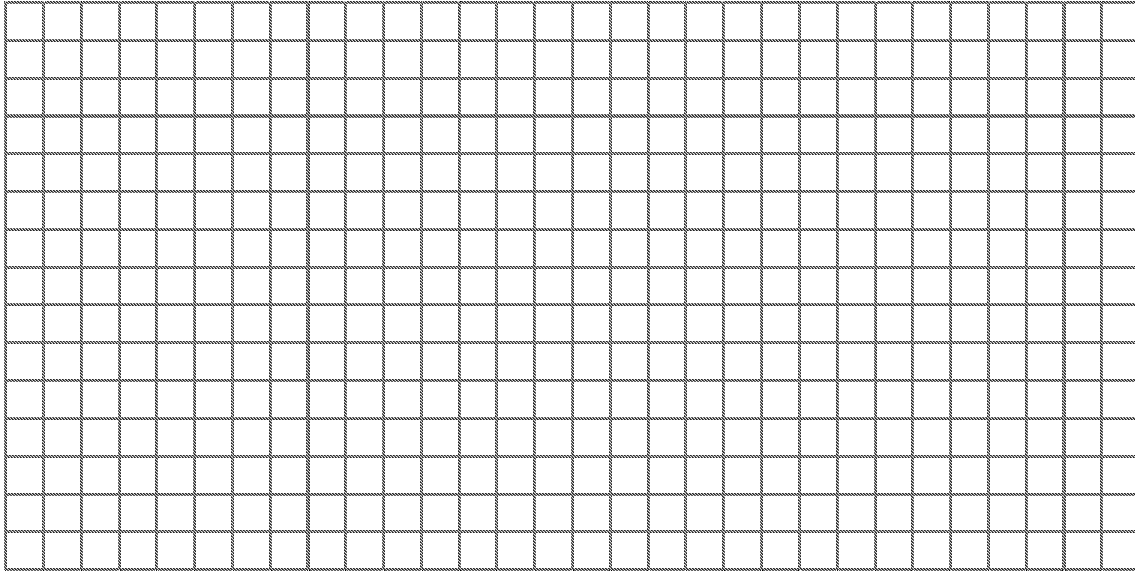

Phase

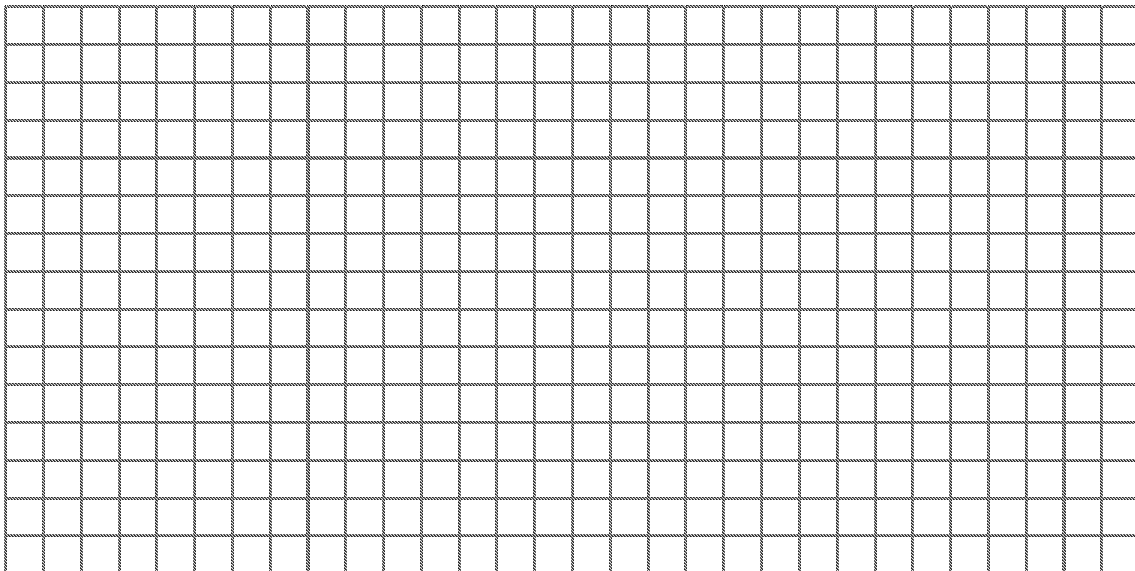

b) Estimate the minimum closed-loop gain, A_{\min} , that can be realized while having a phase margin about 45°

$$A_{\min} =$$

c) If it is desired to have a closed-loop gain of 10 estimate the new value of ω_{p1} if it is moved to a lower freq and a phase margin of about 45° is desired.

$$\omega_{p1}' =$$

ECE331

Analog Electronics

Equation Sheet

Constants: $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$; $q = 1.602 \times 10^{-19} \text{ C}$; $V_T = kT/q \approx 26\text{mV}$ at $300 \text{ }^\circ\text{K}$;

$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$; $k_{ox} = 3.9$; $C_{ox} = (k_{ox}\epsilon_0)/t_{ox}$

NMOS: $k_n = \mu_n C_{ox}(W/L)$; $V_{in} > 0$; $v_{DS} \geq 0$; $v_{ov} = v_{GS} - V_{tn}$

(triode) $v_{DS} \leq v_{ov}$ (or $v_D < v_G - V_{tn}$); $i_D = k_n((v_{ov})v_{DS} - (v_{DS}^2/2))$

(active) $v_{DS} \geq v_{ov}$; $i_D = 0.5k_n v_{ov}^2(1 + \lambda v_{DS})$; $g_m = k_n V_{ov} = 2I_D/V_{ov} = \sqrt{2k_n I_D}$; $r_s = 1/g_m$; $r_o = L/(|\lambda'|I_D)$


PMOS: $k_p = \mu_p C_{ox}(W/L)$; $V_{tp} < 0$; $v_{SD} \geq 0$; $v_{ov} = v_{SG} - |V_{tp}|$

(triode) $v_{SD} \leq v_{ov}$ (or $(v_D > v_G + |V_{tp}|)$); $i_D = k_p((v_{ov})v_{SD} - (v_{SD}^2/2))$

(active) $v_{SD} \geq v_{ov}$; $i_D = 0.5k_p v_{ov}^2(1 + |\lambda|v_{SD})$; $g_m = k_p V_{ov} = 2I_D/V_{ov} = \sqrt{2k_p I_D}$; $r_s = 1/g_m$; $r_o = L/(|\lambda'|I_D)$

BJT: (active) $i_C = I_S e^{(v_{BE}/V_T)}(1 + (v_{CE}/V_A))$; $g_m = \alpha/r_e = I_C/V_T$; $r_\pi = \beta/g_m$; $r_o = |V_A|/I_C$

$i_C = \beta i_B$; $i_E = (\beta + 1)i_B$; $\alpha = \beta/(\beta + 1)$; $i_C = \alpha i_E$; $R_b = (\beta + 1)(r_e + R_E)$; $R_e = (R_B + r_\pi)/(\beta + 1)$

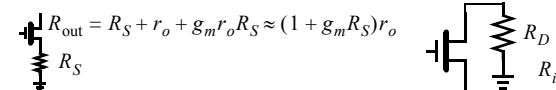Cascode: 

Diff Pair: $A_d = g_m R_D$; $A_{CM} = -(R_D/(2R_{SS}))((\Delta R_D)/R_D)$; $A_{CM} = -(R_D/(2R_{SS}))((\Delta g_m)/g_m)$

$V_{os} = \Delta V_t$; $V_{os} = (V_{ov}/2)((\Delta R_D)/R_D)$; $V_{os} = (V_{ov}/2)((\Delta(W/L))/(W/L))$

1st order: step response $y(t) = Y_\infty - (Y_\infty - Y_{0+})e^{-t/\tau}$ unity gain freq for $T(s) = \frac{A_M}{1 + s/\omega_{3dB}}$ $f_t \approx |A_M|\omega_{3dB}$ when $A_M \gg 1$

Freq: for real axis poles/zeros $T(s) = k_{dc} \frac{(1 + s/z_1)(1 + s/z_2) \dots (1 + s/z_m)}{(1 + s/\omega_1)(1 + s/\omega_2) \dots (1 + s/\omega_n)}$

OTC estimate $f_H = 1/(2\pi \sum \tau_i)$; dominant pole estimate $f_H = 1/(2\pi \tau_{max})$

Miller: $Z_1 = Z/(1 - K)$; $Z_2 = Z/(1 - 1/K)$

Mos caps: $C_{gs} = (2/3)WLC_{ox} + WL_{ov}C_{ox}$; $C_{gd} = WL_{ov}C_{ox}$; $C_{db} = C_{db0}/(\sqrt{1 + V_{db}/V_0})$

$f_t = g_m/(2\pi(C_{gs} + C_{gd}))$ assuming $C_{gd} \ll C_{gs}$ $f_t = (3\mu V_{ov})/(4\pi L^2)$

Feedback: $A_f = A/(1 + A\beta)$; $x_i = (1/(1 + A\beta))x_s$; $dA_f/A_f = (1/(1 + A\beta))dA/A$; $\omega_{Hf} = \omega_H(1 + A\beta)$; $\omega_{Lf} = \omega_L/(1 + A\beta)$

Loop Gain $L \equiv -s_r/s_t$; $A_f = A_\infty(L/(1 + L)) + d/(1 + L)$; $Z_{port} = Z_{port(k=0)}((1 + L_S)/(1 + L_O))$

PM = $\angle L(j\omega_1) + 180$; GM = $-|L(j\omega_{180})|_{dB}$

Pole Splitting $\omega_{p1}' \approx 1/(g_m R_2 C_f R_1)$; $\omega_{p2}' \approx (g_m C_f)/(C_1 C_2 + C_f(C_1 + C_2))$

Pole Pair $s^2 + (\omega_o/Q)s + \omega_o^2 = 0$; $Q \leq 0.5 \Rightarrow$ real poles; $Q > 1/\sqrt{2} \Rightarrow$ freq resp peaking

MOS Transistor: CMOS basic parameters. Channel length = $0.18\mu m$

	V_t (V)	μC_{ox} ($\mu A/V^2$)	λ' ($\mu m/V$)	C_{ox} ($fF/\mu m^2$)	t_{ox} (nm)	L_{ov} (μm)	$\frac{C_{db0}}{W}$ ($\frac{fF}{\mu m}$)
NMOS	0.4	240	0.05	8.5	4	0.04	0.3
PMOS	-0.4	60	-0.05	8.5	4	0.04	0.3