

University of Toronto

Term Test 1

Date - Oct 12, 2012 (3:15pm to 4:45pm)

Duration: 1.5 hrs

ECE331 — Analog Electronics

Lecturer - D. Johns

ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY

1. Equation sheet is on last page of test.
 2. Unless otherwise stated, use transistor parameters on equation sheet.
 3. Non-programmable calculator allowed; No other aids allowed
 4. Grading indicated by []. Attempt all questions since a blank answer will certainly get 0.
-

Last Name: _____


First Name: _____

Student #: _____

Question	Mark
1	
2	
3	
4	
5	
6	
Total	

(max grade = 36)

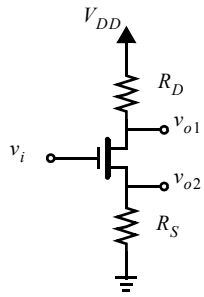
[6] **Question 1:** For the nmos circuit below, draw the small-signal T-model and derive expressions for v_{o1}/v_i and v_{o2}/v_i in terms of R_D , R_S and $r_s = 1/g_m$. Assume $\lambda = 0$.



$$\frac{v_{o1}}{v_i} =$$


$$\frac{v_{o2}}{v_i} =$$

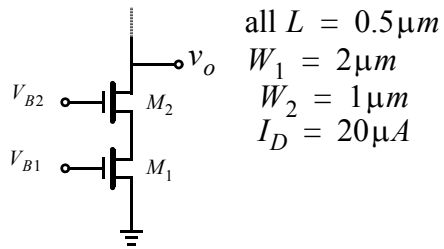[6] **Question 2:** Consider the current mirror below. If the current mirror is designed for a current of $20\mu A$, find the voltages V_{B1} and V_{B2} such that v_o can go as low as possible while the transistors remain in the active region. Find the minimum output voltage, v_{O_min} ?




$V_{B1} =$
$V_{B2} =$
$v_{O_min} =$

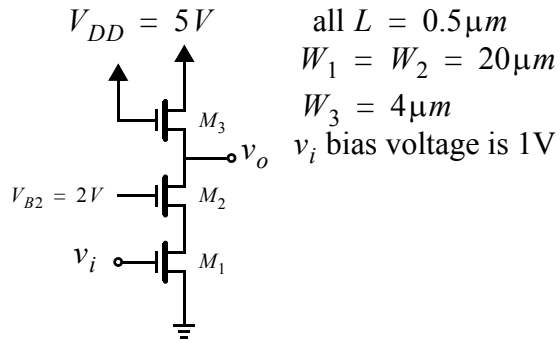[6] **Question 3:** Find the small-signal gain, v_o/v_i and output resistance R_o . (ignore r_o when finding i_{sc} but include r_o when finding R_o).




$\frac{v_o}{v_i} =$
$R_o =$

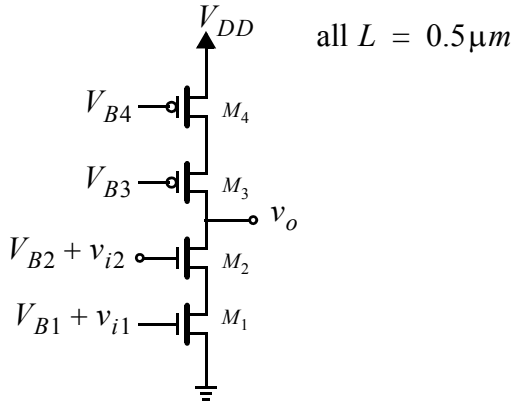[6] **Question 4:** For the circuit below, all $V_{ov} = 200mV$ and all $I_D = 50\mu A$. The designer is concerned about noise on V_{B1} and V_{B2} bias lines. Find the gains v_o/v_{i1} and v_o/v_{i2} . (Include r_{o1} when finding i_{SC} for v_o/v_{i2} otherwise ignore r_o when finding i_{SC})



$\frac{v_o}{v_{i1}} =$
$\frac{v_o}{v_{i2}} =$

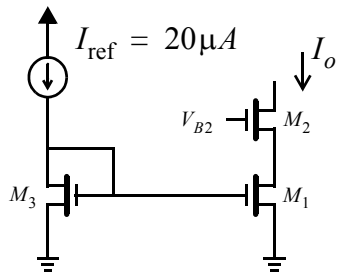
[6] **Question 5:** Consider the current mirror shown below. Using small-signal analysis, estimate the change in I_o when there is a V_{tn} mismatch of 5mV between M_1 and M_3 . Ignore r_o .



all $L = 0.5\mu m$
 $W_1 = W_2 = W_3 = 2\mu m$

$\Delta I_o =$

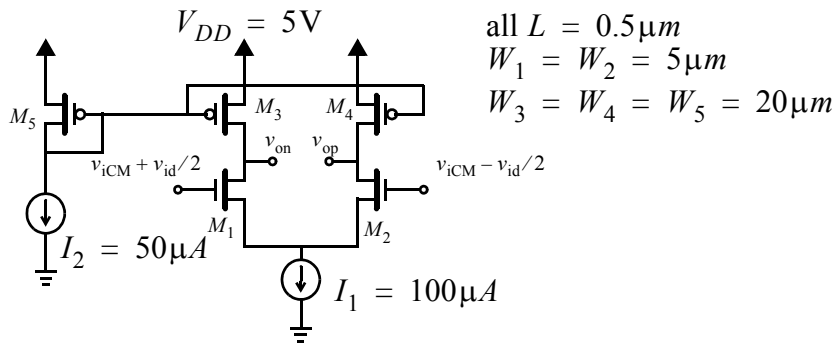[6] Question 6: Consider the circuit below where $v_{iCM} = 2V$.



a) What is the max and min for v_{op} ?

$v_{op_min} =$
$v_{op_max} =$

b) Find the gain, v_o/v_{id} .

$v_o/v_{id} =$

ECE331

Analog Electronics


Equation Sheet

Constants: $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$; $q = 1.602 \times 10^{-19} \text{ C}$; $V_T = kT/q \approx 26\text{mV}$ at $300 \text{ }^\circ\text{K}$;
 $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$; $k_{ox} = 3.9$; $C_{ox} = (k_{ox}\epsilon_0)/t_{ox}$

NMOS: $k_n = \mu_n C_{ox}(W/L)$; $V_{tn} > 0$; $v_{DS} \geq 0$; $v_{ov} = v_{GS} - V_{tn}$
 (triode) $v_{DS} \leq v_{ov}$ (or $v_D < v_G - V_{tn}$); $i_D = k_n((v_{ov})v_{DS} - (v_{DS}^2/2))$
 (active) $v_{DS} \geq v_{ov}$; $i_D = 0.5k_n v_{ov}^2(1 + \lambda v_{DS})$; $g_m = k_n V_{ov} = 2I_D/V_{ov} = \sqrt{2k_n I_D}$; $r_s = 1/g_m$; $r_o = L/(|\lambda'|I_D)$

PMOS: $k_p = \mu_p C_{ox}(W/L)$; $V_{tp} < 0$; $v_{SD} \geq 0$; $v_{ov} = v_{SG} - |V_{tp}|$
 (triode) $v_{SD} \leq v_{ov}$ (or $(v_D > v_G + |V_{tp}|)$); $i_D = k_p((v_{ov})v_{SD} - (v_{SD}^2/2))$
 (active) $v_{SD} \geq v_{ov}$; $i_D = 0.5k_p v_{ov}^2(1 + |\lambda|v_{SD})$; $g_m = k_p V_{ov} = 2I_D/V_{ov} = \sqrt{2k_p I_D}$; $r_s = 1/g_m$; $r_o = L/(|\lambda'|I_D)$

BJT: (active) $i_C = I_S e^{(v_{BE}/V_T)}(1 + (v_{CE}/V_A))$; $g_m = \alpha/r_e = I_C/V_T$; $r_\pi = \beta/g_m$; $r_o = |V_A|/I_C$
 $i_C = \beta i_B$; $i_E = (\beta + 1)i_B$; $\alpha = \beta/(\beta + 1)$; $i_C = \alpha i_E$; $R_b = (\beta + 1)(r_e + R_E)$; $R_e = (R_B + r_\pi)/(\beta + 1)$

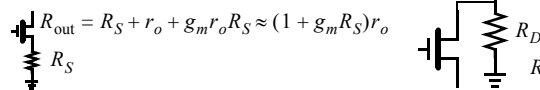Cascode:  $R_{out} = R_S + r_o + g_m r_o R_S \approx (1 + g_m R_S)r_o$ $R_{in} = (R_D + r_o)/(1 + g_m r_o) \approx R_D/(g_m r_o) + 1/g_m$

Diff Pair: $A_d = g_m R_D$; $A_{CM} = -(R_D/(2R_{SS}))((\Delta R_D)/R_D)$; $A_{CM} = -(R_D/(2R_{SS}))((\Delta g_m)/g_m)$
 $V_{os} = \Delta V_t$; $V_{os} = (V_{ov}/2)((\Delta R_D)/R_D)$; $V_{os} = (V_{ov}/2)((\Delta(W/L))/(W/L))$

MOS Transistor: CMOS basic parameters. Channel length = $0.18\mu\text{m}$

	V_t (V)	μC_{ox} ($\mu\text{A}/\text{V}^2$)	λ' ($\mu\text{m}/\text{V}$)	C_{ox} ($\text{fF}/\mu\text{m}^2$)	t_{ox} (nm)
NMOS	0.4	240	0.05	8.5	4
PMOS	-0.4	60	-0.05	8.5	4