

University of Toronto

Term Test 1

Date - Oct 12, 2012 (3:15pm to 4:45pm)

Duration: 1.5 hrs

ECE331 — Analog Electronics

Lecturer - D. Johns

ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY

1. Equation sheet is on last page of test.
2. Unless otherwise stated, use transistor parameters on equation sheet.
3. Non-programmable calculator allowed; No other aids allowed
4. Grading indicated by []. Attempt all questions since a blank answer will certainly get 0.

Last Name: SOLUTIONS


First Name: _____

Student #: _____

Question	Mark
1	
2	
3	
4	
5	
6	
Total	


(max grade = 36)

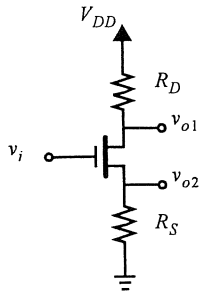[6] **Question 1:** For the nmos circuit below, draw the small-signal T-model and derive expressions for v_{o1}/v_i and v_{o2}/v_i in terms of R_D , R_S and $r_s = 1/g_m$. Assume $\lambda = 0$.



$$\frac{v_{o1}}{v_i} = -\frac{R_D}{r_s + R_S}$$
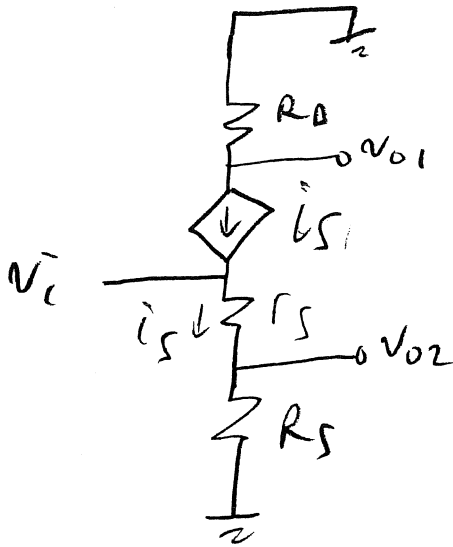
$$\frac{v_{o2}}{v_i} = \frac{R_S}{r_s + R_S}$$



$$i_s = \frac{v_i}{r_s + R_S}$$


$$v_{o1} = -i_s R_D = -\frac{R_D}{r_s + R_S} v_i$$

$$\frac{v_{o1}}{v_i} = -\frac{R_D}{r_s + R_S}$$

$$v_{o2} = \frac{R_S}{r_s + R_S} v_i$$

$$\frac{v_{o2}}{v_i} = \frac{R_S}{r_s + R_S}$$

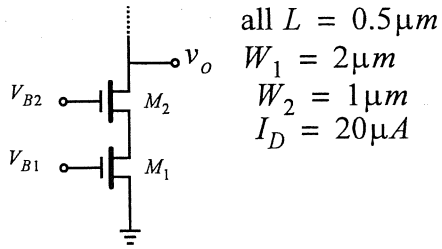[6] **Question 2:** Consider the current mirror below. If the current mirror is designed for a current of $20\mu A$, find the voltages V_{B1} and V_{B2} such that v_O can go as low as possible while the transistors remain in the active region. Find the minimum output voltage, v_{O_min} ?



$$V_{B1} = 0.604$$

$$V_{B2} = 1.293V$$

$$v_{O_min} = 0.493V$$

$$i_{D1} = \frac{\mu_n C_{ox}}{2} \left(\frac{W_1}{L}\right) (V_{ov1})^2$$

$$20\mu A = \left(\frac{240e-6}{2}\right) (4) V_{ov1}^2 \Rightarrow V_{ov1} = 0.204V$$

$$i_{D2} = i_{D1} \Rightarrow 20\mu A = \left(\frac{240e-6}{2}\right) (2) V_{ov2}^2 \Rightarrow V_{ov2} = 0.289V$$


$$V_{B1} = V_{ov1} + V_{tn} = 0.204 + 0.4 = 0.604$$

$$\downarrow \text{min } V_{D2} = V_{ov1} = 0.204V$$

$$V_{B2} = V_{ov2} + V_{tn} + V_{D2} = 0.893V$$

$$v_{O_min} = V_{ov1} + V_{ov2} = 0.493V$$

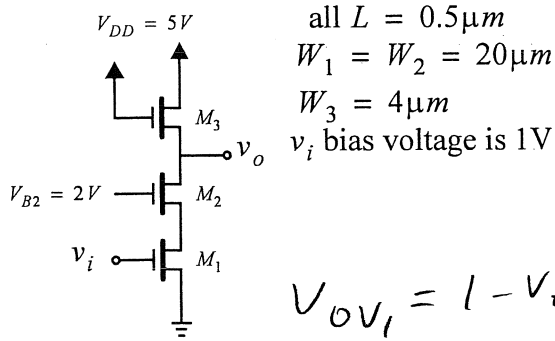[6] Question 3: Find the small-signal gain, v_o/v_i and output resistance R_o . (ignore r_o when finding i_{sc} but include r_o when finding R_o).



$\frac{v_o}{v_i} = -2.16 \frac{V}{V}$
$R_o = 750 \Omega$

$V_{OV1} = 1 - V_{tn} = 0.3V$

$I_{D1} = \left(\frac{\mu_n C_{ox}}{2}\right) \left(\frac{W_1}{L}\right) (V_{OV1})^2 = 432 \mu A$

$g_{m1} = \frac{2I_D}{V_{OV1}} = 2.88 \text{ mA/V} \Rightarrow r_{s1} = 347 \Omega$

$g_{m2} = g_{m1}$ (SINCE $I_{D2} = I_{D1}$ & $W_2 = W_1$) & $g_{m3} = \sqrt{2\mu_n C_{ox} \left(\frac{W_3}{L}\right) I_D} = 1.29 \text{ mA}$

$r_o = \frac{L}{\lambda' I_D} = \frac{0.5}{(0.05)(432 \mu A)} = 23.1 \text{ k}\Omega$ $r_{s3} = 776 \Omega$

$i_{sc} = \frac{v_i}{r_{s1}} = \frac{v_i}{347}$

$R_o = r_{s3} \parallel r_{o3} \parallel [r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}]$
 $= 776 \parallel 23.1 \text{ k} \parallel 1.58 \text{ M} = 750 \Omega$


$v_o = -i_{sc} R_o = -\frac{R_o}{r_{s1}} v_i$

$\frac{v_o}{v_i} = -\frac{R_o}{r_{s1}} = -\frac{750 \Omega}{347 \Omega} = -2.16 \frac{V}{V}$

NOTE $\frac{v_o}{v_i} \approx -\frac{g_{m1}}{g_{m3}} = \sqrt{5}$

[6] **Question 4:** For the circuit below, all $V_{ov} = 200mV$ and all $I_D = 50\mu A$. The designer is concerned about noise on V_{B1} and V_{B2} bias lines. Find the gains v_o/v_{i1} and v_o/v_{i2} .

(Include r_{o1} when finding i_{SC})

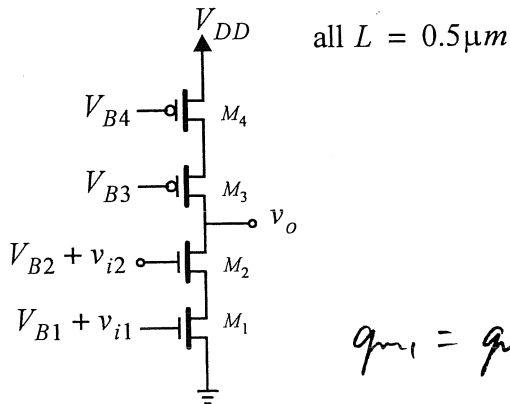

$\frac{v_o}{v_{i1}} = -5100 \frac{V}{V}$
$\frac{v_o}{v_{i2}} = -50.5 \frac{V}{V}$

$$g_{m1} = g_{m2} = g_{m3} = g_{m4} = \frac{2I_D}{V_{ov}} = 0.5mA/V$$

$$r_s = 2k\Omega = r_{s1} = r_{s2}$$

$$r_o = \frac{L}{\lambda' I_D} = 200k\Omega$$

$$R_o = R_{op} || (R_{on} + R_{op}) = R_{on} = r_o + r_o + g_m r_o r_o = 20.4M\Omega$$


$$R_o = 10.2M\Omega$$

$$\frac{v_o}{v_{i1}} = - \frac{1 \cdot R_o}{r_{s1}} = - \frac{10.2M}{2k} = -5100 \frac{V}{V}$$

$$i_{SC2} = \frac{v_{i2}}{r_{s2} + r_{o1}} \quad v_o = -i_{SC2} R_o = - \frac{R_o}{r_{s2} + r_{o1}} v_{i2}$$

$$\frac{v_o}{v_{i2}} = - \frac{R_o}{r_{s2} + r_{o1}} = - \frac{10.2M}{202k} = -50.5 \frac{V}{V}$$

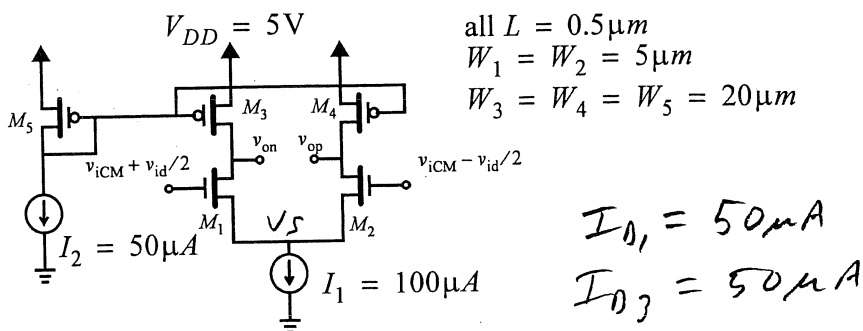[6] Question 6: Consider the circuit below where $v_{iCM} = 2V$.



a) What is the max and min for v_{op} ?

$$I_{D1} = \frac{\mu_n C_{ox}}{2} \left(\frac{W_1}{L}\right) V_{ov1}^2 \Rightarrow V_{ov1} = 0.204 V$$

$$I_{D3} = \frac{\mu_p C_{ox}}{2} \left(\frac{W_3}{L}\right) V_{ov3}^2 \Rightarrow V_{ov3} = 0.204 V$$

$$V_S = V_{iCM} - V_{ov1} - V_{tn} = 1.4 V$$

$$V_{op_min} = V_S + V_{ov1} = 1.6 V$$

$$V_{op_max} = V_{DD} - V_{ov3} = 4.8 V$$


$v_{op_min} = 1.6 V$
$v_{op_max} = 4.8 V$

b) Find the gain, v_o/v_{id} .

$$r_{o1} = \frac{L}{\lambda I_{D1}} = 200 k\Omega = r_{o3}$$

$$g_{m1} = \frac{2I_{D1}}{V_{ov1}} = 0.49 mA/V \quad r_{s1} = 2.04 k\Omega$$

$v_o/v_{id} = 49 V/V$

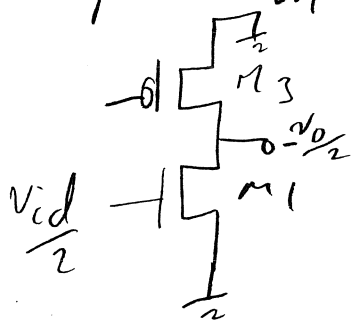

Half circuit

$$-\frac{v_o}{2} = -g_{m1}(r_{o1} || r_{o3}) \frac{v_{id}}{2}$$

$$\frac{v_o}{v_{id}} = g_{m1}(r_{o1} || r_{o2}) = 49 V/V$$

ECE331

Analog Electronics

Equation Sheet

Constants: $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$; $q = 1.602 \times 10^{-19} \text{ C}$; $V_T = kT/q \approx 26 \text{ mV}$ at $300 \text{ }^\circ\text{K}$;
 $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$; $k_{ox} = 3.9$; $C_{ox} = (k_{ox}\epsilon_0)/t_{ox}$


NMOS: $k_n = \mu_n C_{ox}(W/L)$; $V_{in} > 0$; $v_{DS} \geq 0$; $v_{ov} = v_{GS} - V_{tn}$
 (triode) $v_{DS} \leq v_{ov}$ (or $v_D < v_G - V_{tn}$); $i_D = k_n((v_{ov})v_{DS} - (v_{DS}^2/2))$

(active) $v_{DS} \geq v_{ov}$; $i_D = 0.5k_n v_{ov}^2(1 + \lambda v_{DS})$; $g_m = k_n V_{ov} = 2I_D/V_{ov} = \sqrt{2k_n I_D}$; $r_s = 1/g_m$; $r_o = L/(\lambda' I_D)$

PMOS: $k_p = \mu_p C_{ox}(W/L)$; $V_{ip} < 0$; $v_{SD} \geq 0$; $v_{ov} = v_{SG} - |V_{tp}|$
 (triode) $v_{SD} \leq v_{ov}$ (or $(v_D > v_G + |V_{tp}|)$); $i_D = k_p((v_{ov})v_{SD} - (v_{SD}^2/2))$

(active) $v_{DS} \geq v_{ov}$; $i_D = 0.5k_p v_{ov}^2(1 + |\lambda|v_{SD})$; $g_m = k_p V_{ov} = 2I_D/V_{ov} = \sqrt{2k_p I_D}$; $r_s = 1/g_m$; $r_o = L/(\lambda' |I_D|)$

BJT: (active) $i_C = I_S e^{(v_{BE}/V_T)}(1 + (v_{CE}/V_A))$; $g_m = \alpha/r_e = I_C/V_T$; $r_\pi = \beta/g_m$; $r_o = |V_A|/I_C$
 $i_C = \beta i_B$; $i_E = (\beta + 1)i_B$; $\alpha = \beta/(\beta + 1)$; $i_C = \alpha i_E$; $R_b = (\beta + 1)(r_e + R_E)$; $R_e = (R_B + r_\pi)/(\beta + 1)$

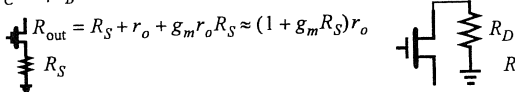Cascode:  $R_{out} = R_S + r_o + g_m r_o R_S \approx (1 + g_m R_S)r_o$
 $R_{in} = (R_D + r_o)/(1 + g_m r_o) \approx R_D/(g_m r_o) + 1/g_m$

Diff Pair: $A_d = g_m R_D$; $A_{CM} = -(R_D/(2R_{SS}))((\Delta R_D)/R_D)$; $A_{CM} = -(R_D/(2R_{SS}))((\Delta g_m)/g_m)$
 $V_{os} = \Delta V_t$; $V_{os} = (V_{ov}/2)((\Delta R_D)/R_D)$; $V_{os} = (V_{ov}/2)((\Delta(W/L))/(W/L))$

MOS Transistor: CMOS basic parameters. Channel length = $0.18 \mu\text{m}$

	V_t (V)	μC_{ox} ($\mu\text{A}/\text{V}^2$)	λ' ($\mu\text{m}/\text{V}$)	C_{ox} ($\text{fF}/\mu\text{m}^2$)	t_{ox} (nm)
NMOS	0.4	240	0.05	8.5	4
PMOS	-0.4	60	-0.05	8.5	4