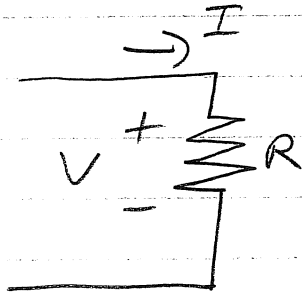


CIRCUIT REVIEW

OHMS LAW




$$I = \frac{V}{R}$$

$$V = IR$$

* IMPORTANT TO GET V "+" CORRECT WITH RESPECT TO I "→"

POWER DISSIPATED $P = VI$

KCL (KIRCHHOFF CURRENT LAW)

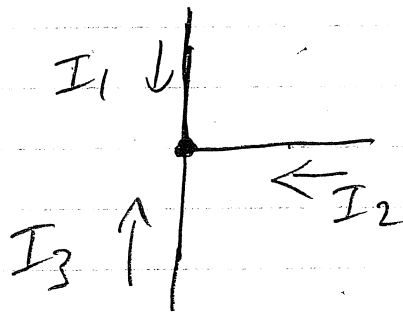


$$I_1 + I_2 + I_3 = 0$$

$$\sum_{k=1}^n I_k = 0$$

SUM OF CURRENTS FLOWING INTO A NODE EQUALS 0

KVL (KIRCHHOFF VOLTAGE LAW)

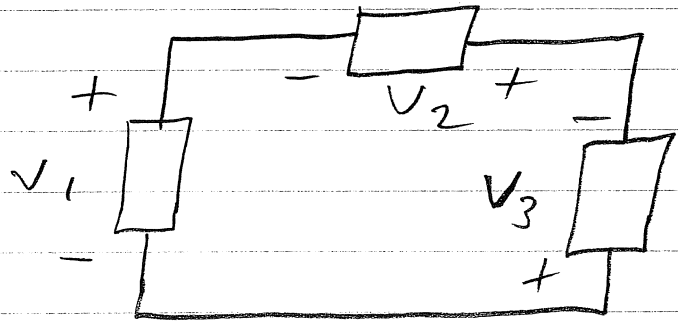

$$V_1 + V_2 + V_3 = 0$$


$$\sum_{R=1}^n V_R = 0$$

SUM OF VOLTAGES
AROUND A LOOP EQUALS 0

GETTING SIGNS CORRECT

CAN DEFINE I (OR V) ANYWAY YOU WANT BUT MUST HAVE I, V FOR ONE DEVICE TO BE CONSISTENT

Ex 1

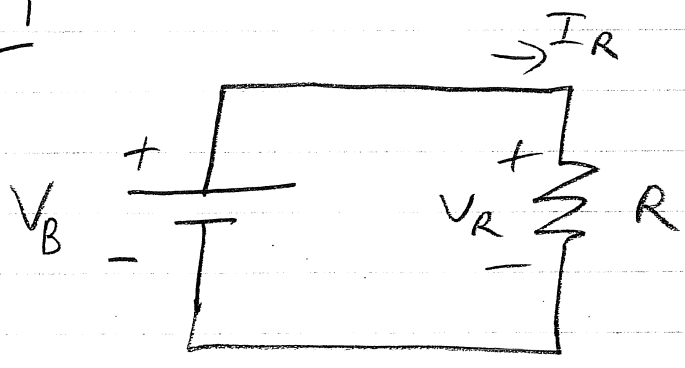

KVL

$$V_B - V_R = 0$$

$$V_R = V_B$$


$$I_R = \frac{V_R}{R} \quad \checkmark$$

IF $V_B = +1V$

$$R = 1\Omega \Rightarrow I_R = 1A$$

$$V_R = 1V$$

EX 2

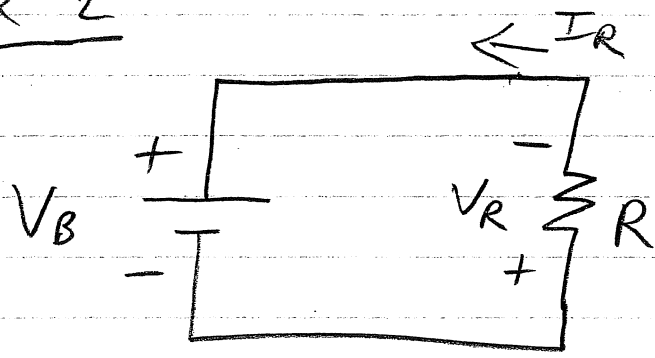

KVL

$$V_B + V_R = 0$$

$$V_R = -V_B$$

$$I_R = \frac{V_R}{R}$$


IF $V_B = 1V$
 $R = 1\Omega \Rightarrow I_R = \frac{-1V}{1\Omega} = -1A \checkmark$

$$V_R = -1V$$

EX 3

WRONG

I_R, V_R INCONSISTENT

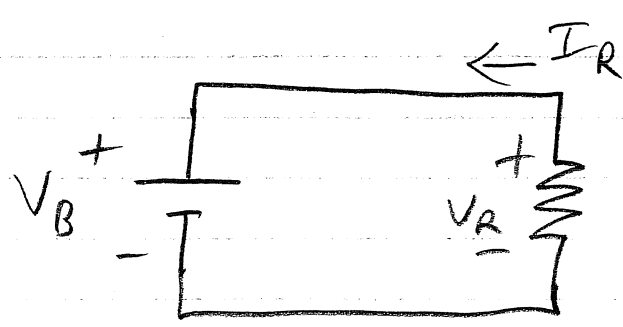

$$V_R = V_B$$

$$I_R = \frac{V_R}{R} \quad X$$


IF $V_B = 1V$
 $R = 1\Omega \Rightarrow I_R = 1A \quad X$

ACTUALLY


$$I_R = -1A$$

COULD USE $I_R = \frac{-V_R}{R}$ BUT WHY NOT
 JUST GET DEVICE I, V CONSISTENT.

INDEPENDENT SOURCES

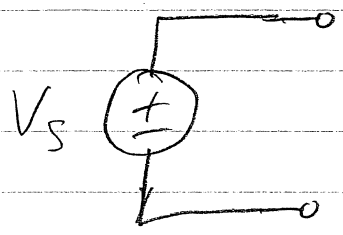


VOLTAGE

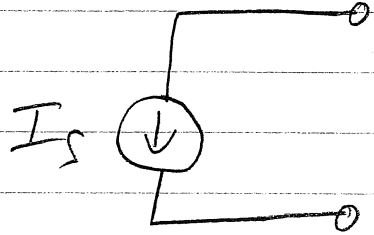


CURRENT

DEPENDENT SOURCES

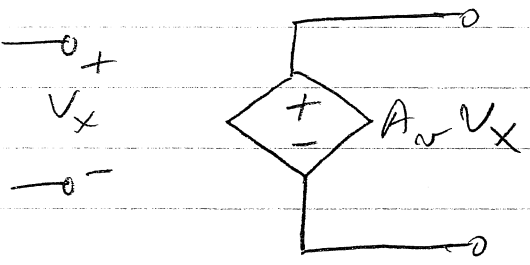


VCVS

VOLTAGE CONTROLLED
VOLTAGE SOURCE

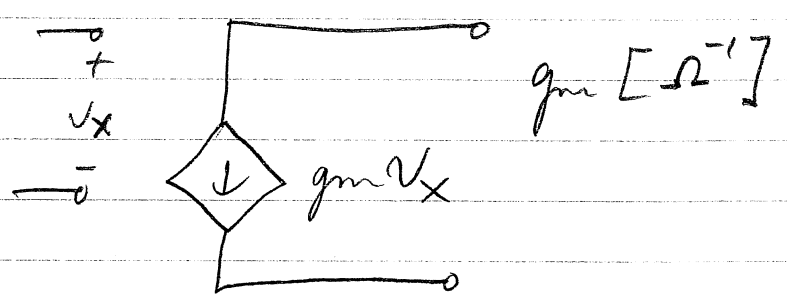


VCCS

VOLTAGE CONTROLLED
CURRENT SOURCE

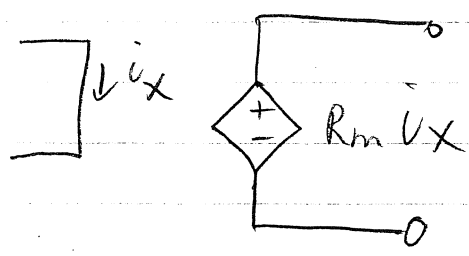

CCVS


$R_m [R]$

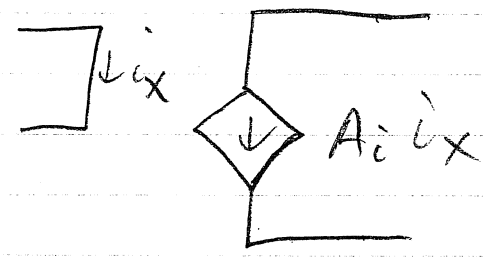

CCCS

VOLTAGE SOURCE EQUIVALENT
(THEVENIN EQUIVALENT)

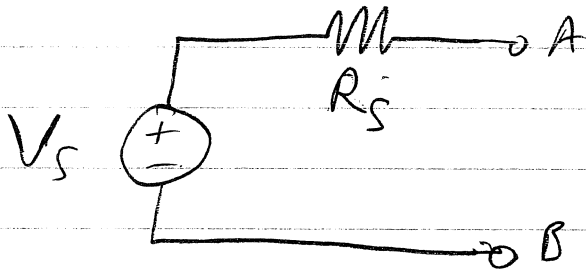A CIRCUIT OF VOLTAGE SOURCES,
CURRENT SOURCES AND RESISTORS
(INDEPENDENT + DEPENDENT SOURCES)
CAN BE CONVERTED TO




WHERE V_s IS OPEN CIRCUIT VOLTAGE, V_{OC}
SEEN AT A-B & R_s IS RESISTANCE
SEEN AT A-B WHEN INDEPENDENT

SOURCES ARE ZEROED.

VOLTAGE SOURCE ZEROED => SHORT CIRCUIT
CURRENT " " OPEN "

CURRENT SOURCE EQUIVALENT
(NORTON EQUIVALENT)

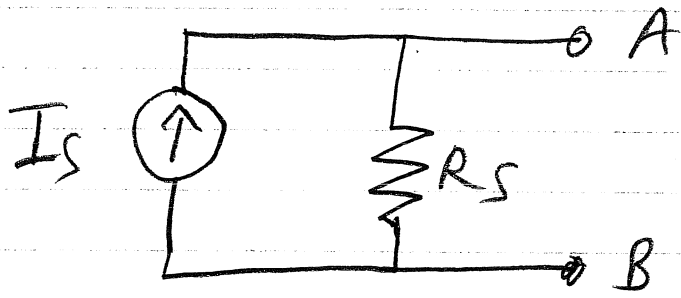A VOLTAGE SOURCE EQUIVALENT
CAN BE CONVERTED TO



$$I_s = \frac{V_s}{R_s}$$

I_s IS SHORT CIRCUIT CURRENT, I_{sc}
AT A-B


R_s IS RESISTANCE SEEN AT A-B
WHEN INDEPENDENT SOURCES ARE
ZEROED

NOTE $R_s = \frac{V_s}{I_s}$ OR $R_s = \frac{V_{oc}}{I_{sc}}$


$V_{oc} \Rightarrow V_{AB}$ WHEN OPEN CIRCUIT

$I_{sc} \Rightarrow I_{AB}$ WHEN SHORT CIRCUIT

Ex

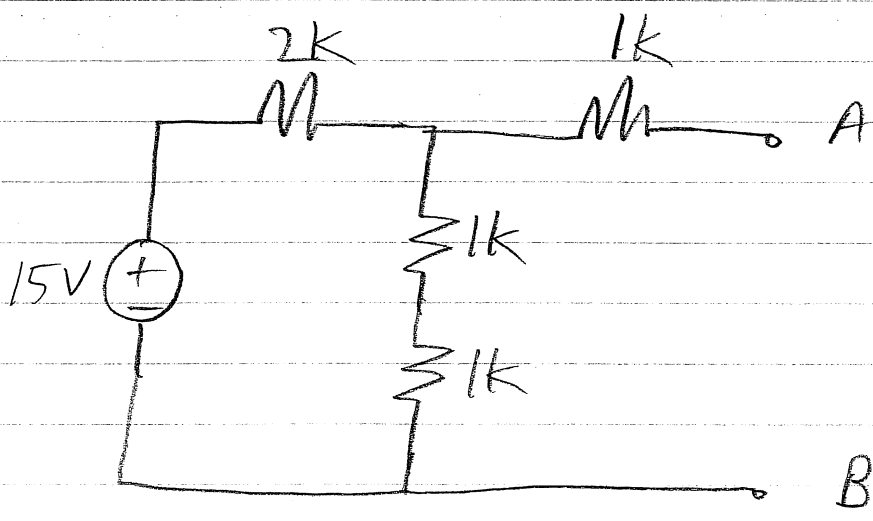


CALCULATE V_{oc}

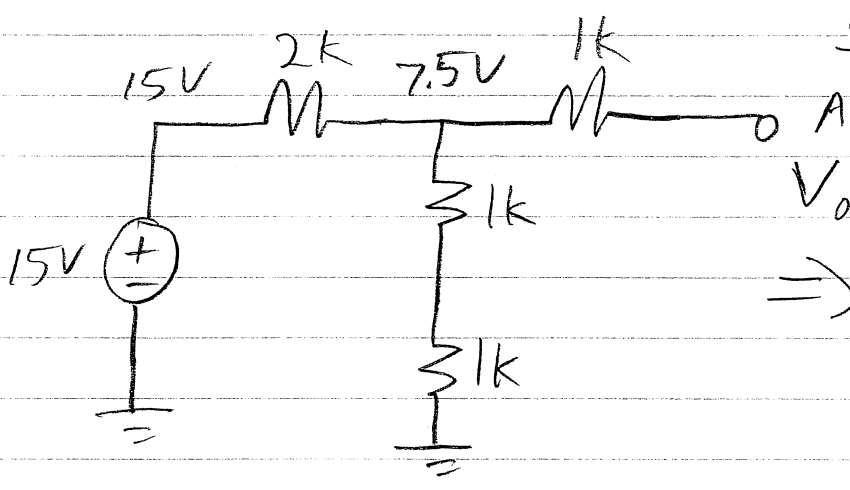


$V_{oc} = 7.5V$
 $\Rightarrow V_S = 7.5V$

CALCULATE R_S

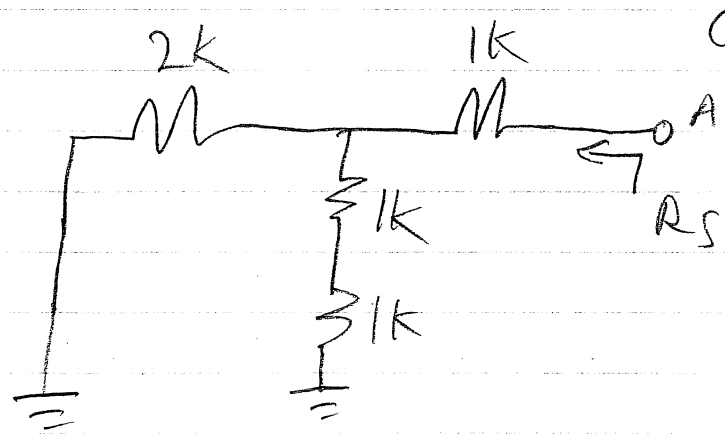


$R_S = 2k$

CR8

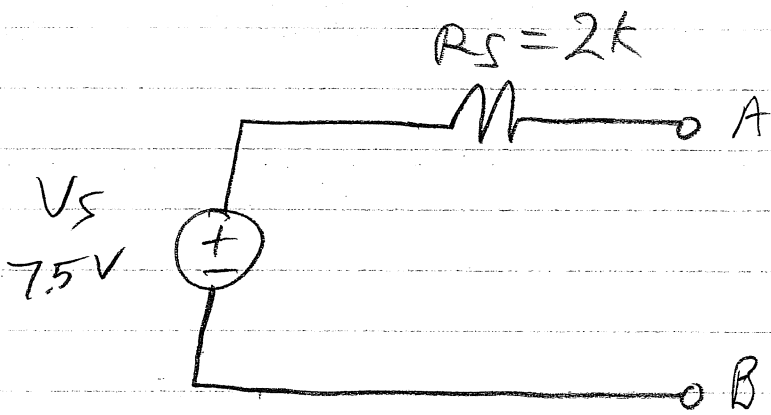

VOLTAGE SOURCE
EQUIVALENT

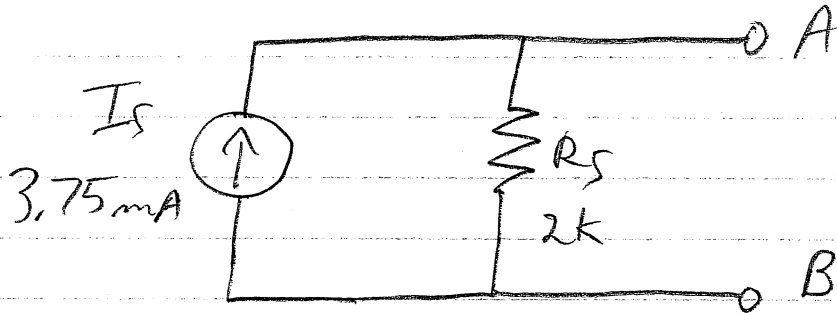


$$I_S = \frac{V_S}{R_S} = 3.75\text{mA}$$

WHEN TO USE VOLTAGE SOURCE OR CURRENT SOURCE?


EITHER CAN BE USED BUT BETTER INSIGHT IF ...

R_S SMALL \Rightarrow VOLTAGE SOURCE

R_S LARGE \Rightarrow CURRENT SOURCE

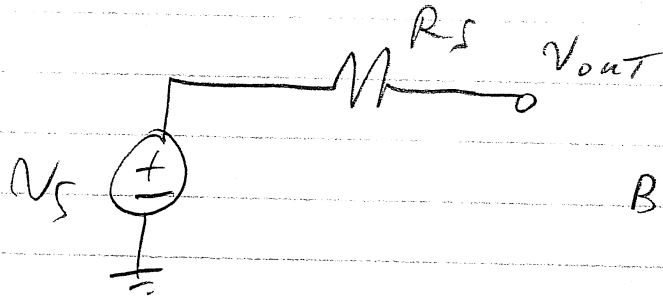

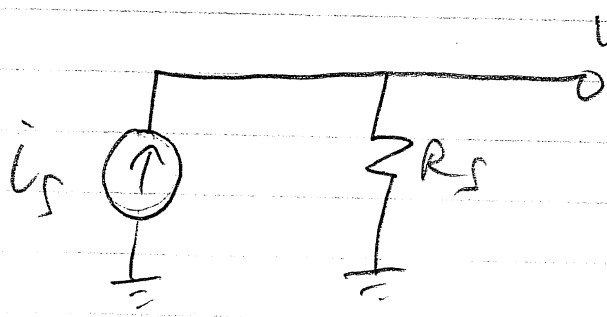AS $R_S \rightarrow 0$ BECOMES MORE IDEAL



AS $R_S \rightarrow \infty$ BECOMES MORE IDEAL.

LARGE OR SMALL COMPARED TO NEXT STAGE INPUT RESISTANCE


THIS KEEPS VALUE OF " V_S " OR " I_S " A REASONABLE VALUE (NOT UNREASONABLY LARGE)

CR9

CAPACITORS & INDUCTORS

CAPACITOR

CAPACITANCE C

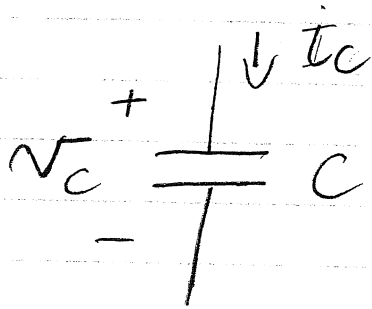

$q = CV_c$
 ↑
 CHARGE


$$\frac{dq}{dt} = C \frac{dV_c}{dt}$$

$$I_c = C \frac{\Delta V_c}{\Delta t} \quad \text{IF CONSTANT CURRENT } I_c$$

CHARGE, q UNITS OF COULOMBS

CURRENT, I_c UNITS OF AMPS \Rightarrow COULOMBS/SECOND

CAPACITOR IMPEDANCE

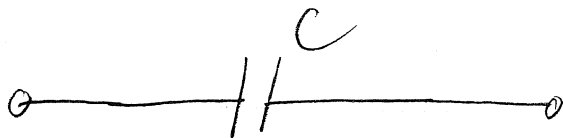

$$Z = \frac{1}{sC}$$

$s \Rightarrow$ LAPLACE TRANSFORM VARIABLE

LET $s = j\omega$ FOR SINGULAR FREQUENCIES

CAPACITOR ENERGY

(POTENTIAL ENERGY)
(STORED IN ELECTRIC FIELD)


$$E_C = \frac{1}{2} C V_C^2$$

(CR10)

INDUCTOR INDUCTANCE L

$\begin{array}{c} + \\ \downarrow \\ \uparrow \\ - \end{array} \left. \begin{array}{l} \downarrow \\ \downarrow \\ \downarrow \\ \downarrow \end{array} \right\} L \quad \mathcal{N}_L = L \frac{di_L}{dt}$

INDUCTOR IMPEDANCE

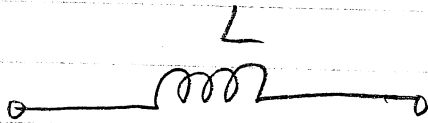

$$Z = sL$$

INDUCTOR ENERGY

(POTENTIAL ENERGY)
(STORED IN MAGNETIC FIELD)

$$E_L = \frac{1}{2} L i_L^2$$