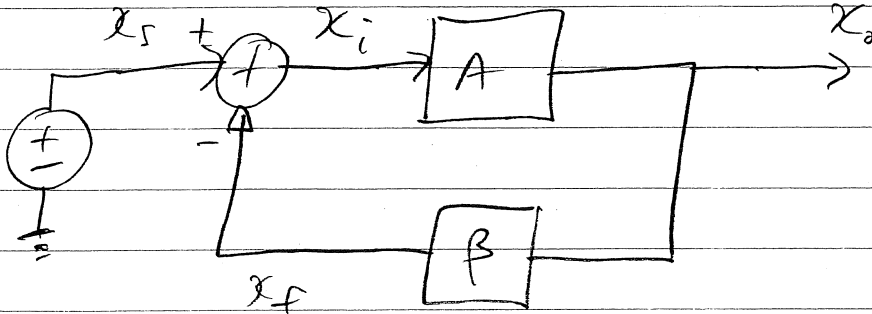


4 BASIC FEEDBACK STRUCTURES




4 BASIC TYPES DEPENDING ON TYPES OF SIGNALS AT X_s, X_f, X_i + X_o

<u>X_s, X_f, X_i</u>	<u>X_o</u>	<u>TYPE</u> (INPUT/OUTPUT)
VOLTAGE	VOLTAGE	SERIES-SHUNT
CURRENT	VOLTAGE	SHUNT-SHUNT
CURRENT	CURRENT	SHUNT-SERIES
VOLTAGE	CURRENT	SERIES-SERIES

SO SERIES-SHUNT MEANS OUTPUT IS A VOLTAGE AND IS SAMPLED WITH A SHUNT NETWORK WHILE INPUT IS ALSO A VOLTAGE AND THE SUBTRACTION IS DONE WITH A SERIES NETWORK.


SERIES-SHUNT EXAMPLES

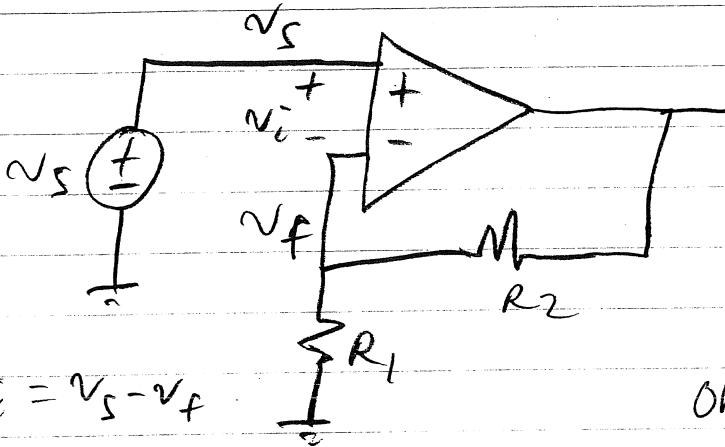

NEG FEEDBACK CHECK

- $v_s \uparrow \Rightarrow v_i \uparrow$
- $v_i \uparrow \Rightarrow v_o \uparrow$
- $v_o \uparrow \Rightarrow v_f \uparrow$
- $v_f \uparrow \Rightarrow v_i \downarrow$ ✓

OPPOSITE OF ORIGINAL v_i CHANGE

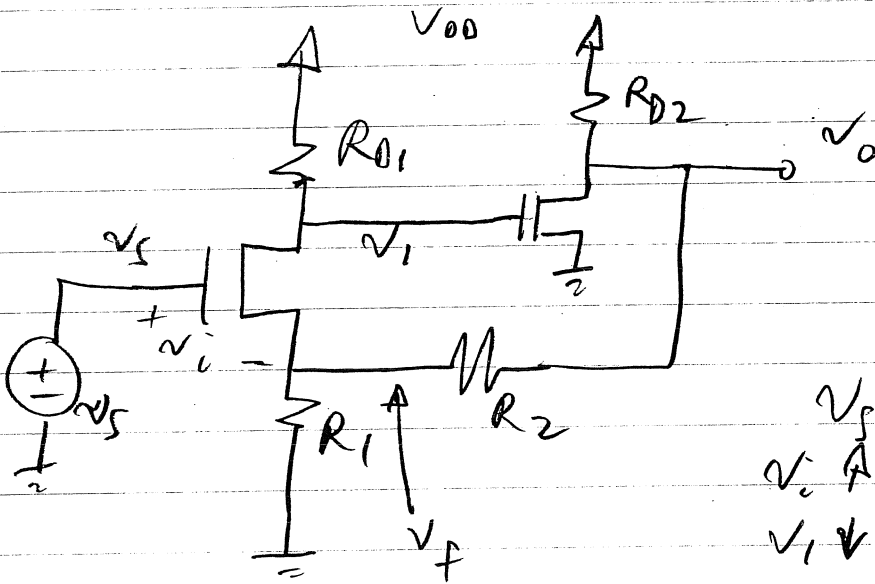


NEG FEEDBACK CHECK

- $v_s \uparrow \Rightarrow v_i \uparrow$
- $v_i \uparrow \Rightarrow v_1 \downarrow$
- $v_1 \downarrow \Rightarrow v_o \uparrow$
- $v_o \uparrow \Rightarrow v_f \uparrow$
- $v_f \uparrow \Rightarrow v_i \downarrow$ ✓

$v_i = v_s - v_f$

FF3

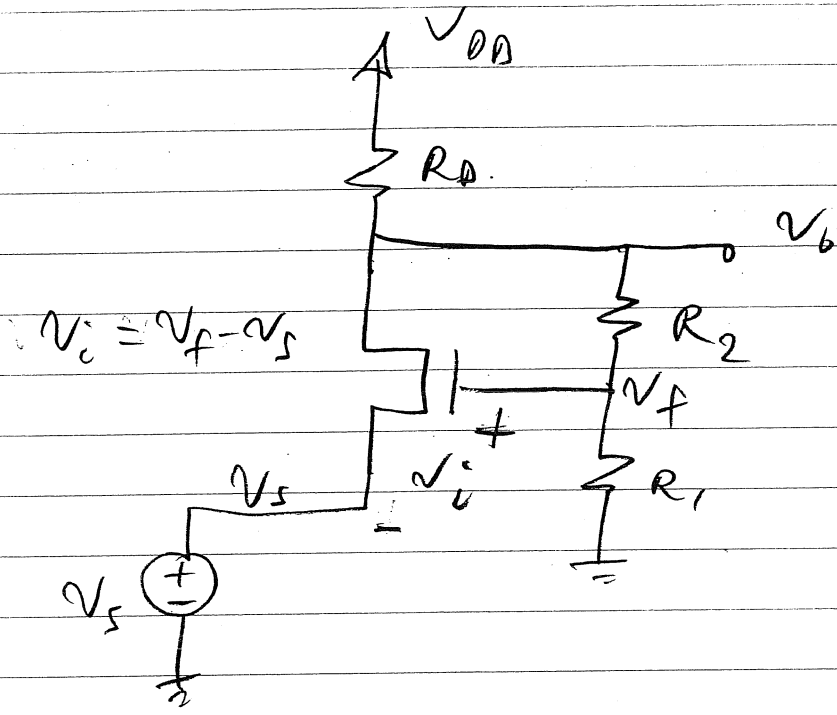


NEG FEEDBACK CHECK

$$v_s \uparrow \Rightarrow v_i \downarrow$$

$$v_i \downarrow \Rightarrow v_o \uparrow$$


$$v_o \uparrow \Rightarrow v_f \uparrow$$
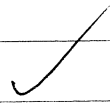
$$v_o \uparrow \Rightarrow \underline{v_i \uparrow}$$




OPPOSITE OF ORIGINAL v_i CHANGE

SHUNT-SHUNT EXAMPLES

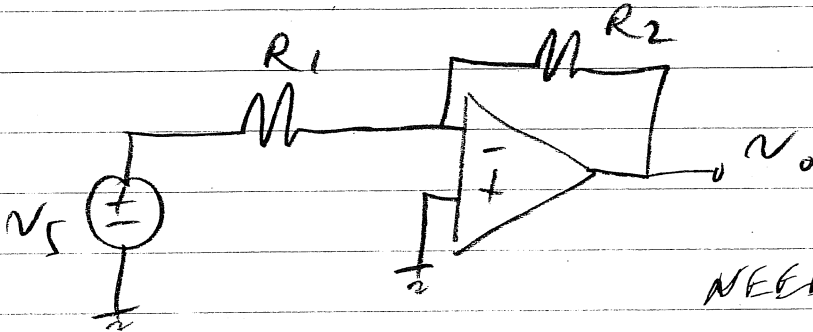

NEEDS MODIFICATION

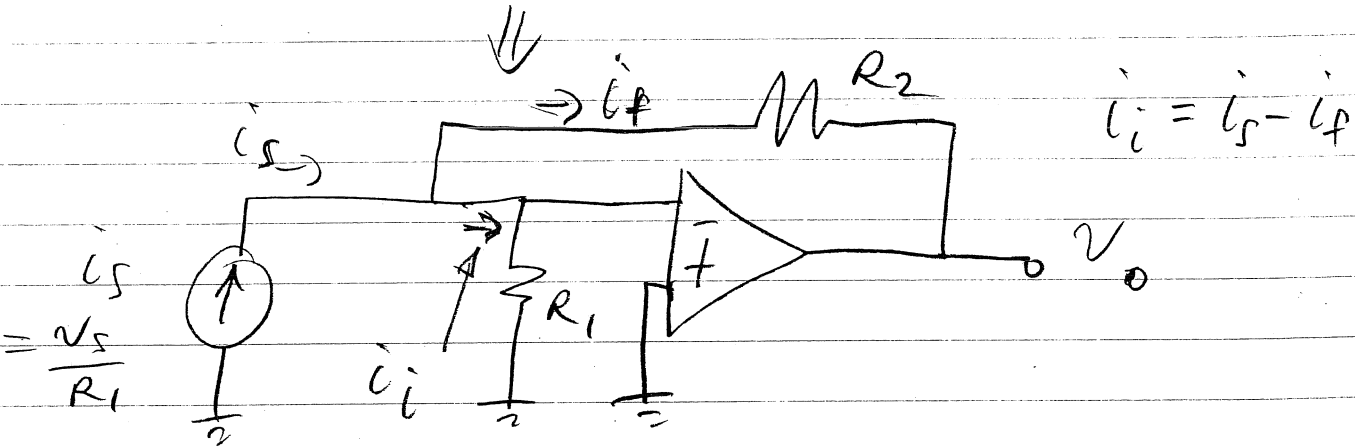


$i_s \uparrow \Rightarrow i_i \uparrow$

$i_i \uparrow \Rightarrow V_o \downarrow$ (SINCE $v_- \uparrow$ DUE TO $i_i \downarrow$ $V_o = A(V_+ - v_-)$)

$V_o \downarrow \Rightarrow i_f \uparrow$

$i_f \uparrow \Rightarrow i_i \downarrow$ ✓

FF5

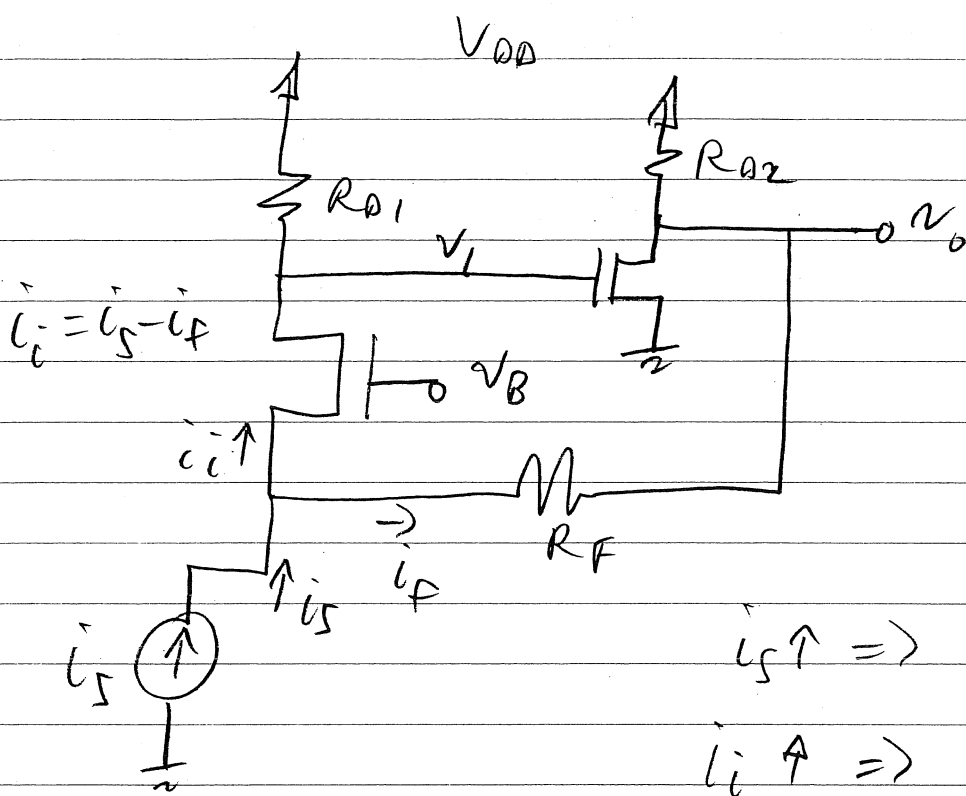

$i_S \uparrow \Rightarrow i_i \uparrow$
 $i_i \uparrow \Rightarrow v_i \uparrow$
 $v_i \uparrow \Rightarrow v_o \downarrow$
 $v_o \downarrow \Rightarrow i_f \uparrow$
 $i_f \uparrow \Rightarrow i_i \downarrow$ ✓

A BIT MORE DIFFICULT TO SEE NEG FEEDBACK HERE. EASIER TO LOOK AROUND LOOP AT v_i WITH $i_S = 0$ (OPEN)


BREAK LOOP AT v_i

INSERT TEST VOLTAGE v_{it} & FIND

RETURN SIGNAL v_{ir}

IF $v_{it} \uparrow$ THEN $v_{ir} \downarrow$

FF-6

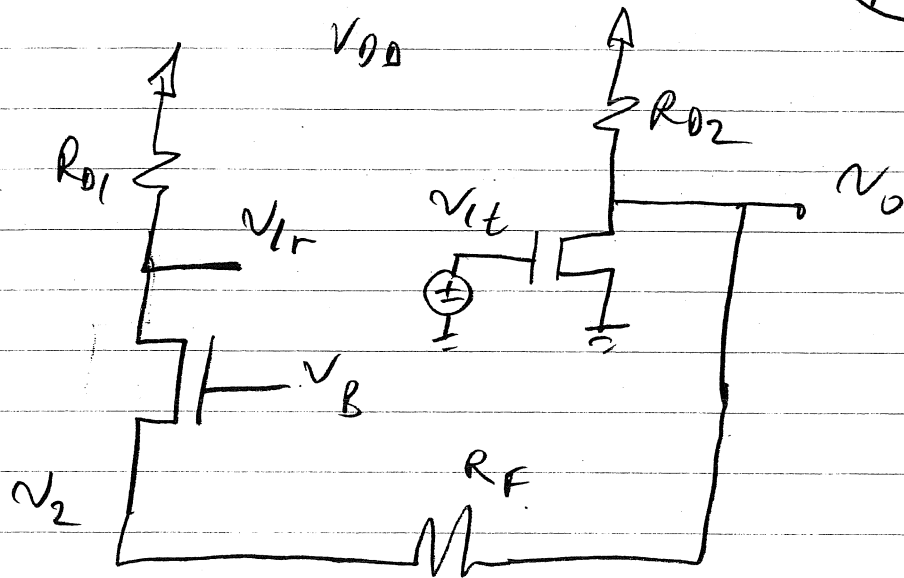

$$V_{IT} \uparrow \Rightarrow V_0 \downarrow$$


$$V_0 \downarrow \Rightarrow V_2 \downarrow$$

$$V_2 \downarrow \Rightarrow V_{IR} \downarrow$$


✓
OPPOSITE OF
 V_{IT}

FF7

SHUNT-SERIES EXAMPLE

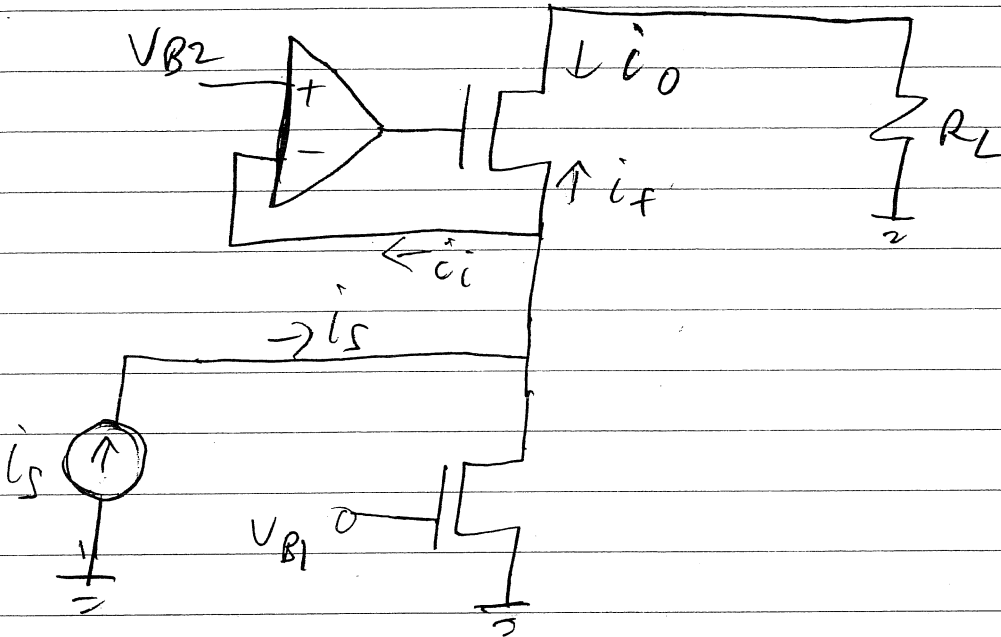

SERIES-SERIES EXAMPLE

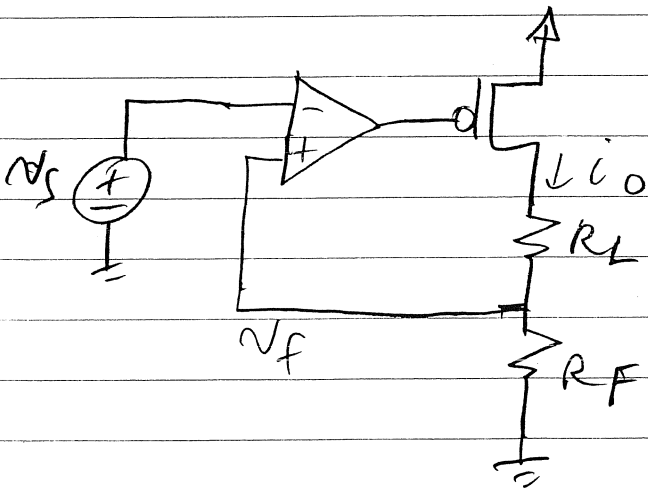

- IN GENERAL, TYPE OF FEEDBACK IS DETERMINED BY WHERE INPUT IS APPLIED AND WHAT IS CONSIDERED TO BE THE OUTPUT.
- THIS MAKES A FEEDBACK APPROACH DIFFICULT TO USE & PRONE TO ERRORS
- WE SHALL DEVIATE FROM TEXTBOOK HERE AND USE THE LOOP GAIN ANALYSIS APPROACH
- IT IS DESCRIBED IN THE 5TH EDITION OF "ANALYSIS AND DESIGN OF ANALOG INTEGRATED CIRCUITS" BY GRAY/HURST/LEWIS/MEYER, 2009
- ANOTHER ISSUE WITH A FEEDBACK APPROACH IS THAT $A\beta$ DEPENDS ON INPUT APPLIED & OUTPUT TAKEN ESPECIALLY WHEN β IS NOT UNIDIRECTIONAL
- THE LOOP GAIN IS UNCHANGED IN THE RETURN-RATIO APPROACH
- LOOP GAIN DETERMINES STABILITY OF A CIRCUIT.