
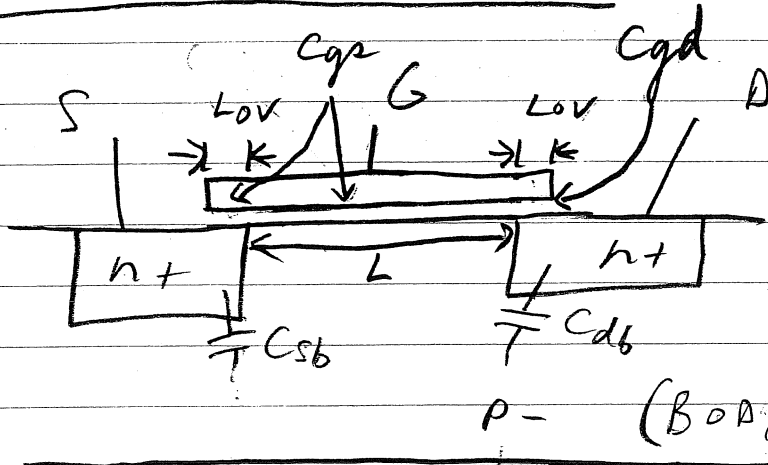


MCI

MOS CAPACITOR MODEL

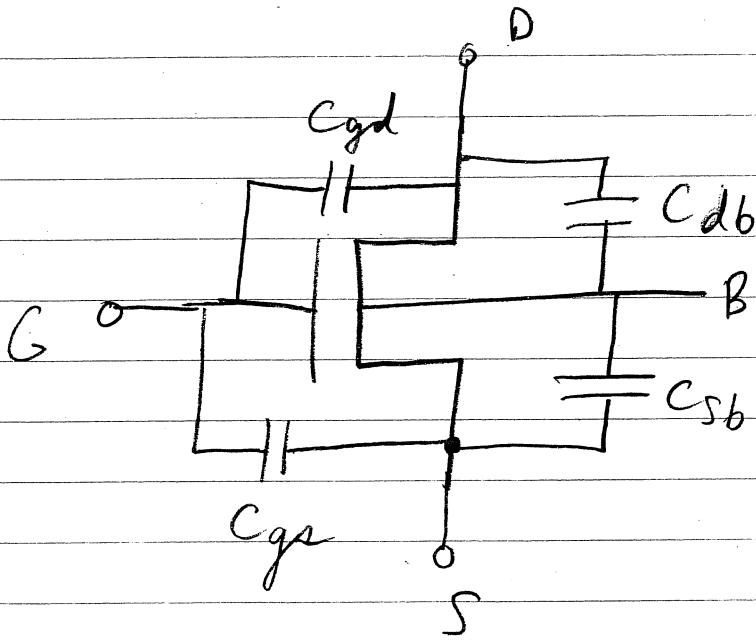

WHEN ACTIVE



NORMALLY
 $V_B = V_S$ so
 C_{sb} UNIMPORTANT

$$C_{gs} = \frac{2}{3} W L C_{ox} + W L_{ov} C_{ox}$$

$$C_{gd} = W L_{ov} C_{ox}$$

$$C_{db} = \frac{C_{db0}}{\sqrt{1 + \frac{V_{DB}}{V_0}}}$$

C_{ox} GATE CAPACITANCE PER UNIT AREA

M2

$\frac{2}{3} W L C_{ox}$ IS GATE TO CHANNEL CAP WHEN DEVICE ACTIVE CHANNEL IS CONNECTED TO SOURCE

$\frac{2}{3}$ FACTOR DUE TO CHANNEL SHAPE

$W L_{ov} C_{ox}$ IS GATE OVERLAP CAPACITANCE
 L_{ov} IS OVERLAP LENGTH


C_{db0} IS DRAIN BODY CAPACITANCE WHEN $V_{DB} = 0$

V_{DB} IS DRAIN BODY VOLTAGE (REVERSE BIAS VOLTAGE)

V_0 IS JUNCTION BUILT-IN VOLTAGE
 $V_0 \approx 0.7 \text{ V}$


(MC3)

MOSFET MODEL WHEN $V_{SB} = 0$

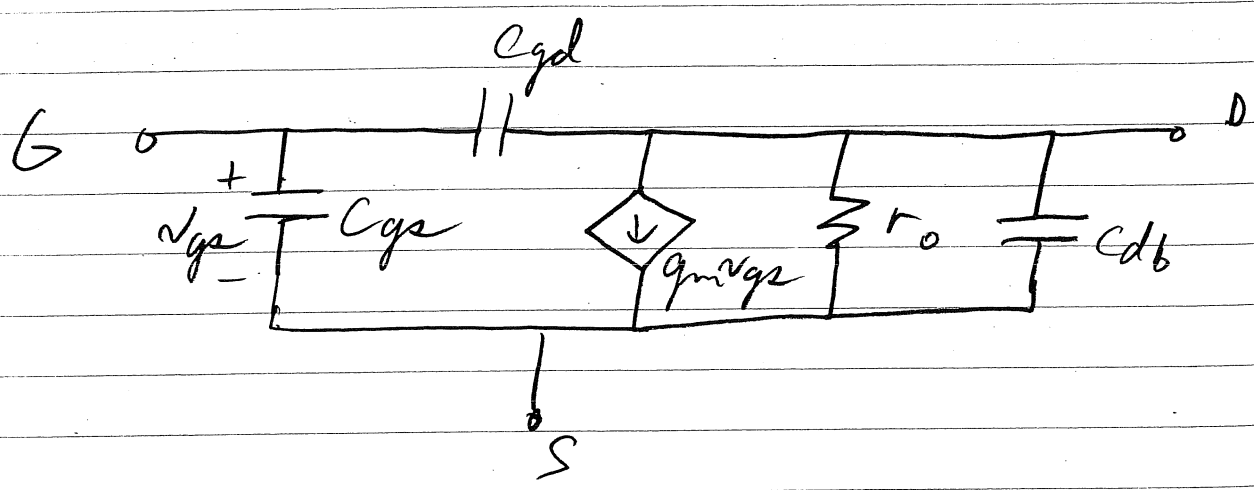

f_T MOSFET UNITY GAIN FREQ

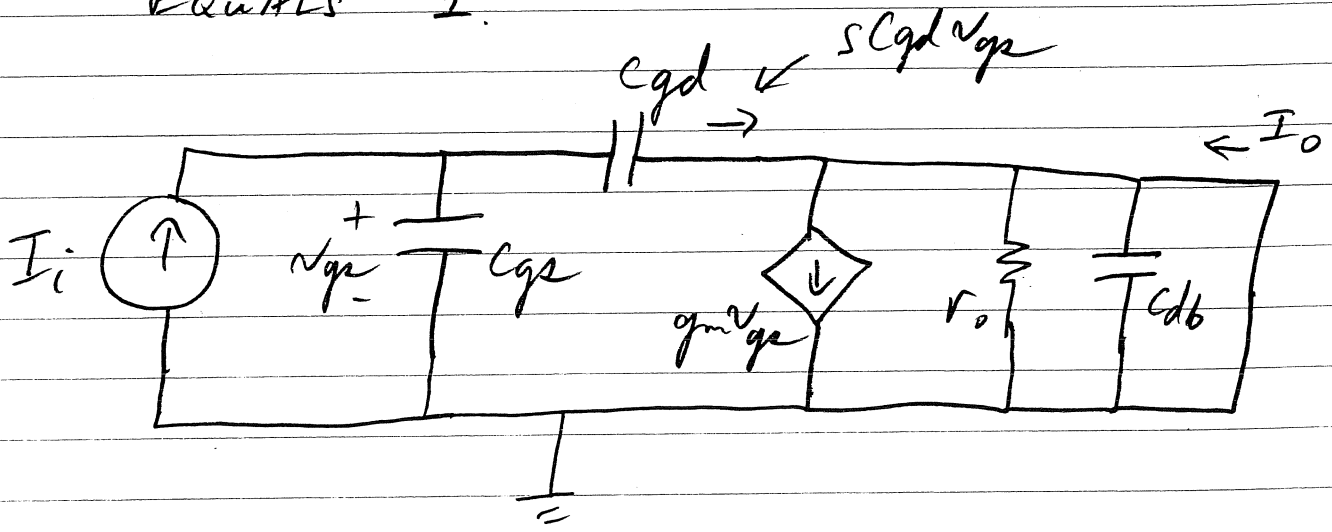FREQ WHERE SHORT-CIRCUIT CURRENT GAIN EQUALS 1.



$$I_0 = g_m V_{gs} - s C_{gd} V_{gs}$$

CAN SHOW TYPICALLY $s C_{gd} V_{gs} \ll g_m V_{gs}$

$$I_0 \approx g_m V_{gs} \quad (1)$$

MCA

$$V_{gs} = I_i / s(C_{gs} + C_{gd}) \quad (2)$$

$$(1) + (2) \Rightarrow \frac{I_o}{I_i} = \frac{g_m}{s(C_{gs} + C_{gd})} \quad (3)$$

LET (3) = 1 TO FIND WHEN $I_o = I_i$
LET $s = j\omega_T$

$$\left| \frac{g_m}{j\omega_T(C_{gs} + C_{gd})} \right| = 1 \Rightarrow \omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

RECALL $g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) V_{ov}$

$$\downarrow C_{gs} = \frac{2}{3} W L C_{ox}$$

ASSUMING $C_{gd} \ll C_{gs}$


$$f_T = \frac{3 \mu_n V_{ov}}{4\pi L^2}$$

INDEPENDENT OF
W

PROPORTIONAL TO $\frac{1}{L^2}$

PROPORTIONAL TO V_{ov}

MC5

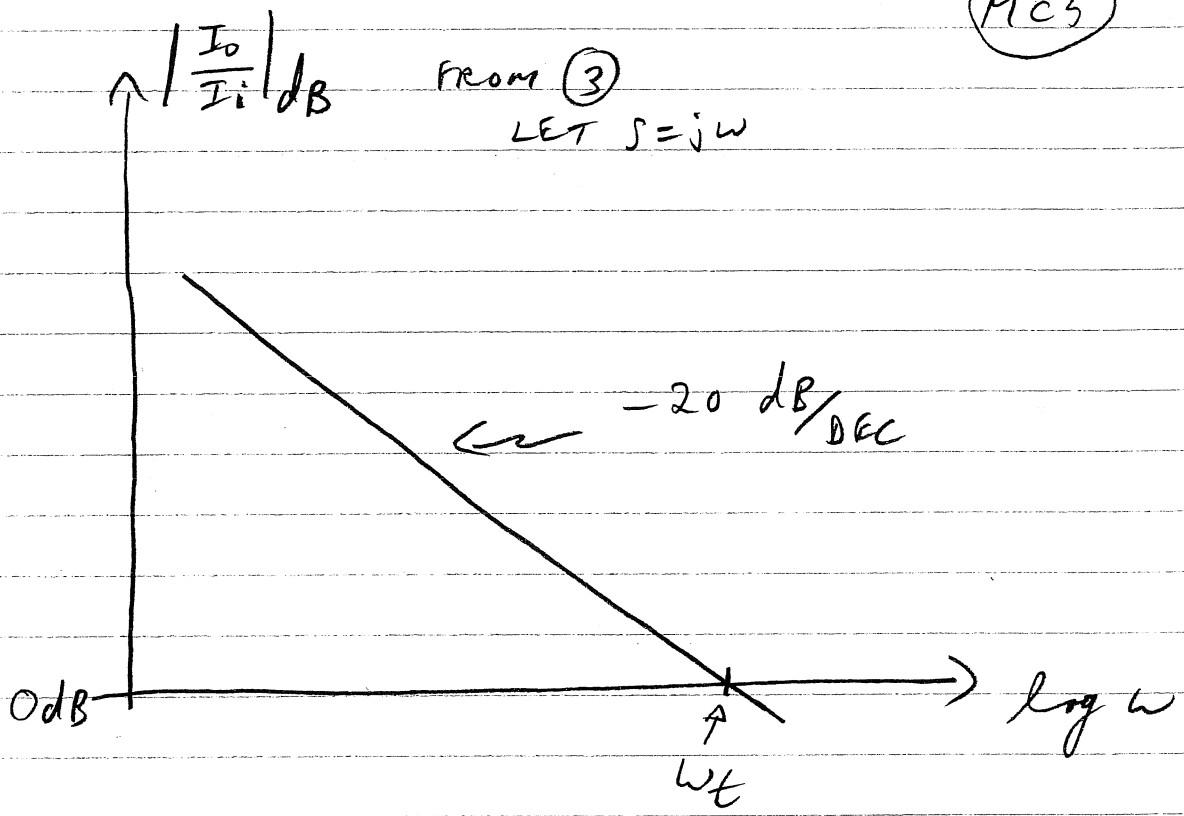

$$\omega_t = 2\pi f_t$$

$$\omega_t = \frac{g_m}{C_{gs} + C_{gd}}$$