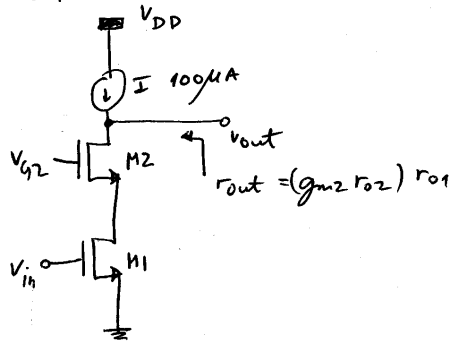


EL2 FP 3

Ex D7.24



Dasja-se

$$g_{m1} = 1 \text{ mA/V}$$

$$R_o = 400 \text{ k}\Omega$$

$$L = ? \text{ } 0.4 \text{ }\mu\text{m}$$

$$W = ? \text{ } 5 \text{ }\mu\text{m}$$

$$V_{G2} = ?$$

maximum possible negative swing  $\Delta V_{out} = ?$

minimum  $V_{out} = ? \text{ } 0.4 \text{ V } (= 2 V_{ov})$

$$V_T = 0.5 \text{ V}$$

$$V_A' = 5 \text{ V}/\mu\text{m}$$

$$\mu_n C_{ox} = 400 \text{ }\mu\text{A/V}^2$$

$$V_{ov} = (V_{GS} - V_T) = 0.2 \text{ V}$$

$$g_{m1} = \frac{2 I_D}{(V_{GS} - V_T)_{M1}} \Leftrightarrow I_D = \frac{g_{m1} (V_{GS} - V_T)}{2} = \frac{1 \times 10^{-3} \times 0.2}{2} = 1 \times 10^{-4} \text{ A}$$

$$r_{o1} = r_{o2} = \frac{V_A' \times L}{I_D}$$

$$g_{m2} = \frac{2 I_D}{(V_{GS} - V_T)_{M2}} = g_{m1} = 1 \text{ mA/V}$$

$$r_o = g_{m2} r_{o2} r_{o1} = g_{m2} \frac{V_A' L}{I_D} \frac{V_A' L}{I_D}$$

$$L = \sqrt{\frac{r_o I_D}{g_{m2} (V_A')^2}} = \sqrt{\frac{400 \times 10^3 \times (100 \times 10^{-6})^2}{1 \times 10^{-3} \times (5 \times 10^6)^2}} = 0.4 \text{ }\mu\text{m}$$


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \Leftrightarrow \frac{W}{L} = \frac{2 I_D}{\mu_n C_{ox} (V_{GS} - V_T)^2} = \frac{2 \times 100 \times 10^{-6}}{400 \times 10^{-6} \times (0.2)^2} = 12.5$$

$$W = 1 \text{ }\mu\text{m}$$

SATURATION REGION

$$V_{GS} > V_T \quad ; \quad V_T = 0.5V$$
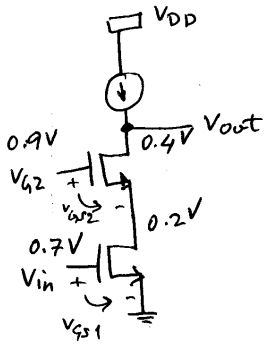
$$V_{GD} \leq V_T \quad \Leftrightarrow \quad V_{DG} \geq -V_T$$




$$(V_{GS} - V_T) = 0.2V \quad \Leftrightarrow \quad V_G - V_S - V_T = 0.2V$$

$$V_{G2} = 0.2V + V_S + V_T$$

$$V_{G2} = 0.2 + 0.2 + 0.5$$

D 7.27

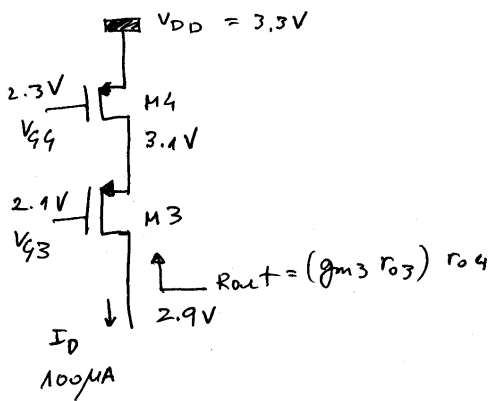

$$\mu C_{ox} = 60 \mu A/V^2$$

$$|V_T| = 0.8V$$

$$|V_A| = 5V$$

$$V_{ov} = 0.2V$$

$$\frac{W}{L} = ?$$

$$V_{G3} = 2.1V$$

$$V_{G4} = 2.3V$$

$$R_{out} =$$

$$\text{maximum } V_{out} = 2.9V$$

$$(\quad = V_{DD} - 2V_{ov})$$

$$V_{SG} - V_T = V_{ov}$$

$$V_S - V_G - V_T = V_{ov}$$

$$V_S = V_{ov} + V_T + V_G \quad \Leftrightarrow \quad V_{DD} = V_{ov} + V_T + V_{G4}$$

$$\Leftrightarrow \quad V_{G4} = V_{DD} - V_T - V_{ov} = 2.3V$$

$$V_{G3} = V_{S3} - V_T - V_{ov} = 2.1V$$


$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} V_{ov}^2$$

$$\frac{W}{L} = \frac{2 I_D}{(\mu C_{ox}) V_{ov}^2} = \frac{2 \times 100 \times 10^{-6}}{60 \times 10^{-6} (0.2)^2} = 83.3$$

$$R_o = g_{m3} r_{o3} r_{o4} = \frac{2 I_D}{(V_{GS} - V_T)} \frac{V_A}{I_D} \frac{V_A}{I_D} = \frac{2 \times 5^2}{0.2 \times 100 \times 10^{-6}} = 2.5 \text{ M}\Omega$$

EL2 FP3

D7.46

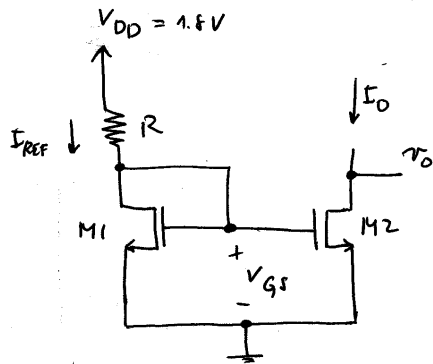

$$V_{DD} = 1.8V$$

$$I_{REF} = 100\mu A$$

$$I_O = 100\mu A$$

$$R = ?$$

$$\mu_1 = \mu_2$$

$$L = 0.5\mu m$$

$$W = 8\mu m$$

$$V_T = 0.5V \quad V_A' = 10V/\mu m$$

$$K_n = \mu C_{ox} = 400\mu A/V^2$$

minimum possible for  $V_O = ?$

$$R_O = ?$$

$$\Delta V_O = +0.5V$$

$$\Delta I_O = ?$$

$$I_1 = I_2 = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

$$(V_{GS} - V_T) = \sqrt{\frac{2I}{\mu C_{ox}(W/L)}} = \sqrt{\frac{2 \times 100 \times 10^{-6}}{400 \times 10^{-6} \times 8}} = 0.25V$$

$$V_{GS} = V_T + 0.25 = 0.75$$

$$R = \frac{V_{DD} - V_{GS}}{I} = \frac{1.8 - 0.75}{100 \times 10^{-6}} = 10.5K\Omega$$

$$R_O \approx r_{o2} = \frac{V_A' \times L}{I} = \frac{10 \times 0.5}{100 \times 10^{-6}} = 50K\Omega$$

EL2 FP3

$$\frac{1}{r_o} = \frac{\partial I_D}{\partial V_{DS}} \rightarrow \Delta I_D = \frac{1}{r_o} \Delta V$$

$$\Delta I_D = \frac{0.5V}{50 \times 10^3} = 10 \mu A$$

$$\frac{\Delta I_D}{I_D} \times 100\% = 10\%$$

minimum possible for  $V_O$ :

$$V_{GS} - V_T = 0.25$$

$$V_{GS} = V_T + 0.25$$

$$V_G - V_S = V_T + 0.25$$

$$V_G = V_S + V_T + 0.25 = 0.75V$$

$$V_{GD} \leq V_T$$

$$V_{DG} \geq -V_T$$

$$V_D \geq V_G - V_T$$

$$V_{D \min} = V_G - V_T = 0.75 - 0.5 = 0.25V (= V_{OV})$$