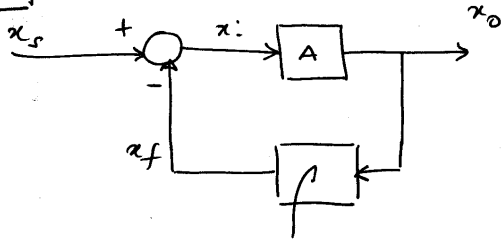


EL2 F7

10.1



$$\left. \begin{aligned} x_i &= x_s - x_f \\ x_f &= \beta x_o \\ x_o &= A x_i \end{aligned} \right\} \frac{x_o}{A} = x_o - \beta x_o$$

$$(1 + A\beta) x_o = A x_i$$

$$A_f \equiv \frac{x_o}{x_i} = \frac{A}{1 + A\beta} \quad \xrightarrow{A \gg 1} \quad A_f \approx \frac{1}{\beta}$$

Conditions:

$$A = 10^4$$

$$A_f + A_f A \beta = A$$

$$A_f = 100$$

$$\beta = \frac{A - A_f}{A_f \times A} = \frac{10000 - 100}{10^4 \times 10^2} = 0.0099$$

$$\beta = ?$$

$$A_f = \frac{A}{1 + A\beta} = \frac{10^3}{1 + 10^2 \times 0.0099} = 91.743$$

$$\frac{\Delta A_f}{A_f} = \frac{100 - 91.743}{100} \approx 8.26\%$$

EL2 FP7

10.10

$$A_f = \frac{A}{1+A\beta}$$

$$dA_f = \frac{1}{1+A\beta} dA - \frac{A\beta}{(1+A\beta)^2} dA$$

$$dA_f = \frac{1+A\beta - A\beta}{(1+A\beta)^2} dA$$

$$\frac{dA_f}{A_f} = \frac{1}{1+A\beta} \frac{dA}{A}$$

$$A_f = 25 \pm 1\%$$

$$A = A \pm 10\%$$

$$A = ?$$

$$\beta = ?$$

$$0.01 = \frac{1}{1+A\beta} \times 0.1$$



$$0.01 + 0.01 A\beta = 0.1$$

$$A\beta = \frac{0.1 - 0.01}{0.01} = 9$$



$$A = A_f (1+A\beta) = 25 \times 10 = 250$$

$$A\beta = 9 \Rightarrow \beta = \frac{9}{250} = 0.036$$


10.16

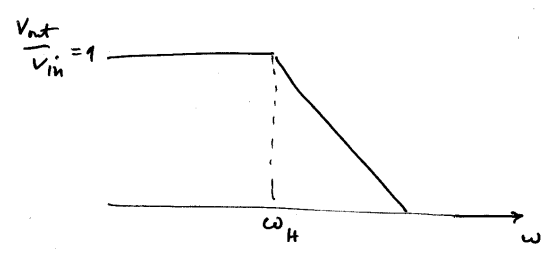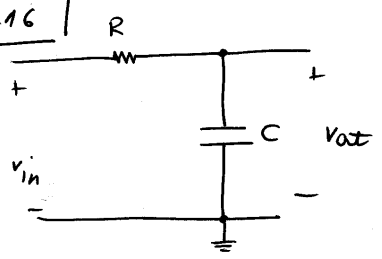
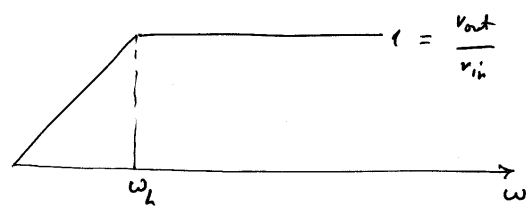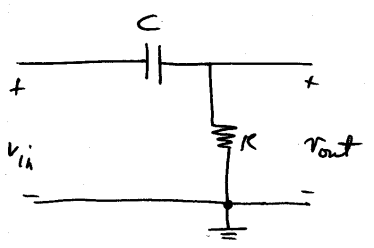
$$\frac{v_{out}}{v_{in}} = \frac{1/j\omega C}{R + \frac{1}{j\omega C}} = \frac{1/sC}{R + \frac{1}{sC}} = \frac{1}{1 + sRC} = \frac{1}{1 + s/\omega_H} \quad \text{where } \omega_H = \frac{1}{RC}$$


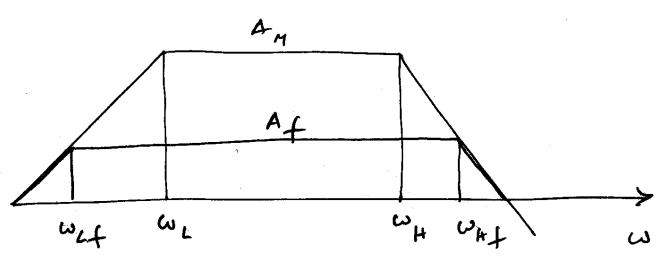
$$\frac{v_{out}}{v_{in}} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC} = \frac{1}{1 + \frac{1}{sRC}} = \frac{1}{1 + \frac{\omega_L}{s}} \quad \text{where } \omega_L = \frac{1}{RC}$$



$$A_f = \frac{A}{1 + A\beta}$$

$$A(s) = \frac{A_M}{1 + s/\omega_H} \rightarrow A_f = \frac{\frac{A_M}{1 + s/\omega_H}}{1 + \beta \frac{A_M}{1 + s/\omega_H}}$$

$$A_f = \frac{\frac{A_M}{1 + s/\omega_H}}{\frac{1 + s/\omega_H + \beta A_M}{1 + s/\omega_H}} = \frac{A_M}{1 + s/\omega_H + \beta A_M} = \frac{A_M}{(1 + \beta A_M) \left[1 + \frac{s}{\omega_H (1 + \beta A_M)} \right]}$$

EL2 FP7

$$A_f = \frac{\frac{A_M}{1 + \beta A_M}}{1 + s / [\omega_H (1 + \beta A_M)]}$$

$$\omega_{Hf} = \omega_H (1 + \beta A_M)$$

$$A(s) = \frac{A_M}{1 + \omega_L/s} \rightarrow A_f = \frac{\frac{A_M}{1 + \omega_L/s}}{1 + \beta \frac{A_M}{1 + \omega_L/s}}$$

$$A_f = \frac{\frac{A_M}{1 + \omega_L/s}}{\frac{1 + \omega_L/s + \beta A_M}{1 + \omega_L/s}} = \frac{A_M}{1 + \omega_L/s + \beta A_M} = \frac{A_M}{(1 + \beta A_M) \left[1 + \frac{\omega_L}{s(1 + \beta A_M)} \right]}$$




$$\omega_{Lf} = \frac{\omega_L}{1 + \beta A_M}$$

$$A_f = \frac{A_M}{1 + \beta A_M} \rightarrow 10 = \frac{1000}{(1 + \beta A_M)} \Leftrightarrow (1 + \beta A_M) = 100$$

$$\omega_{Hf} = \omega_H (1 + \beta A_M) = 10 \text{ kHz} \times 100 = 1 \text{ MHz}$$

$$\omega_{Lf} = \frac{\omega_L}{1 + \beta A_M} = \frac{100 \text{ Hz}}{100} = 1 \text{ Hz}$$

10.22

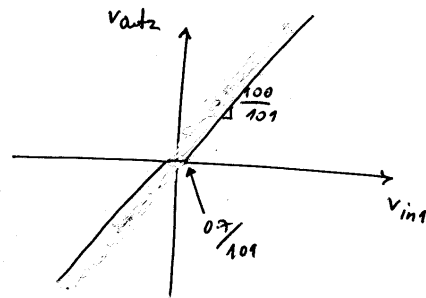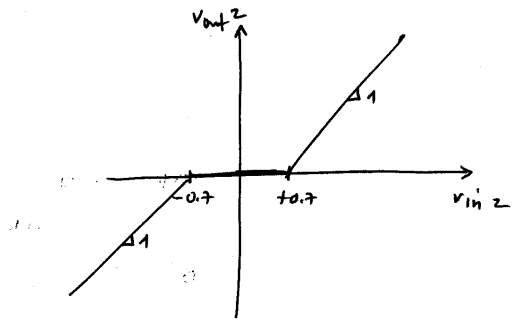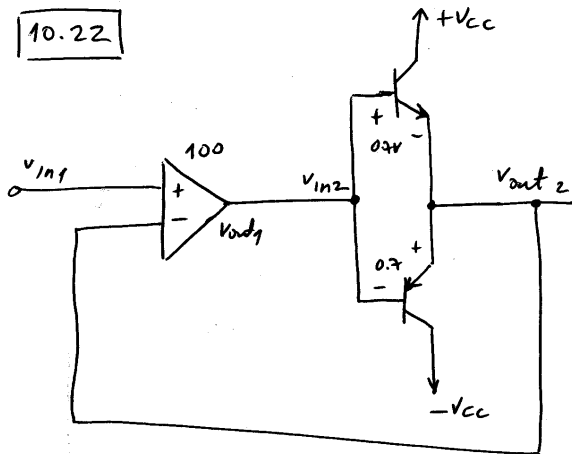

$$v_{out1} = 100 (v_{in1} - v_{out2})$$

$$v_{out1} = v_{out2} \pm 0.7 \text{ V}$$

$$v_{out2} \pm 0.7 = 100 v_{in1} - 100 v_{out2}$$

$$100 v_{in1} = (1 + 100) v_{out2} \pm 0.7$$

$$v_{out2} = \frac{100}{101} v_{in1} \mp \frac{0.7}{101}$$