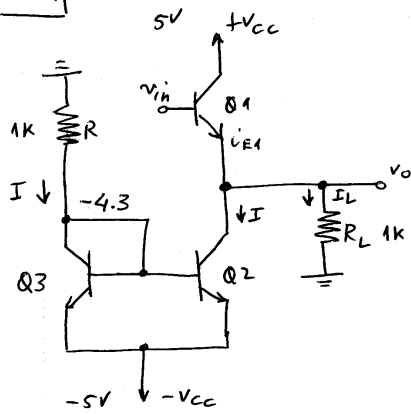


11.1



$V_{BE} = 0.7V$
 $V_{CEsat} = 0.3V$

$V_{OHIGH} = V_{CE} - V_{CESAT} = +5 - 0.3 = 4.7V$

$V_{INHIGH} = V_{OHIGH} + 0.7 = +5.4V$

V_{OLOW} :

2 HIPÓTESIS

a) Q2 SATURADO


$V_{OLOW} = -V_{CC} + V_{CESAT} = -5 + 0.3 = -4.7V$

b) Q1 OFF

$+I_L = -I \Rightarrow V_{OLOW} = -R_L I = -1 \times 10^3 \times \frac{4.3}{1 \times 10^3} = -4.3V$

$\therefore V_{OLOW} = -4.3V$

$V_{INLOW} = -4.3 + 0.7 = -3.6V$

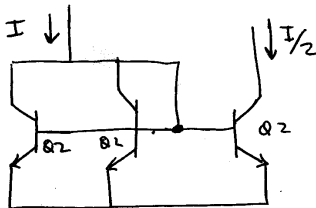

$V_{OLOW} = -R_L \frac{I}{2} = -2.15V$

$V_{INLOW} = -2.15 + 0.7 = -1.45V$


$$\eta = \frac{P_L}{P_S}$$

$$P_{L_{MAX}} = \frac{1}{R} \frac{V_{CC}^2}{2} \quad (\text{See page 4})$$

$$P_S = \frac{1}{T} \int_0^T (2V_{CC}) \times I \, dt = 2V_{CC} I$$

$$\eta_{MAX} = \frac{P_L}{P_S} = \frac{V_{CC}^2}{4V_{CC}RI} \Rightarrow \eta_{MAX} = \frac{V_{CC}}{4R} I_{MAX} = \frac{1}{4} = 25\%$$

11.4

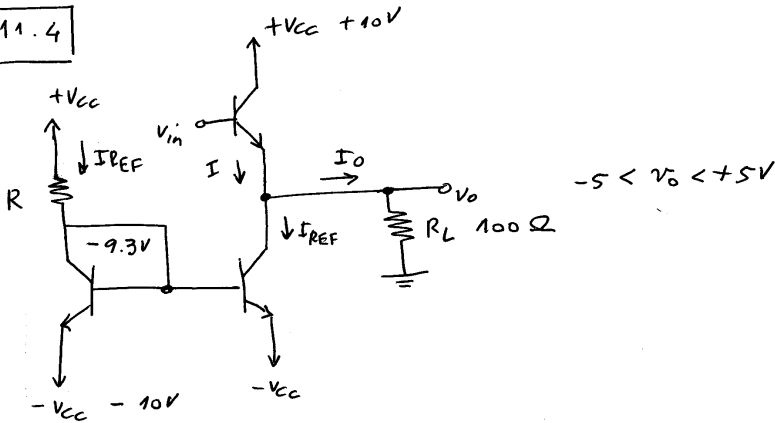


$$\frac{I_{REF} + I_O}{I_{REF} - I_O} = 10 ; \quad \frac{I + \frac{5}{100}}{I - \frac{5}{100}} = 10 ; \quad \frac{I + 0.05}{I - 0.05} = 10$$

$$I + 0.05 = 10 I_{REF} - 0.5$$

$$0.55 = 9 I_{REF} \Leftrightarrow I_{REF} = \frac{0.55}{9} = 61 \text{ mA}$$
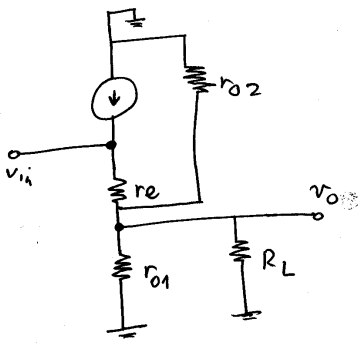
$$R = \frac{V_{CC} - V_C}{I_{REF}} = \frac{10 - (-9.3)}{61 \times 10^{-3}} = 316 \Omega$$



$$v_o = \frac{R_L \parallel r_{o1} \parallel r_{o2}}{r_e + (R_L \parallel r_{o1} \parallel r_{o2})} v_{in}$$

$$v_o \approx \frac{R_L}{r_e + R_L} v_{in}$$

$$A_V \equiv \frac{v_o}{v_{in}} = \frac{R_L}{r_e + R_L}$$

$$(a) \quad v_o = +5V$$

$$r_o = \frac{V_T}{I} = \frac{V_T}{I_{REF} + \frac{V_o}{R_L}} = \frac{25 \times 10^{-3}}{61 \times 10^{-3} + 50 \times 10^{-3}} = 0.225 \, \Omega$$

$$\frac{v_o}{v_{in}} = \frac{100}{0.225 + 100} = 0.9977$$

$$(b) \quad r_o = \frac{V_T}{I_{REF} - \frac{V_o}{R_L}} = \frac{25}{61 - 50} = 2.27 \, \Omega$$

$$\frac{v_o}{v_{in}} = \frac{100}{2.27 + 100} = 0.9778$$

$$\frac{\Delta A_v}{A_v} = \frac{0.9977 - 0.9778}{0.9778} = 0.02 \quad (2\%)$$

11.11

$$v(t) = V \sin(\omega t)$$

$$P_i = v(t) \cdot i(t)$$

$$i(t) = \frac{v(t)}{R}$$

$$\bar{P} = \frac{1}{T} \int_0^T P_i(t) dt = \frac{1}{R} \frac{1}{T} \int_0^T V^2 \sin^2\left(\frac{2\pi}{T} t\right) dt$$

mudança de variável

$$\frac{2\pi}{T} t = x$$

$$dt = \frac{T}{2\pi} dx$$

$$\text{Quando } t = T \Rightarrow x = 2\pi$$

$$\bar{P} = \frac{1}{R} \frac{1}{2\pi} \int_0^{2\pi} V^2 \sin^2 x dx$$

$$\sin^2 x = \frac{1}{2} - \frac{1}{2} \cos 2x$$

$$\bar{P} = \frac{1}{R} \frac{V^2}{2}$$

$$\left(V_{\text{eff}} = \frac{V}{\sqrt{2}} \right)$$

$$\bar{P}_{\text{MAX}} = \frac{1}{R} \frac{V_{cc}^2}{2} = \frac{1 \cdot 10^2}{100 \cdot 2} = 0.5 \text{ W}$$

$$\bar{P}_{St} = \bar{P}_s = V_{cc} \frac{1}{T} \int_0^{T/2} I \sin\left(\frac{2\pi}{T} t\right) dt$$

$$= V_{cc} \frac{V_0}{R} \frac{1}{2\pi} \int_0^{\pi} \sin x dx = \frac{V_{cc}}{\pi} \frac{V_0}{R}$$

$$\bar{P}_{St \text{ MAX}} = \frac{V_{cc}}{\pi} \frac{V_{cc}}{R} = \frac{1}{3.14} \frac{10^2}{100} = 0.318 \text{ W}$$

$$\eta = \frac{P_L}{P_s} = \frac{P_L}{2 \times P_{St}} = \frac{0.5}{2 \times 0.318} = 78.6\%$$

EL 2 FPII

$$\text{PARA } V_0 = \frac{V_{cc}}{2} = 5$$

$$P_L = \frac{1}{R} \frac{V_0^2}{2} = \frac{1}{100} \frac{5^2}{2} = 0.125 \text{ W}$$

$$P_{St} = \frac{V_{cc}}{\pi} \frac{V_0/2}{R} = \frac{10}{3.14} \frac{5}{100} = 0.159 \text{ W}$$

$$\eta = \frac{P_L}{2 P_{St}} = \frac{0.125}{2 \times 0.159} = 39\%$$

11.13

$$\bar{P} = \frac{1}{R} \frac{V_0^2}{2} \quad 100 = \frac{1}{16} \frac{V_0^2}{2} \quad V_0 = 56.5 \text{ V}$$

$$V_{cc} = V_0 + 4 = 56.5 + 4 = 60.5 \text{ V} \rightarrow 61 \text{ V}$$

$$I_{\text{peak}} = \frac{V_0}{R} = \frac{56.5}{16} = 3.53 \text{ A}$$

$$\bar{P}_{St} = \bar{P}_{S-} = \frac{V_{cc}}{\pi} I_{\text{peak}} = \frac{61}{3.14} \times 3.53 = 68 \text{ W}$$

$$\bar{P}_S = \bar{P}_{St} + \bar{P}_{S-} = 136 \text{ W}$$

$$\eta = \frac{100}{136} = 73.5\%$$

Transistor power dissipation

$$P_D = P_S - P_L$$
$$= \frac{2}{\pi} \frac{V_o}{R_L} V_{CC} - \frac{1}{R_L} \frac{V_o^2}{2}$$

P_D max:

$$\frac{\partial P_D}{\partial V_o} = 0 \quad 0 = \frac{2}{\pi} \frac{V_{CC}}{R_L} - \frac{V_o}{R_L} \quad \Rightarrow V_o = \frac{2 V_{CC}}{\pi}$$

$$P_{D \text{ max}} = \frac{2 V_{CC}^2}{\pi^2 R_L}$$

$$P_{DN} = P_{DP} = \frac{V_{CC}^2}{\pi^2 R_L} = \frac{61^2}{3.14^2 \times 16} = 23 \text{ W}$$