
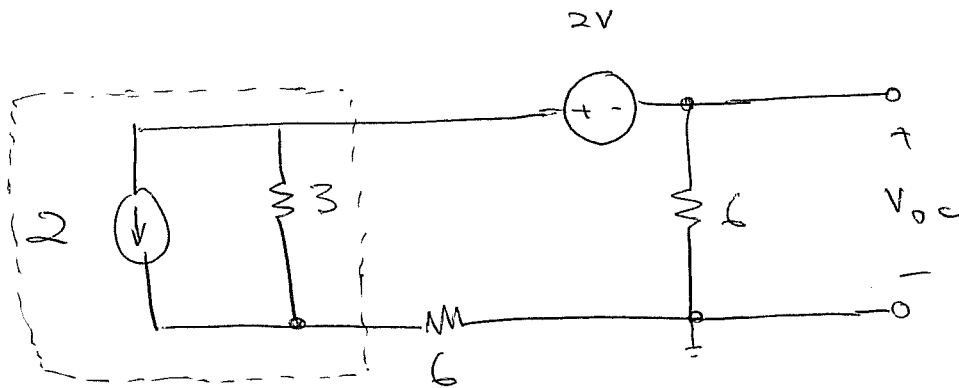



Q1a)

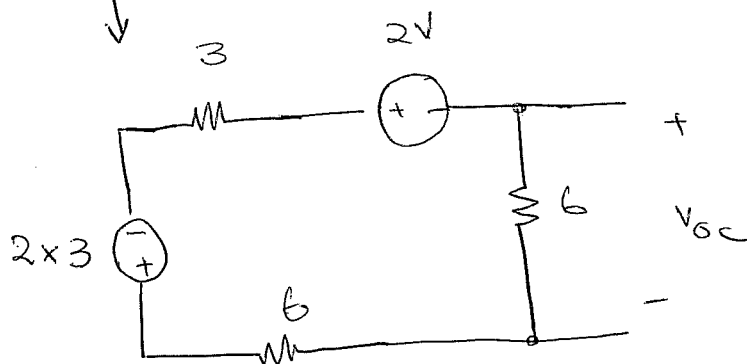

Source transformation



which simplifies to

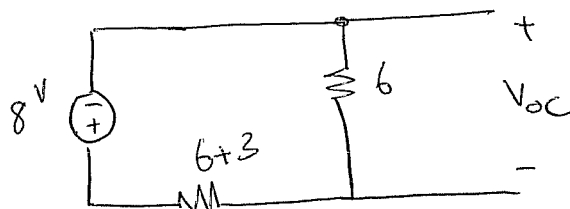


$$V_{oc} = \frac{6}{6+9} \times -8 = -3.2V$$

$$R_{th} = 6 \parallel 9 = 3.6 \Omega = R_{no}$$

$$I_{short} = \frac{V_{oc}}{R_{th}} = -0.889 A$$


Q 1 b)

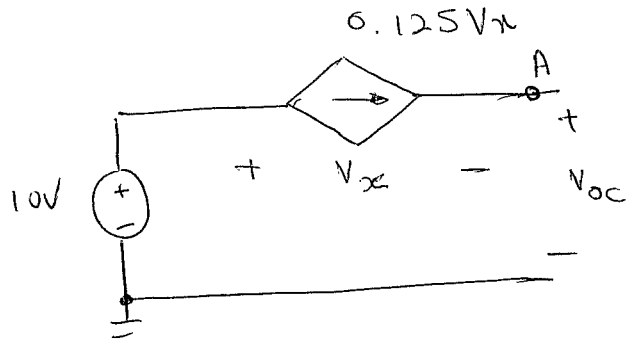

Since no current can flow through the open circuit, $0.125 V_x = 0 \Rightarrow V_x = 0$

KVL $-10 + V_x + V_{oc} = 0 \Rightarrow \frac{V_{oc} = 10V}{0.125 V_x}$

To find I_{sc} :

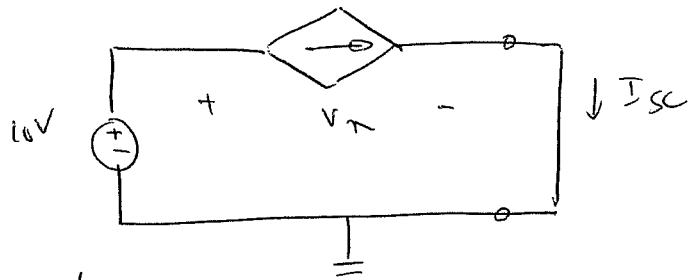


KVL: $-10 + V_x = 0 \Rightarrow V_x = 10V$

$I_{sc} = 0.125 V_x = 1.25 A$


$R_{th} = R_{No} = \frac{V_{oc}}{I_{sc}} = 8 \Omega$

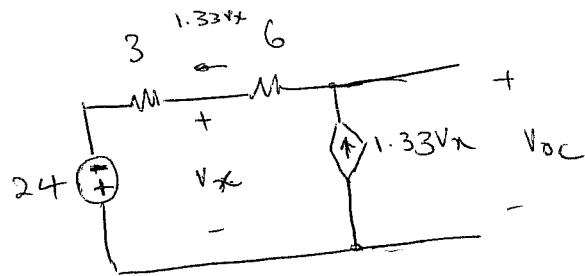Q 1 c)

KVL $-24 - V_x + 3.99 V_x = 0$
 $\Rightarrow V_x = 8.02 V$



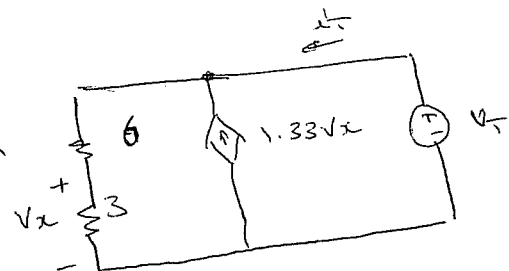KVL $-24 - V_{oc} + 9 \times 1.33 \times 8.02 = 0$
 $\Rightarrow V_{oc} = 72 V$



$V_x = \frac{1}{3} V_{I_1}$
KCL: $I_{I_1} + 1.33 V_x = \frac{V_{I_1}}{9 \Omega}$
 $\frac{V_{I_1}}{1} = -3.01 \Omega = R_{th}$

Q. 5.4

with V_{DS} small compared to V_{ov} , eq. 5.13a applies:

$$r_{DS} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) V_{ov}}$$

- (a) V_{ov} is doubled $\Rightarrow r_{DS}$ is halved. Factor = 0.5
(b) W is doubled $\Rightarrow r_{DS}$ is halved. Factor = 0.5
(c) W and L are doubled $\Rightarrow r_{DS}$ is unchanged. Factor = 1.
(d) If oxide thickness t_{ox} is halved and $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$, C_{ox} is doubled. If W and L are also halved, r_{DS} is halved. Factor = 0.5.
-

Q. 5.9

$$V_{DSsat} = V_{ov} = V_{GS} - V_t = 2.5 - 1 = 1.5 \text{ V}$$

in saturation:

$$\begin{aligned} i_D &= \frac{1}{2} k'_n \left(\frac{W}{L}\right) V_{ov}^2 = \frac{1}{2} k_n V_{ov}^2 \\ &= \frac{1}{2} \times 1 \frac{\text{mA}}{\text{V}^2} \times (1.5 \text{ V})^2 = 1.125 \text{ mA} \end{aligned}$$

Q. 5.12

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_{th})^2, \text{ where } k_n' = \mu_n C_{ox}$$

for equal drain currents:

$$\mu_n C_{ox} \frac{W_n}{L} = \mu_p C_{ox} \frac{W_p}{L} \Rightarrow \mu_n W_n = \mu_p W_p$$

$$\Rightarrow \frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} = \frac{1}{0.4} = 2.5$$

Q. 5.34

$$V_A = V_A' L = 20 \times 1.6 = 32V$$

$$\lambda = \frac{1}{V_A} = 0.031 V^{-1}$$

$$V_{DS} = 2V > (V_{GS} - V_t) = 0.5 \Rightarrow \text{Saturation}$$

$$i_D = \frac{1}{2} k_n' \frac{W}{L} V_{ov}^2 = \frac{1}{2} \times 130 \times \frac{16}{1.6} \times 0.5^2 = 162.5 \mu A$$

$$r_o = \frac{V_A}{i_D} = \frac{32}{162.5 \mu A} = 197 k\Omega = \frac{\Delta V_{DS}}{\Delta i_D} = \frac{1}{\Delta i_D} \Rightarrow \Delta i_D = 5.1 \mu A$$

Q. 5.39

$$V_{GS} = -3V,$$

$$V_{SG} = 3V,$$

$$V_{DS} = -4V,$$

$$V_{SD} = 4V,$$

$$V_t = -1V,$$

$$i_D = \frac{1}{2} k_p' \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

$$\Rightarrow 3 = \frac{1}{2} k_p' \frac{W}{L} (-3 - (-1))^2 (1 - 0.02 \times (-4))$$

$$= 2.16 k_p' \frac{W}{L}$$

$$\Rightarrow k_p' \frac{W}{L} = 1.39 \frac{mA}{V^2}$$

2. 5. 76

$$\lambda = 0 \Rightarrow r_o = \infty$$

$$V_i = g_m V_{GS} \left(\frac{1}{g_m} + R_S \right)$$


$$V_d = -g_m V_{GS} R_D$$

$$V_S = g_m V_{GS} R_S$$


$$\frac{V_S}{V_i} = \frac{R_S}{\frac{1}{g_m} + R_S} \quad \left(\text{Note: Voltage divider} \right)$$

$$= \frac{g_m R_S}{1 + g_m R_S}$$
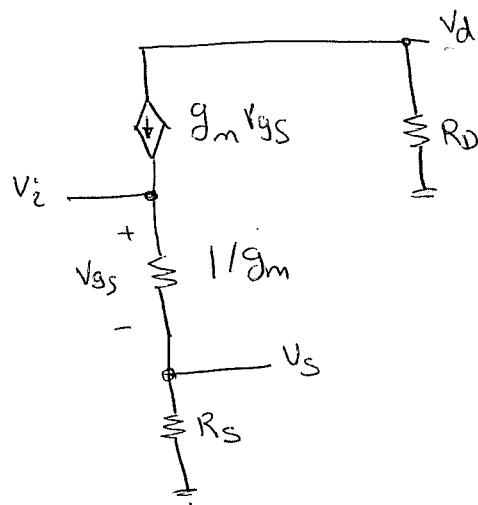
$$\frac{V_d}{V_i} = \frac{-R_D}{\frac{1}{g_m} + R_S} = \frac{-g_m R_D}{1 + g_m R_S}$$



for example:

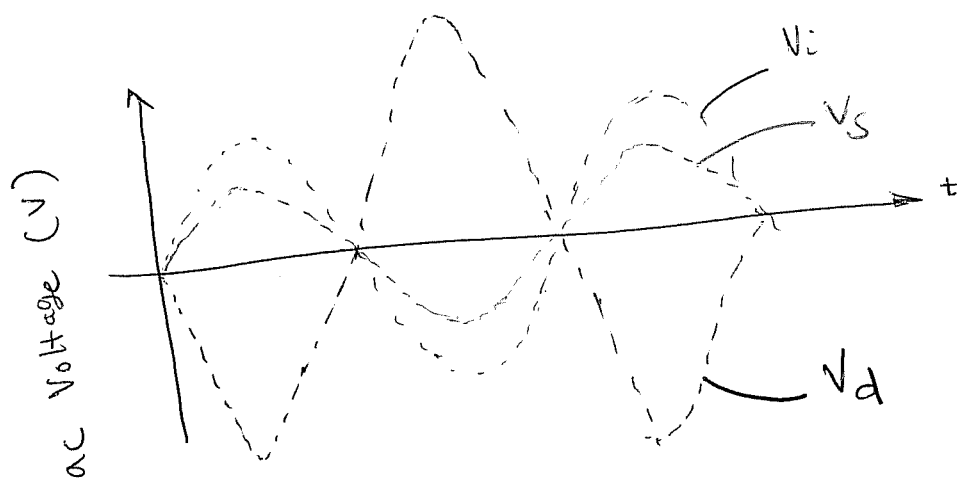

* Remember that the actual nodes have DC components to, i.e.

$$V_{TOT} = V_{DC} + V_{AC}$$