

8.1

(a) Referring to Fig. 8.2,

$$\text{note that } I_{D1} = I_{D2} = \frac{I}{2} = \frac{0.2 \text{ mA}}{2} \\ = 0.1 \text{ mA}$$

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) V_{OV}^2$$

$$V_{OV} = \sqrt{\frac{2I_D}{k_n'(W/L)}} = \sqrt{\frac{2(0.1 \text{ mA})}{0.4 \text{ mA/V}^2(12.5)}} \\ = 0.2 \text{ V}$$

$$V_{GS} = V_{ni} + V_{OV} = 0.5 + 0.2 = 0.7 \text{ V}$$

(b) If $V_{cm} = 0$,

$$V_{S1} = V_{S2} = V_G - V_{GS} = 0 - 0.7 = -0.7 \text{ V}$$

$$I_{D1} = I_{D2} = \frac{0.2 \text{ mA}}{2} = 0.1 \text{ mA}$$

$$V_{D1} = V_{D2} = V_{DD} - I_{D1}R_D \\ = 1 \text{ V} - (0.1 \text{ mA})(10 \text{ K}) = 0 \text{ V}$$

(c) Now, if $V_{ICM} = 0.1 \text{ V}$,

$$V_{S1} = V_{S2} = V_C - V_{GS} = 0.1 \text{ V} - 0.7 \text{ V} \\ = -0.6 \text{ V}$$

Since I is a constant current source, I_{D1} and I_{D2} remain at 0.1 mA

This means that

 V_{D1} and V_{D2} are still 0 V(d) $V_{ICM} = -0.1 \text{ V}$,

$$V_{S1} = V_{S2} = V_G - V_{GS} = -0.1 \text{ V} - 0.7 \\ = -0.8 \text{ V}$$

Still, $I_{D1} = I_{D2} = 0.1 \text{ mA}$

$$V_{D1} = V_{D2} = 0 \text{ V}$$

$$(e) V_{CM(\max)} = V_{DD} - I_D R_D - V_{OV} + V_{GS} \\ = 1 - (0.1 \text{ mA})(10 \text{ K}) - 0.2 + 0.7 = +0.5 \text{ V}$$

$$(f) V_S(\min) = -V_{SS} + V_{CS}(\min) \\ = -1 + 0.2 = -0.8 \text{ V}$$

$$V_{CM}(\min) = V_S(\min) + V_{GS} = -0.8 \text{ V} + 0.7 \text{ V} \\ = -0.1 \text{ V}$$

8.2

$$V_{ip} = -0.8 \text{ V } k_p' \frac{W}{L} = 4 \text{ mA/V}^2$$

$$(a) V_{G1} = V_{G2} = 0 \text{ V}$$

$$|V_{ov}| = \sqrt{0.5 \text{ mA} / 4 \text{ mA/V}^2} = 0.354 \text{ V}$$

$$|V_{GS}| = |V_{ip}| + |V_{ov}| = 1.154 \text{ V}$$

$$V_S = V_{G1} + |V_{GS}| = 1.154 \text{ V}$$

$$V_{D1} = V_{D2} = -2.5 \text{ V} + \left(\frac{0.5 \text{ mA}}{2} \right) (4 \text{ k}\Omega) \\ = -1.5 \text{ V}$$

(b) Current source requires 0.5 V

$$V_{CM(\max)} = 2.5 \text{ V} - 0.5 \text{ V} - 0.8 \text{ V} - 0.354 \text{ V} \\ = 0.846 \text{ V}$$

$$V_{CM(\min)} = -2.5 \text{ V} + \left(\frac{0.5 \text{ mA}}{2} \right) (4 \text{ k}\Omega) - 0.8 \text{ V} \\ = -2.3 \text{ V}$$

8.3

Refer to Fig. 8.2

$$V_{OV} = \sqrt{\frac{2I_D}{k_n'(W/L)}} = \sqrt{\frac{2(0.1 \text{ mA})}{0.4 \text{ mA/V}^2(12.5)}} = 0.2 \text{ V}$$

$$(a) V_{GS} = V_{OV} + V_t = 0.2 \text{ V} + 0.5 \text{ V} = 0.7 \text{ V}$$

$$V_S = V_G - V_{GS} = 0 - 0.7 \text{ V} = -0.7 \text{ V}$$

$$V_{D1} = V_{D2} = V_{DD} - i_{D1}R_D = 1.0 \text{ V} - 0.1 \text{ mA} \\ (10 \text{ k}\Omega) = 0 \text{ V}$$

$$V_{D2} - V_{D1} = 0 \text{ V}$$

(b) For $i_{D1} = 0.15 \text{ mA}$, $i_{D2} = 0.05 \text{ mA}$,

$$i_{D1} = \frac{I}{2} + \frac{I}{V_{OV}} \cdot \frac{v_{id}}{2} \rightarrow v_{id} = \left(\frac{2i_{D1}}{I} - 1 \right) \cdot V_{OV}$$

$$v_{id} = \left[\frac{2(0.15 \text{ mA})}{0.2 \text{ mA}} - 1 \right] (0.2 \text{ V}) = 0.1 \text{ V}$$

$$V_{GS1} = \sqrt{\frac{2(0.15 \text{ mA})}{0.4 \text{ mA/V}^2(12.5)}} + 0.5 \text{ V} = 0.745 \text{ V}$$

$$V_S = V_G - V_{GS1} = 0.1 \text{ V} - 0.745 \text{ V} = -0.645 \text{ V}$$

$$V_{D1} = V_{DD} - i_{D1}R_D = 1.0 \text{ V} - 0.15 \text{ mA}(10 \text{ k}\Omega) \\ = -0.5 \text{ V}$$

$$V_{D2} = 1.0 \text{ V} - (0.05 \text{ mA})(10 \text{ k}\Omega) = +0.5 \text{ V}$$

$$V_{D2} - V_{D1} = 1.0 \text{ V}$$

(c) $i_{D1} = 0.2 \text{ mA}$, $i_{D2} = 0$:

$$V_{G1} = v_{id} = \sqrt{2} \cdot V_{OV} = 1.414(0.2 \text{ V}) = 0.283 \text{ V}$$

$$V_{GS} = \sqrt{\frac{2(0.2 \text{ mA})}{0.4 \text{ mA/V}^2(12.5)}} + 0.5 \text{ V} = 0.783$$

$$V_S = V_G - V_{GS} = 0.283 \text{ V} - 0.783 \text{ V} = -0.5 \text{ V}$$

$$V_{D1} = 1.0 \text{ V} - (0.2 \text{ mA})(10 \text{ k}\Omega) = -1.0 \text{ V}$$

$$V_{D2} = +1.0 \text{ V}$$

$$V_{D2} - V_{D1} = 2.0 \text{ V}$$

(d) $i_{D1} = 0.05 \text{ mA}$ } opposite case of (b)
 $i_{D2} = 0.05 \text{ mA}$ }

For example,

$$v_{id} = \left[\frac{2(0.05 \text{ mA})}{0.2 \text{ mA}} - 1 \right] (0.2 \text{ V}) = -0.1 \text{ V}$$

$$V_{GS} = \sqrt{\frac{2(0.05 \text{ mA})}{0.4 \text{ mA/V}^2(12.5)}} + 0.5 \text{ V} = 0.641 \text{ V}$$

$$V_S = V_G - V_{GS} = -0.1 \text{ V} - 0.641 \text{ V} = -0.741 \text{ V}$$

$$V_{D1} = 1.0 \text{ V} - (0.05 \text{ mA})(10 \text{ k}\Omega) = +0.5 \text{ V}$$

$$V_{D2} = 1.0 \text{ V} - (0.05 \text{ mA})(10 \text{ k}\Omega) = -0.5 \text{ V}$$

$$V_{D2} - V_{D1} = -1.0 \text{ V}$$

(e) $i_{D1} = 0 \text{ mA}$, $i_{D2} = 0.2 \text{ mA}$ is the opposite of (c):

$$v_{id} = -\sqrt{2}(V_{OV}) = -\sqrt{2}(0.2 \text{ V}) = -0.283 \text{ V}$$

For $i_{D2} = 0.2 \text{ mA}$, $V_{GS2} = 0.783 \text{ V}$, So that

$$V_S = -0.783 \text{ V}$$


$$V_{D1} = 1.0 \text{ V},$$

$$V_{D2} = -1.0 \text{ V} \rightarrow V_{D2} - V_{D1} = -2 \text{ V}$$

The results are summarized in the following table:

Case	V_{id} (V)	i_{D1} (mA)	i_{D2} (mA)	V_S (V)	V_{D1} (V)	V_{D2} (V)	$V_{D2} - V_{D1}$ (V)
(a)	0	0.1	0.1	-0.7	0	0	0
(b)	0.1	0.15	0.05	-0.645	-0.5	0.5	1.0
(c)	0.283	0.2	0	-0.5	-1.0	1.0	2.0
(d)	-0.1	0.05	0.15	-0.741	0.5	-0.5	-1.0
(e)	-0.283	0	0.2	-0.783	1.0	-1.0	-2.0

8.4

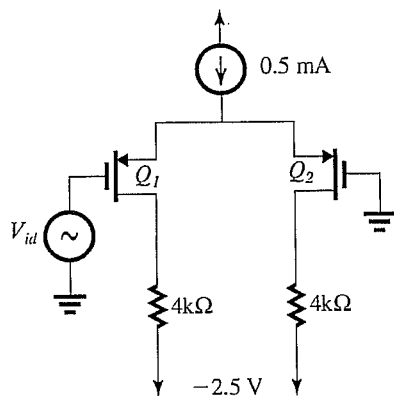

$$V_{G2} = 0$$

$$V_{G1} = v_{id}$$

When all the current is on Q_1 :

$$I = \frac{1}{2} \left(k'_p \frac{W}{L} \right) (V_{GS1} - V_t)^2$$

$$\Rightarrow V_{GS1} = V_t + \sqrt{\frac{2I}{k'_p W/L}}$$

$$= V_t + \sqrt{2} V_{OV}$$

and V_{GS2} is reduced to V_t , thus $V_S = -V_t$.

Then $v_{id} = v_{GS1} + v_S$

$$= V_t + \sqrt{2} V_{OV} - V_t = \sqrt{2} V_{OV}$$

In a similar manner as for the NMOS Differential

Amplifier, as v_i reaches $-\sqrt{2} V_{OV}$ Q_1 turns off and Q_2 on. Thus the steering range is

$$\sqrt{2} V_{OV} \leq v_i \leq -\sqrt{2} V_{OV}$$

For this particular case

$$V_{OV} = \sqrt{\frac{0.25 \text{ mA}}{4 \text{ mA/V}^2}} = 0.25 \text{ V}$$

$$\sqrt{2} \times -0.25 \leq v_{id} \leq \sqrt{2} \times 0.25$$

$$-0.35 \leq v_{id} \leq 0.35$$

when $V_{id} = -0.35 \text{ V}$,

$$i_{D1} = 0.5 \text{ mA}, i_{D2} = 0$$

$$V_S = -V_{r2} = +0.8 \text{ V}$$

$$V_{D1} = 4 \text{ k}\Omega \times 0.5 \text{ mA} - 2.5 = -0.5 \text{ V}$$

$$V_{D2} = 0 - 2.5 \text{ V} = -2.5 \text{ V}$$

when $v_{id} = +0.35 \text{ V}$,

$$i_{D1} = 0 ; i_{D2} = 0.5 \text{ mA}$$

$$V_S = v_{id} - v_{GS1} = v_{id} - V_{t1} = 0.35 \text{ V} + 0.8 \text{ V} = 1.15 \text{ V}$$

$$V_{D1} = -2.5 \text{ V}$$

$$V_{D2} = -0.5 \text{ V}$$

8.5

$$V_{G1} = v_{id} i_{D1} = 0.11 \text{ mA}$$

$$V_{G2} = 0 \quad i_{D2} = 0.09 \text{ mA}$$

$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2$$

For Q_1 :

$$0.11 \text{ m} = \frac{1}{2} 5 \text{ m} (V_{GS1} - 0.5)^2$$

$$\rightarrow V_{GS1} = 0.71 \text{ V}$$

For Q_2 :

$$0.09 \text{ m} = \frac{1}{2} 5 \text{ m} (V_{GS2} - 0.5)^2$$

$$\rightarrow V_{GS2} = 0.69 \text{ V}$$

$$V_S = -V_{GS2} = -0.69 \text{ V}$$

$$v_{id} = V_S + V_{GS1} = -0.69 + 0.71 = 0.02 \text{ V}$$

$$\begin{aligned} V_{D2} - V_{D1} &= 10 \text{ k}\Omega (i_{D1} - i_{D2}) \\ &= 10 \text{ kV} (0.11 - 0.09) \text{ mA} \\ &= 0.2 \text{ V} \end{aligned}$$

thus

$$\frac{V_{D2} - V_{D1}}{v_{id}} = \frac{0.2}{0.02} = 10$$

when $i_{D1} = 0.09 \text{ mA}$ and

$$i_{D2} = 0.11 \text{ mA}$$

is the reverse condition from the case we just studied, thus $v_{id} = -0.02 \text{ V}$

8.6

$$\begin{aligned} V_{GS} &= V_{in} + V_{OV} = 0.5 \text{ V} + 0.2 \text{ V} = 0.7 \text{ V} \\ V_{D4} &= V_{G4} = -V_{S5} + V_{GS} = -1.2 \text{ V} + 0.7 \text{ V} \\ &= -0.5 \text{ V} \end{aligned}$$

$$R = \frac{V_{DD} - V_{D4}}{0.1 \text{ mA}} = \frac{1.2 \text{ V} - (-0.5 \text{ V})}{0.1 \text{ mA}} = 17 \text{ k}\Omega$$

$$R_D = \frac{V_{DD} - V_{D1}}{0.4 \text{ mA} / 2} = \frac{1.2 \text{ V} - 0.2 \text{ V}}{0.2 \text{ mA}} = 5 \text{ k}\Omega$$

$$\begin{aligned} \left(\frac{W}{L}\right)_1 &= \left(\frac{W}{L}\right)_2 = \frac{0.4 \text{ mA}}{2} \left[\frac{k'_n V_{OV}^2}{n} \right]^{-1} \\ &= 0.2 \text{ mA} [(0.25 \text{ mA} / \text{V}^2)(0.2 \text{ V})^2]^{-1} = 20 \end{aligned}$$

$$\left(\frac{W}{L}\right)_3 = 0.4 \text{ mA} [0.01 \text{ mA}]^{-1} = 40$$

$$\left(\frac{W}{L}\right)_4 = 0.1 \text{ mA} [0.01 \text{ mA}]^{-1} = 10$$

$$\begin{aligned} V_{Cm(\max)} &= V_{in} + V_{DD} - (I/2)R_D \\ &= 0.5 \text{ V} + 1.2 \text{ V} - (0.2 \text{ mA})(5 \text{ k}\Omega) = 0.7 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{Cm(\min)} &= -V_{S5} + V_{OV3} + V_{in} + V_{OV1} \\ &= -1.2 \text{ V} + 0.2 \text{ V} + 0.5 \text{ V} + 0.2 \text{ V} = -0.3 \text{ V} \end{aligned}$$

8.7

$$|V_{id}|_{\max} = 160 \text{ mV}$$

$$\left(\frac{V_{id}/2}{V_{OV}}\right)^2 = 0.1$$

$$V_{OV}^2 = \frac{(80 \text{ mV})^2}{0.1}$$

$$V_{OV} = \sqrt{\frac{(80 \text{ mV})^2}{0.1}} = 253 \text{ mV}$$

$$I = 0.4 \text{ mA}$$

$$k'_n = 0.2 \text{ mA} / \text{V}^2$$

$$\begin{aligned} \frac{W}{L} &= I \cdot \left[\frac{k'_n V_{OV}^2}{n} \right]^{-1} \\ &= 0.4 \cdot [(0.2)(0.253)^2]^{-1} = 31.2 \end{aligned}$$

$$g_m = \frac{I}{V_{OV}} = \frac{0.4 \text{ mA}}{0.253 \text{ V}} = 1.58 \text{ mA} / \text{V}$$

8.8

$$\left(\frac{v_{id\max}/2}{V_{OV}}\right)^2 = K$$

$$\Rightarrow 2V_{OV}\sqrt{K} = v_{id\max}$$

Q.E.D.

$$i_{D1} = \frac{I}{2} + \left(\frac{I}{V_{OV}}\right)\frac{v_{id}}{2}\sqrt{1-K}$$

$$i_{D1} = \frac{I}{2} \pm \frac{I}{V_{OV}} \cdot \frac{2}{2} V_{OV}\sqrt{K} \cdot \sqrt{1-K}$$

$$\rightarrow i_{D1} = \frac{I}{2} \pm I\sqrt{K(1-K)}$$

$$\text{thus } \Delta I = 2I\sqrt{K(1-K)}$$

Q.E.D.

For $K = 0.01$

$$\begin{aligned} \Delta I &= 2I\sqrt{0.01(1-0.01)} \\ &= 0.198 \times I \end{aligned}$$

$$V_{id\max} = 2V_{OV}\sqrt{0.01} = 0.2V_{OV}$$

For $K = 0.1$

$$\Delta I = 2I\sqrt{0.1(1-0.1)} = 0.8I$$

$$\begin{aligned} V_{id\max} &= 2V_{OV}\sqrt{0.2} \\ &= 0.894 \cdot V_{OV} \end{aligned}$$

8.9

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{tn})^2$$

$$\frac{400}{2} = \frac{1}{2} (200) \left(\frac{20}{0.5}\right) (V_{GS} - 0.5)^2$$

$$(V_{GS} - 0.5)^2 = 1/20 \text{ V}$$

$$V_{GS} = 0.724 \text{ V}$$

$$g_m = \frac{2I_D}{V_{GS} - V_{tn}} = \frac{2 \cdot 400 \mu\text{A}}{0.724 \text{ V} - 0.5 \text{ V}}$$

$$= 3.57 \text{ mA/V}$$

V_{id} for full current switching

$$= \sqrt{2} (V_{GS} - V_{tn}) = 0.317 \text{ V}$$

To double this value, V_{OV} , so quadruple I_D to 1.6 mA

8.10

$$V_{OV} = 0.25 \text{ V} \quad g_m = 1 \text{ mA} / \text{V} \quad V_{tn} = 0.8 \text{ V}$$

$$k'_n = 100 \mu\text{A} / \text{V}^2$$

$$I = g_m V_{OV} = 0.25 \text{ mA}$$

$$I_D = \frac{I}{2} = \frac{1}{2} k'_n \frac{W}{L} V_{OV}^2$$

$$\begin{aligned} \frac{W}{L} &= I / \left(k'_n V_{OV}^2 \right) \\ &= 0.25 \text{ mA} / (0.1 \text{ mA} / \text{V}^2 \cdot (0.25 \text{ V})^2) \\ &= 0.25 \text{ mA} / 0.00625 \text{ mA} = 40 \end{aligned}$$

8.11

$$i_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_t)^2$$

$$50 = \frac{1}{2} \times 400 (V_{GS} - 1)^2$$

$$\Rightarrow V_{GS} = 1.5 \text{ V}$$

$$\text{For } v_{G1} = v_{G2} = 0, v_S = -1.5 \text{ V}$$

$$\text{For } v_{G1} = v_{G2} = 2 \text{ V}, v_S = +0.5 \text{ V}$$

The drain currents are equal in both cases.

$$\text{For } V_{G2} = 0 :$$

To reduce i_{D2} by 10%,

$$i_{D2} = 0.9 \times 50 = 45 \mu\text{A}$$

$$i_{D1} = 55 \mu\text{A}$$

$$v_{GS2} = \sqrt{\frac{2i_{D2}}{400}} + 1 = 1.47 \text{ V}$$

$$v_{GS1} = \sqrt{\frac{2 \times 55}{400}} + 1 = 1.52 \text{ V}$$

$$\text{Thus, } V_{G1} \equiv v_{GS1} - v_{GS2} = 0.05 \text{ V}$$

To increase i_{D2} by 10%

$$i_{D2} = 55 \mu\text{A}$$

$$i_{D1} = 45 \mu\text{A}$$

$$v_{GS2} = 1.52 \text{ V}$$

$$v_{GS1} = 1.47 \text{ V}$$

$$\Rightarrow V_{G1} = -0.05 \text{ V}$$

i_{D2}/i_{D1}	i_{D2} (μA)	i_{D1} (μA)	V_{GS2} (V)	V_{GS1} (V)	$V_G - V_{G1}$ (V)
1	50	50	1.5	1.5	0
0.5	33.3	66.7	1.408	1.577	-0.17
0.8	47.4	52.6	1.487	1.513	-0.026
0.99	47.75	50.25	1.4886	1.5012	-0.013

$$\text{For } i_{D1}/i_{D2} = 20 \Rightarrow i_{D2} = 4.76 \mu\text{A}$$

$$i_{D1} = 95.24 \mu\text{A}$$

$$V_{GS2} = 1.154 \text{ V}, V_{GS1} = 1.690$$

$$\text{Thus } V_{G1} - V_{G2} = 0.536 \text{ V}$$

8.12

$$\text{(a) } V_{od} = V_{D2} - V_{D1} =$$

$$(V_{DD} - i_{D2}R_D) - (V_{DD} - i_{D1}R_D) = (i_{D1} - i_{D2})R_D$$

USING 8.23 AND 8.24

$$V_{od} = \left[\left(\frac{I}{V_{OV}} \right) \left(\frac{V_{id}}{2} \right) \sqrt{1 - \left(\frac{V_{id}/2}{V_{OV}} \right)^2} \right] R_D$$

$$= IR_D \frac{V_{id}}{V_{OV}} \sqrt{1 - \left(\frac{V_{id}/2}{V_{OV}} \right)^2}$$

(b) see plot

slope of linear portion

$$= \frac{d}{dV_{id}} \left(\frac{IR_D}{V_{OV}} \cdot V_{id} \right) = IR_D / V_{OV}$$

(c) see plot

when the bias current is doubled, V_{OV} so

$$V_{od}/V_{id} = \frac{2IR_D}{\sqrt{2} V_{OV}} \sqrt{1 - \left(\frac{V_{id}/2}{\sqrt{2} V_{OV}} \right)^2}$$

increases by a factor of $\sqrt{2}$ the slope of the linear

part has increased by a factor of $\sqrt{2}$

(d) see plot

If W/L is doubled, V_{OV} reduces by a factor at $\sqrt{2}$

$$\text{so } V_{od}/V_{id} = \frac{2IR_D}{\sqrt{2} V_{OV}} \sqrt{1 - \left(\frac{V_{id}/\sqrt{2}}{V_{OV}} \right)^2}$$

The slope of the linear part has increased by factor of $\sqrt{2}$ compared to (b)

8.13

$$I = 0.4 \text{ mA} \quad W/L = 32 \quad k_n' = \mu_n C_{ox}$$

$$= 200 \mu\text{A}/\text{V}^2$$

$$V_A = 10 \text{ V} \quad R_D = 5 \text{ k}\Omega$$

$$V_{OV}' = \sqrt{I/k_n' \left(\frac{W}{L} \right)} = \sqrt{0.4/(0.2 \cdot 32)}$$

$$= 0.25 \text{ V}$$

$$g_m = \frac{I}{V_{OV}} = \frac{0.4 \text{ mA}}{0.25 \text{ V}} = 1.6 \text{ mA/V}$$

$$r_O = \frac{V_A}{I_D} = \frac{10 \text{ V}}{0.2 \text{ mA}} = 50 \text{ k}\Omega$$

$$A_d = g_m (R_D \parallel r_O) = 1.6 (5 \parallel 50)$$

$$= 1.6 (4.54) = 7.3 \text{ V/V}$$

8.14


$$\left(\frac{V_{id}/2}{V_{OV}} \right)^2 = 0.05$$

$$\left(\frac{0.1/2}{V_{OV}} \right) = \sqrt{0.05}$$

$$V_{OV} = \frac{0.05}{\sqrt{0.05}} = 0.224 \text{ V}$$

$$g_m = \frac{I}{V_{OV}}$$

The figure belongs to 8.12

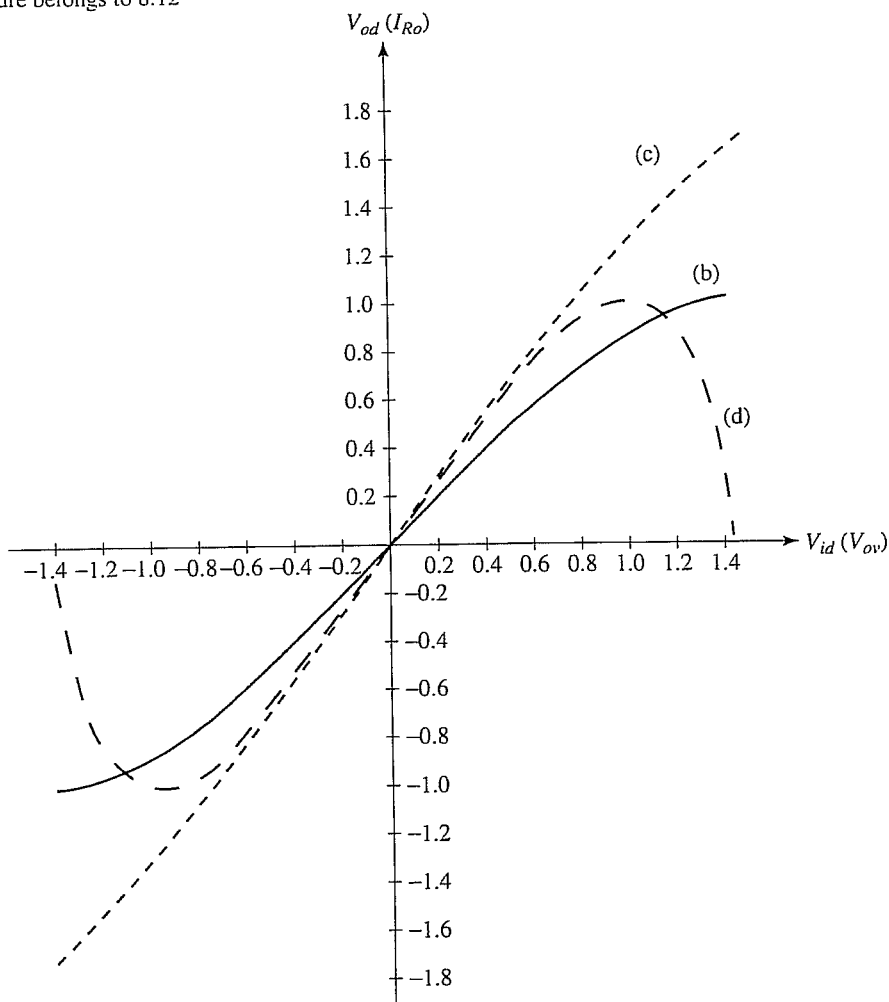

$$I = g_m V_{OV} = (1 \text{ mA/V})(0.224 \text{ V}) \\ = 0.224 \text{ mA}$$

$$A_d = g_m R_D = (1 \text{ mA/V})(10 \text{ k}\Omega) = 10 \\ V_{od} = A_d V_{id} = (10)(0.1 \text{ V}) = 1 \text{ V}$$

$$\frac{W}{L} = I / (k'_n V_{OV}^2) \\ = 0.224 / (0.2 \times 0.224^2) \\ = 22.3$$

8.15+1 V supplies not more than 2 mW $A_n = 5 \text{ V/V}$

$$V_D = 0.5 \text{ V} \quad K_n' = \mu_n C_{ox} = 0.4 \text{ mA/V}^2$$

$$I = \frac{2 \text{ mW}}{1 \text{ V} - (-1 \text{ V})} = 1 \text{ mA}$$

$$R_D = \frac{1 \text{ V} - 0.5 \text{ V}}{1/2 I} = \frac{0.5 \text{ V}}{0.5 \text{ mA}} = 1 \text{ k}\Omega$$

$$g_m = \frac{A_d}{R_D} = \frac{5 \text{ V/V}}{1 \text{ k}\Omega} = 5 \text{ mA/V}$$

$$V_{OV} = \frac{I}{g_m} = \frac{1 \text{ mA}}{5 \text{ mA/V}} = 0.2 \text{ V}$$

$$\frac{W}{L} = 2(I/2) / (k'_n V_{OV}^2)$$

$$= 1 \text{ mA} / (0.4 \text{ mA/V}^2 \cdot (0.2 \text{ V})^2) = 62.5$$

BECAUSE WE PICKED $I = 1 \text{ mA}$ THIS IS THE SOLUTION WITH THE HIGHEST ALLOWABLE POWER. THIS SOLUTION WILL ALSO THEREFORE HAVE THE WIDEST RANGE OF DIFFERENTIAL MODE OPERATION. AN INFINITE NUMBER OF OTHER SOLUTIONS EXIST.

8.16

$$I = \frac{2 \text{ mW}}{1 \text{ V} - (-1 \text{ V})} = 1 \text{ mA}$$

$$0.4 \text{ V} = 2\sqrt{2} V_{OV} \quad V_{OV} = 0.141 \text{ V}$$

$$R_D = A_d \frac{V_{OV}}{I} = 5^{V/V} \left(\frac{0.141 \text{ V}}{1 \text{ mA}} \right) = 705 \Omega$$

$$\frac{W}{L} = I / (k'_n V_{OV}^2) = 125$$

since $A_d = g_{m1,2}(r_{O1} \parallel R'_O)$,

$$A_d = g_{m1,2} \left[r_{O1,2} \parallel \left(\frac{r_{O3,4}}{1 + g_{m3,4} r_{O3,4}} \right) \right]$$

(b) If r_O is ignored,

$$R'_D = \frac{1}{\frac{1}{r_O} + g_m} \approx \frac{1}{g_m}$$

so that

$$A_d = g_{m1,2} \left(\frac{1}{g_{m3,4}} \right)$$

since $g_m = \sqrt{2 \mu_n C_{OX} (W/L) I_D}$,

$$\begin{aligned} A_d &= \frac{g_{m1,2}}{g_{m3,4}} = \frac{\sqrt{2 \mu_n C_{OX} (W/L)_{1,2} I_D}}{\sqrt{2 \mu_p C_{OX} (W/L)_{3,4} I_D}} \\ &= \sqrt{\frac{\mu_n}{\mu_p} \cdot \frac{(W/L)_{1,2}}{(W/L)_{3,4}}} \end{aligned}$$


(c) If $\mu_n = 4\mu_p$ and $L_1 = L_2 = L_3 = L_4 = L$,

$$A_d = 10 \text{ V/V} = \sqrt{\frac{4\mu_n}{\mu_p} \cdot \frac{(W/L)_{1,2}}{(W/L)_{3,4}}}$$

$$\frac{10}{2} = \sqrt{\frac{(W)_{1,2}}{(W)_{3,4}}}$$

$$\left(\frac{W_{1,2}}{W_{3,4}} \right) = 25$$

8.21
HALF-CIRCUIT

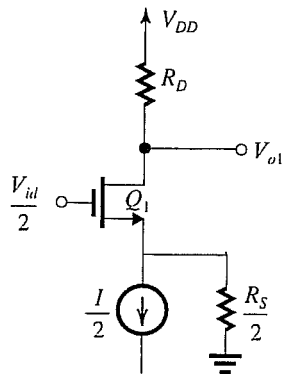

small-signal analysis

$$V_{gs} = \frac{V_{id}}{2} - g_m V_{gs} \frac{R_s}{2}$$

$$V_{gs} = \frac{V_{id}/2}{1 + g_m \frac{R_s}{2}}$$

$$V_{O1} = -g_m V_{gs} R_D = -g_m \left[\frac{V_{id}/2}{1 + g_m \frac{R_s}{2}} \right] R_D$$

$$A_d = \frac{V_{O1}}{V_{id}} = \frac{g_m R_D}{1 + g_m \frac{R_s}{2}}$$

when $R_s = 0$ $A_d = g_m R_D$ (agrees with Eqn. 8.35)

when $R_s = \frac{2}{g_m}$ the differential gain is reduced

by half

8.22

(a) $V_{G1} = V_{G2} = 0V$

$V_{S1} = V_{S2}$ assuming matching components

$$\begin{aligned} V_{S1} &= V_{G1} - V_{GS1} = 0V - (V_t + V_{OV}) \\ &= -(V_t + V_{OV}) \end{aligned}$$

(b) zero current flows through Q_3

$$\begin{aligned} V_{OV3} &= V_C - V_{S1} - V_t = V_C - (-(V_t + V_{OV})) - V_t \\ &= V_C + V_t \\ &= V_C + V_{OV} \end{aligned}$$

(c) $V_{G1} = -V_{G2} = V_{id}/2$

V_{S1} is now more negative than in (a) and V_{S2} is now less negative than in (a) so there is a voltage across Q_3 . If this voltage is small and if V_C is such that $V_{GS3} > V_t$ then Q_3 will operate in triode.

$$r_{Ds3} = \left[k'_n \frac{W}{L} V_{ov3} \right]^{-1}$$

$$g_{m1} = g_{m2} = \frac{1/2 k'_n \frac{W}{L} V_{ov}^2}{V_{ov}} = 1/2 k'_n \frac{W}{L} V_{ov}$$

$$\text{so } r_{Ds3} = \left[g_{m1} \frac{V_{ov3}}{V_{ov}} \right]^{-1} = \frac{V_{ov}}{V_{ov3} g_{m1}}$$

$$(d) r_{DS3} = \frac{V_{OV}}{V_{OV3}} \cdot \frac{1}{g_{m1}}$$

$$(i) R_s = \frac{1}{g_{m1}} \therefore V_{OV3} = V_{OV}$$

From (b) $V_{OV3} = V_C + V_{OV}$ so $V_C = 0V$

$$(ii) R_s = \frac{1}{2 g_{m1}} \therefore V_{OV3} = 2 V_{OV}$$

so $V_C = V_{OV}$

8.23

(a) $V_{G1} = V_{G2} = 0V$

$$V_{S1} = V_{S2} = -(V_t + V_{OV})$$

Zero current flows through Q_3 and Q_4

Q_3 and Q_4 have the same overdrive voltage as Q_1 and Q_2

$$r_{DS3} = r_{DS4} = \left[k'_n \left(\frac{W}{L} \right)_{3,4} V_{OV3,4} \right]^{-1}$$

	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7	
I_{Dm}	30	30	30	90	90	30	90	$\mu\text{A}/\text{V}^2$
I_D	50	50	100	50	50	100	100	μA
V_{OV}	-0.25	-0.25	-0.3	0.3	0.3	-0.3	0.3	V
$\frac{W}{L}$	53.3	53.3	74.1	12.3	12.3	74.1	24.7	
V_{GS}	-0.95	-0.95	-1	1	1	-1	1	V

Since $g_m = \frac{|I_D|}{|V_{OV}|/2}$,

$$|V_{OV1}| = |V_{OV2}| = |V_{OV4}| = |V_{OV5}| = \frac{2I_D}{g_m}$$

$$= \frac{2(50 \mu\text{A})}{400 \mu\text{A}/\text{V}} = 0.25 \text{ V}$$

so,

$$V_{GS1} = V_{GS2} = V_{OV} + V_{xp} = -0.25 - 0.7$$

$$= -0.95 \text{ V}$$

For $\left(\frac{W}{L}\right)$ ratios

$$I_D = \frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{OV})^2$$

So that

$$\frac{W}{L} = \frac{2I_D}{\mu C_{ox} V_{OV}^2}$$

For Q_7 ,

$$\left(\frac{W}{L}\right)_7 = \frac{2(100 \mu\text{A})}{90 \mu\text{A}/\text{V}^2 (0.3 \text{ V})^2} = 24.7$$

For Q_4 and Q_5 ,

$$\left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_5 = \frac{2(50 \mu\text{A})}{90 \mu\text{A}/\text{V}^2 (0.3)^2} = 12.3$$

For Q_1 and Q_2 ,

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \frac{2(50 \mu\text{A})}{30 \mu\text{A}/\text{V}^2 (0.25)^2} = 53.3$$

For Q_6 and Q_3 ,

$$\left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_3 = \frac{2(100 \mu\text{A})}{30 \mu\text{A}/\text{V}^2 (0.3 \text{ V})^2} = 74.1$$

In summary, the results are as follows:

8.25

$$(a) I_{D1} = \frac{1}{2} k_n' \frac{W}{L} (V_{GS1} - V_t)^2$$

$$I_{D2} = \frac{1}{2} k_n' \left(2 \times \frac{W}{L}\right) (V_{GS2} - V_t)^2$$

Since $V_{GS} - V_t$ is equal for both transistors :

$$\Rightarrow \frac{I_{D1}}{I_{D2}} = \frac{1}{2}; I_{D2} = 2I_{D1}$$

$$\text{but } I = I_{D1} + I_{D2} = 3I_{D1}$$

$$I_{D1} = I/3$$

$$I_{D2} = 2I/3$$

$$(b) V_{OV} = V_{GS} - V_t$$

$$V_{OV1} = V_{OV2} = V_{OV}$$

$$\text{For } Q_1: \frac{I}{3} = \frac{1}{2} k_n' \left(\frac{W}{L}\right) V_{OV}^2$$

$$\Rightarrow V_{OV} = \sqrt{\frac{2}{3} \frac{I}{k_n' W/L}}$$

$$(c) g_m = \frac{2I_D}{V_{OV}} \rightarrow g_{m1} = \frac{2I}{3V_{OV}}$$

$$g_{m2} = \frac{4}{3} \frac{I}{V_{OV}}$$

$$v_{O1} = -g_{m1} \times \frac{v_{id}}{2} \cdot R_D$$

$$= -\frac{2}{3} \frac{I}{V_{OV}} \cdot R_D \cdot v_{id}$$

$$v_{O2} = +g_{m2} \times \frac{v_{id}}{2} \cdot R_D$$

$$= \frac{4}{3} \frac{I}{V_{OV}} \cdot R_D \cdot v_{id}$$

$$\Rightarrow \frac{v_{O2} - v_{O1}}{v_{id}} = \left(\frac{4}{3} + \frac{2}{3}\right) \frac{I}{V_{OV}} \cdot R_D$$

$$= 2 \times \frac{I}{V_{OV}} \cdot R_D$$

8.26

By equation 8.38 $A_d = g_{m1}(R_{on} \parallel R_{op})$

$$= g_{m1}[(g_{m3}r_{O3})r_{O1} \parallel (g_{m5}r_{O5})r_{O7}]$$

If all transistors have the same channel length and the

same $|V_{OV}|$ and $|V_A|$ Since $g_m = \frac{2I_D}{V_{OV}}$ and

$$r_O = \frac{V_A}{I_D} \text{ and with } g_m \text{ and } r_o \text{ the same for all devices,}$$

$$A_d = \frac{2I_D}{V_{OV}} \left(\left(\frac{2I_D}{V_{OV}} \cdot \frac{V_A}{I_D} \right) \frac{V_A}{I_D} \right) \parallel \left(\left(\frac{2I_D}{V_{OV}} \cdot \frac{V_A}{I_D} \right) \frac{V_A}{I_D} \right)$$

$$= \frac{2I_D}{V_{OV}} \left[\frac{2V_A^2}{V_{OV} I_D} \parallel \frac{2V_A^2}{V_{OV} I_D} \right]$$

$$= \left(\frac{2I_D}{V_{OV}} \cdot \frac{V_A^2}{V_{OV} I_D} \right)$$

$$= \frac{2V_A^2}{V_{OV}^2} = 2 \left(\frac{|V_A|}{|V_{OV}|} \right)^2$$

For $A_d = 1000 \text{ V/V}$ and $|V_{OV}| = 0.2 \text{ V}$

$$1000 = 2 \frac{|V_A|^2}{|V_{OV}|^2}$$

$$V_A = \sqrt{500} \cdot 0.2 \text{ V} = 4.47 \text{ V}$$

If $|V_A'| = 10 \text{ V}/\mu\text{A}$

$$L = \frac{4.47 \text{ V}}{10 \text{ V}/\mu\text{M}} = 0.447 \mu\text{m}$$

For high g_m the bias current should be high, but with $\pm 0.9 \text{ V}$ Supplies the bias current must not exceed $\frac{1 \text{ mW}}{1.8 \text{ V}} = 0.556 \text{ mA}$ to keep power dissipation at 1 mW

8.27

$I = 0.2 \text{ mA}$ $R_{SS} = 100 \text{ k}\Omega$ $R_D = 10 \text{ k}\Omega$

$k_n' \frac{W}{L} = 3 \frac{\text{mA}}{\text{V}^2}$ 1% mismatch in drain resistances

$$V_{OV} = \sqrt{I/k_n' \frac{W}{L}} = \sqrt{\frac{0.2 \text{ mA}}{3 \text{ mA}/\text{V}^2}} = 0.258 \text{ V}$$

$$g_m = \frac{I}{V_{OV}} = \frac{0.2 \text{ mA}}{0.258 \text{ V}} = 0.775 \text{ mA/V}$$

Equation 8.35

$$|A_d| = g_m R_D = 0.775 \frac{\text{mA}}{\text{V}} \cdot 10 \text{ k}\Omega = 7.75 \text{ V/V}$$

$$\text{Equation 8.49a } |A_{CM}| = \frac{R_D}{2R_{SS}} \cdot \frac{\Delta R_D}{R_D}$$

$$= \frac{10 \text{ k}\Omega}{2 \cdot 100 \text{ k}\Omega} \cdot 1\%$$

$$= 0.0005 = 0.5 \text{ mV/V}$$

Equation 8.50a

$$CMRR = \frac{|A_d|}{|A_{CM}|} = \frac{7.75}{0.0005} = 15500 = 83.8 \text{ dB}$$

8.28

$k_p' \frac{W}{L} = 4 \text{ mA}/\text{V}^2$ Current source resistance

$30 \text{ k}\Omega$

$$|V_{OV}| = \sqrt{I/k_p' \frac{W}{L}} = \sqrt{0.5 \text{ mA}/4 \text{ mA}/\text{V}^2}$$

$$= 0.353 \text{ V}$$

$$g_m = I/|V_{OV}| = \frac{0.5 \text{ mA}}{0.353 \text{ V}} = 1.42 \text{ mA/V}$$

$$|A_d| = g_m R_D = (1.42)(4 \text{ k}) = 5.68 \text{ V/V}$$

$$|A_{CM}| = \frac{R_D}{2R_{SS}} \cdot \frac{\Delta R_D}{R_D} = \frac{4}{2 \times 30} \cdot 2\%$$

$$= 1.33 \text{ mV/V}$$

$$CMRR = \frac{|A_d|}{|A_{CM}|} = \frac{5.68}{1.33 \times 10^{-3}} = 4.27 \times 10^3$$

$$= 72.6 \text{ dB}$$

8.29

$$(a) I_{D1} = I_{D2} = \frac{1 \text{ mA}}{2} = 0.5 \text{ mA}$$

$$= \frac{1}{2} k_n' \frac{W}{L} V_{OV}^2 = \frac{1}{2} (2.5 \text{ mA}/\text{V}^2) V_{OV}^2$$

$$V_{OV} = \left[\frac{2 \times 0.5 \text{ mA}}{2.5 \text{ mA}/\text{V}^2} \right]^{1/2} = \sqrt{0.4 \text{ V}^2} = 0.632 \text{ V}$$

$$V_{GS} = V_t + V_{OV} = 0.7 \text{ V} + 0.632 \text{ V} = 1.332 \text{ V}$$

$$V_S = (1 \text{ mA})(1 \text{ k}\Omega) = 1 \text{ V}$$

$$V_{cn} = V_S + V_{GS} = 1 \text{ V} + 1.332 \text{ V} = 2.332 \text{ V}$$

$$(b) A_d = g_m R_D = \frac{I}{V_{OV}} R_D$$

$$R_D = A_d \cdot \frac{V_{OV}}{I} = 8 \text{ V/V} \cdot \frac{0.632 \text{ V}}{1 \text{ mA}} = 5.06 \text{ k}\Omega$$

$$(c) V_D = V_{DD} - I_D R_D$$

$$= 5 \text{ V} - (0.5 \text{ mA})(5.06 \text{ k}\Omega)$$

$$= 2.47 \text{ V}$$

(d) From Equation 8.43

$$\frac{\Delta V_{D1}}{\Delta V_{CM}} = -\frac{R_D}{\frac{1}{g_m} + 2R_{SS}} = -\frac{-5.06 \text{ k}\Omega}{\frac{0.632 \text{ V}}{1 \text{ mA}} + 2(1 \text{ k}\Omega)}$$

$$= -1.92 \text{ V/V}$$

(e) Triode when $V_G - V_D = V_t$

$$(V_{CM} + \Delta V_{CM}) - (V_D - A_{CM} \cdot \Delta V_{CM}) = V_t$$

$$(2.332 \text{ V} + \Delta V_{CM}) - (2.47 \text{ V} - 1.92 \cdot \Delta V_{CM})$$

$$= 0.7 \text{ V}$$

$$2.92 \Delta V_{CM} = 0.7 \text{ V} - 2.332 \text{ V} + 2.47 \text{ V}$$

$$= 0.838 \text{ V}$$

$$\Delta V_{cm} = 0.838 \text{ V} / 2.92 = 0.287 \text{ V}$$

8.30

$$(a) R_{D1} = R_D + \frac{\Delta R_D}{2} \quad R_{D2} = R_D - \frac{\Delta R_D}{2}$$

$$g_{m1} = g_m + \frac{\Delta g_m}{2} \quad g_{m2} = g_m - \frac{\Delta g_m}{2}$$

$$i_{d1} = \frac{g_{m1} V_{icm}}{g_m R_{SS}} \quad i_{d2} = \frac{g_{m2} V_{icm}}{2g_m R_{SS}}$$

$$i_{d1} - i_{d2} = (g_{m1} - g_{m2}) \frac{V_{icm}}{2g_m R_{SS}}$$

8.70

The bias current I will split between the two differential transistors according to their base-emitter areas. So, the larger device will carry $\frac{2I}{3}$

Amperes,

while the second transistor will carry $\frac{I}{3}$ A

Assuming, for example, that Q_1 has the larger

area, $r_{e1} = \frac{V_T}{2I/3}$ and $r_{e2} = \frac{V_T}{I/3}$

Normally, we could apply the common-mode half circuit symmetry. But here, the amplifier is not symmetrical.

If $r_{e1} = \frac{3V_T}{2I}$ and $r_{e2} = \frac{3V_T}{I}$,

$i_{c1} \neq i_{c2}$

so, $V_{od} = -i_{c2}R_C - (-i_{c1}R_C) = (i_{c1} - i_{c2})R_C$

with $\alpha \approx 1$

$i_{c1} + i_{c2} \approx i_{e1} + i_{e2} = \frac{V_{Icm}}{R_{EE}}$ (since $R_{EE} \gg r_e$)

$$A_{cm} = \left| \frac{V_{od}}{V_{Icm}} \right| = \frac{\frac{1}{3}R_C}{R_{EE}} = \frac{12 \text{ K}}{3(500 \text{ K})} = 0.008 \text{ V/V}$$

8.71

For $I = 160 \mu\text{A}$,

$$I_D = \frac{I}{2} = \frac{160 \mu\text{A}}{2} = 80 \mu\text{A}$$

$$g_m = \sqrt{2k_n' \frac{W}{L} I_D} = \sqrt{2(4 \text{ mA/V}^2)(80 \mu\text{A})}$$

$$= 0.8 \text{ mA/V}$$

$R_D = 10 \text{ k}\Omega$, so that

$$A_d = g_m R_D = (0.8 \text{ mA/V})(10 \text{ k}) = 8 \text{ V/V}$$

using Eq. (8.108),

$$V_{OS} = \left(\frac{V_{ov}}{2} \right) \left(\frac{\Delta R_D}{R_D} \right) \text{ where } \frac{\Delta R_D}{R_D} = 0.02$$

(worst-case)

$$\text{since } g_m = \frac{I_D}{V_{ov}/2},$$

$$\frac{V_{ov}}{2} = \frac{I_D}{g_m} = \frac{80 \mu\text{A}}{0.8 \text{ mA/V}} = 0.1 \text{ V}$$

Therefore, $V_{os} = (0.1 \text{ V})(0.02) = 2 \text{ mV}$

$$\text{For } I = 360 \mu\text{A}, I_D = \frac{360 \mu\text{A}}{2} = 180 \mu\text{A}$$

$$g_m = \sqrt{2k_n' \frac{W}{L} I_D} = \sqrt{2(4 \text{ mA/V}^2)(0.18 \text{ mA})}$$

$$= 1.2 \text{ mA/V}$$

$A_d = g_m R_D = (1.2 \text{ mA/V})(10 \text{ k}) = 12 \text{ V/V}$

$$\frac{V_{ov}}{2} = \frac{I_D}{g_m} = \frac{180 \mu\text{A}}{1.2 \text{ mA/V}} = 0.15 \text{ V}$$

so that

$$V_{os} = \left(\frac{V_{ov}}{2} \right) \left(\frac{\Delta R_D}{R_D} \right) = (0.15 \text{ V})(0.02) = 3 \text{ mV}$$

So both A_d and V_{os} increase at the same ratio since both are proportional to $\sqrt{I_D}$

8.72

Worst-case $\Delta V_{\pi} = 10 \text{ mV}$

$$\text{Worst-case } \frac{\Delta R_D}{R_D} = 0.04$$

$$\text{Worst-case } \frac{\Delta(W/L)}{(W/L)} = 0.04$$

From Eq. (8.108),

$$V_{OS1}(d_{ve} \text{ to } \Delta R_D) = \frac{V_{OV}}{2} \cdot \frac{\Delta R_D}{R_D} = \frac{0.2 \text{ V}}{2} \cdot (0.04)$$

$$= 4 \text{ mV}$$

From Eq. (8.113),

$$V_{OS2}(d_{ve} \text{ to } \Delta \left(\frac{W}{L} \right)) = \frac{V_{OV}}{2} \cdot \frac{\Delta(W/L)}{(W/L)}$$

$$= \frac{0.2 \text{ V}}{2} \cdot (0.04) = 4 \text{ mV}$$

From Eq. (8.116),

$$V_{OS3}(d_{ve} \text{ to } \Delta V_t) = \Delta V_t = 10 \text{ mV}$$

The absolute worst-case total offset would be

$4 + 4 + 10 = 18 \text{ mV}$ However, since these offset sources are not correlated, a realistic observation might be [from Eq. (8.117)]

$$V_{OS} = \sqrt{V_{OS1}^2 + V_{OS2}^2 + V_{OS3}^2}$$

$$= \sqrt{(4)^2 + (4)^2 + (10)^2} = 11.5 \text{ mV}$$

The major contribution is from the variation in V_{π} .

If we attempt to compensate for V_{OS} by changing R_D ,

$$\text{We have, } 11.5 \text{ mV} = \frac{V_{OV}}{2} \cdot \frac{\Delta R_D}{R_D} \text{ or}$$

$$\frac{\Delta R_D}{R_D} = \frac{11.5 \text{ mV}}{0.2 \text{ V}/2} = 0.115 \text{ or } 11\%$$

If V_{OS3} is reduced by a factor of 10,

$$V_{OS} = \sqrt{(4)^2 + (4)^2 + (1)^2} = 5.74 \text{ mV}$$

So that

$$\frac{\Delta R_D}{R_D} = \frac{5.74 \text{ mV}}{0.2 \text{ V}/2} = 5.74\%$$

8.73

$$I_D = \frac{I}{2} = \frac{100 \mu\text{A}}{2} = 50 \mu\text{A}$$

$$I_D = \frac{1}{2} K_n' \left(\frac{W}{L} \right) V_{OV}^2 \text{ or}$$

$$V_{OV} = \sqrt{\frac{2 I_D}{K_n' (W/L)}} = \sqrt{\frac{2(50 \mu\text{A})}{250 \mu\text{A/V}^2(10)}}$$

$$= 0.2 \text{ V}$$

From Eq. (8.108)

$$V_{OS1}(\text{due to } \Delta R_D) = \frac{V_{OV}}{2} \cdot \frac{\Delta R_D}{R_D} = \frac{0.2 \text{ V}}{2} \cdot (0.05)$$

$$= 5 \text{ mV}$$

From Eq. (8.113),

$$V_{OS2}(\text{due to } \Delta \frac{W/L}{W/L}) = \frac{V_{OV}}{2} \cdot \frac{\Delta(W/L)}{(W/L)}$$

$$= \frac{0.2 \text{ V}}{2} \cdot (0.05) = 5 \text{ mV}$$

From Eq. (8.116),

$$V_{OS3}(\text{due to } \Delta V_T) = \Delta V_T = 5 \text{ mV}$$

The worst-case offset is

$$V_{OS} = V_{OS1} + V_{OS2} + V_{OS3} = 5 + 5 + 5 \\ = 15 \text{ mV}$$

The root-sum-square value from Eq. (8.117) is

$$V_{OS} = \sqrt{V_{OS1}^2 + V_{OS2}^2 + V_{OS3}^2} \\ = \sqrt{(5)^2 + (5)^2 + (5)^2} = 8.66 \text{ mV}$$

8.74

The output offset voltage is $\Delta V_C = \Delta R_C \cdot \frac{I}{2}$

$$A_d = g_m R_C = \frac{I/2}{V_T} \cdot R_C = \frac{I R_C}{2 V_T}$$

$$|V_{OS}| = \frac{|\Delta V_C|}{A_d} = \frac{\Delta R_C I}{\frac{I R_C}{2 V_T}} \\ = V_T \cdot \left(\frac{\Delta R_C}{R_C} \right) = 25 \text{ mV} (0.08)$$

$$|V_{OS}| = 2 \text{ mV}$$

8.75

From Eq. (8.126),

$$|V_{OS}| = V_T \left(\frac{\Delta I_S}{I_S} \right)$$

$$|V_{OS}| = 25 \text{ mV} (0.10) = 2.5 \text{ mV}$$

8.76

$$\Delta v_{EE} = \Delta R_C \frac{I}{2}$$

$$A_d = \frac{R_C}{r_e + R_e} = \frac{R_C}{\frac{2 V_T}{I} + R_E} = \frac{I R_C}{2 V_T + I R_E}$$

$$V_{OS} = \frac{\Delta v_C}{A_d} = \frac{\Delta R_C}{R_C} \left(V_T + \frac{I R_E}{2} \right)$$

8.77

$$\Delta v_C = \alpha_1 \frac{I}{2} R_C - \alpha_2 \frac{I}{2} R_C$$

$$= \frac{I}{2} R_C (\alpha_1 - \alpha_2)$$

$$= \frac{I}{2} R_C \left(\frac{\beta_1}{\beta_1 + 1} - \frac{\beta_2}{\beta_2 + 1} \right)$$

For $\beta_1, \beta_2 \gg 1$

$$\Delta v_C = \frac{I}{2} R_C \cdot \frac{\beta_1 - \beta_2}{\beta_1 \cdot \beta_2}$$

$$= \frac{I}{2} R_C \left(\frac{1}{\beta_2} - \frac{1}{\beta_1} \right)$$

$$A_d = \frac{R_C}{r_e} = \frac{I R_C}{2 V_T}$$

$$V_{OS} = \frac{\Delta v_C}{A_d} = V_T \left(\frac{1}{\beta_2} - \frac{1}{\beta_1} \right) \text{ Q.E.D.}$$

For $\beta_1 = 100$ and $\beta_2 = 200$

$$V_{OS} = 25 \left(\frac{1}{200} - \frac{1}{100} \right)$$

$$= -125 \mu\text{V}$$

8.78

CASE 1: BJT Diff. Amp.

From Eq. (8.121)

$$|V_{OS}| = V_T \left(\frac{\Delta R_C}{R_C} \right) = 25 \text{ mV} (0.04) = 1 \text{ mV}$$

CASE 2: MOSFET Diff. Amp.

From Eq. (8.108),

$$V_{OS} = \left(\frac{V_{OV}}{2} \right) \left(\frac{\Delta R_D}{R_D} \right) = \frac{300 \text{ mV}}{2} (0.04) = 6 \text{ mV}$$

If the MOSFET widths, are increased by a factor of 4, and since I_D must remain constant, we see that since

$$I_D = \frac{1}{2} K_n' \left(\frac{W}{L} \right) V_{OV}^2,$$

$$\text{The new } V_{OV} = \sqrt{\frac{2 I_D}{(4) K_n' \left(\frac{W}{L} \right)}} \text{ which is } \sqrt{\frac{1}{4}} \text{ or } \frac{1}{2}$$

of its original value.

So, the new offset voltage is


$$V_{OS} = \left(\frac{150 \text{ mV}}{2} \right) (0.04) = 3 \text{ mV}$$

8.79

Since the two transistors are matched except for their V_A value, we can express the collector currents when the input terminals are grounded as,

$$I_{C1} = I_C \left(1 + \frac{V_{CE}}{V_{A1}} \right)$$

8.89

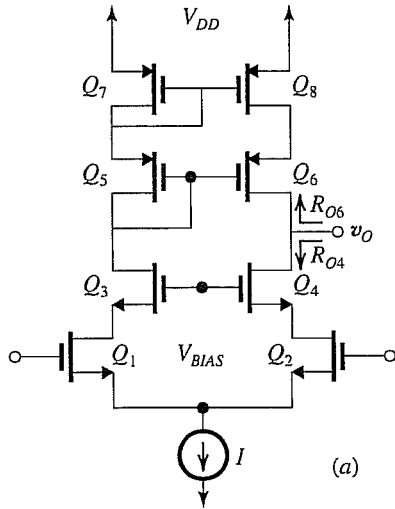

$$\begin{aligned} (b) R_{O4} &= (g_{m4} r_{O4}) r_{O2} \\ &= g_m r_o^2 \\ R_{O6} &= (g_{m6} r_{O6}) r_{O8} \\ &= g_m r_o^2 \\ A_d &= g_m (R_{O4} \parallel R_{O6}) \\ &= g_m \cdot \frac{1}{2} g_m^2 r_o^2 \end{aligned}$$

$$g_m = \frac{2I_D}{V_{OV}} \quad r_o = \frac{V_A}{I_D}$$

$$\begin{aligned} \text{thus, } g_m r_o &= 2V_A / V_{OV} \\ \Rightarrow A_d &= 2(V_A / V_{OV})^2 \end{aligned}$$

Q.E.D.

$$\begin{aligned} \text{For } V_{OV} &= 0.25 \text{ V} \text{ \& } V_A = 20 \text{ V} \\ A_d &= 2(20 / 0.25)^2 = 12800 \text{ V/V} \end{aligned}$$

8.90

Referring to Fig P8.90,

$$\begin{aligned} i_1 &= \frac{V_O}{r_o} = \frac{\frac{1}{2}(g_m r_o) v_{id}}{r_o} = \frac{1}{2} g_m v_{id} \\ i_2 &= g_{m4} v_{gs4} = \frac{g_m v_{id}}{4} \\ i_3 &= i_1 - i_2 = \frac{g_m v_{id}}{2} - g_m \frac{v_{id}}{4} = \frac{g_m v_{id}}{4} \\ i_4 &= -g_{m2} v_{gs2} = -g_m \left[-\frac{v_{id}}{2} - \frac{v_{id}}{4} \right] \\ &= \frac{3}{4} g_m v_{id} \\ i_5 &= i_4 = \frac{3}{4} g_m v_{id} \\ i_6 &= i_4 - i_3 = \frac{3}{4} g_m v_{id} - \frac{1}{4} g_m v_{id} = \frac{1}{2} g_m v_{id} \end{aligned}$$

However, if we use KVL,

$$\begin{aligned} i_6 &= \frac{v_o - v_s}{r_o} = \frac{\frac{1}{2} g_m r_o v_{id} - \frac{V_{id}}{4}}{r_o} \\ &= \frac{1}{2} g_m V_{id} - \frac{V_{id}}{4r_o} \text{ inconsistent} \end{aligned}$$

$$\begin{aligned} i_7 &= i_5 - i_6 = \frac{3}{4} g_m V_{id} - \frac{g_m V_{id}}{2} = \frac{g_m V_{id}}{4} \\ \text{(which is the same as } i_3) \end{aligned}$$

$$i_8 = g_m v_{gs1} = g_m \left(\frac{V_{id}}{2} - \frac{V_{id}}{4} \right) = \frac{1}{4} g_m v_{id}$$

$$i_9 = i_8 = \frac{1}{4} g_m V_{id}$$

$$i_{10} = i_8 - i_7 = \frac{g_m V_{id}}{4} - \frac{g_m V_{id}}{4} = 0$$

$$i_{11} + i_{10} = i_9 \text{ or}$$

$$i_{11} = i_9 - i_{10} = i_9 = \frac{g_m V_{id}}{4}$$

(which is the same as i_7)

$$i_{12} = g_m v_{gs3} = \frac{1}{4} g_m V_{id}$$

$$i_{13} = i_{11} - i_{12} = \frac{1}{4} g_m V_{id} - \frac{1}{4} g_m V_{id} = 0$$

Note, through, that this is inconsistent with KVL. If $i_{13} = 0$, $V_{D3} = 0$, but $V_{D3} = V_{G3} = -V_{id}/4$.

If $i_{10} = 0$, $V_{D1} = \frac{V_{id}}{4}$, but this conflicts with V_{D3} being $-\frac{V_{id}}{4}$.

It appears that the approximations for V_{gs} and v_s prevent a clean solution. If these were more exact, all current and voltage relationships should be consistent.

8.91

Assuming a configuration similar to Fig. 8.32(a),

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = \frac{I}{2} = \frac{100 \mu\text{A}}{2} = 50 \mu\text{A}$$

$$g_{m1} = g_{m2} = \frac{I_D}{V_{ov}/2} = \frac{50 \mu\text{A}}{0.2 \text{ V}/2} = 0.5 \text{ mA/V}$$

$$G_m = g_{m1} = 0.5 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \frac{V_{An}}{I_D} = \frac{20 \text{ V}}{0.05 \text{ mA}} = 400 \text{ k}\Omega$$

$$r_{o3} = r_{o4} = \frac{|V_{Ap}|}{I_D} = \frac{12 \text{ V}}{0.05 \text{ mA}} = 240 \text{ k}\Omega$$

From Eq. (8.140),

$$R_o = r_{o2} \parallel r_{o4} = 400 \text{ k} \parallel 240 \text{ k} = 150 \text{ k}\Omega$$

$$A_d = G_m R_o = (0.5 \text{ mA/V})(150 \text{ k}) = 75 \text{ V/V}$$

Gain will be reduced by a factor of 2 if

$$R_L = R_o = 150 \text{ k}\Omega$$

8.110

$$I_{D7} = \frac{W_7}{W_8} I_{REF} = \frac{50}{40} \times 90 \mu\text{A}$$

$$= 112.5 \mu\text{A}$$

$$\text{Output offset current} = I_{D7} - I_{D6}$$

$$= 112.5 - 90 = 22.5 \mu\text{A}$$

$$\Rightarrow V_o = 22.5 \mu (r_{o6} \parallel r_{o7})$$

$$r_{o7} = \frac{10}{112.5 \mu} = 88.9 \text{ k}\Omega$$

$$\Rightarrow V_o = 22.5 \mu (111 \text{ k} \parallel 88.9 \text{ k})$$

$$= 1.11 \text{ V}$$

$$V_{os} = \frac{V_o}{A_o} = \frac{1.11 \text{ V}}{1109} = 1 \text{ mV}$$

8.111

$$\text{Offset current} = I_{D2} - I_{D4}$$

$$= I_{D3} - I_{D4}$$

$$I_{D3} = \frac{K}{2} (V_{GS} - V_t)^2$$

$$I_{D4} = \frac{K}{2} (V_{GS} - (V_t + \Delta V_t))^2$$

$$I_o = I_{D3} - I_{D4}$$

$$= \frac{K}{2} [(V_{GS} - V_t - V_{GS} + V_t + \Delta V_t) \times$$

$$(V_{GS} - V_t + V_{GS} - V_t - \Delta V_t)]$$

$$= \Delta V_t \cdot \frac{K}{2} (2V_{GS} - 2V_t - \Delta V_t)$$

$$\simeq K(V_{GS} - V_t) \cdot \Delta V_t$$

$$I_o = g_{m3} \Delta V_t$$

$$\text{Recall } I_o = G_{m1} \cdot V_{os}$$

$$\text{and } G_{m1} = g_{m1}$$

$$\Rightarrow V_{os} = \frac{g_{m3}}{g_{m1}} \cdot \Delta V_t$$

$$\text{For } \Delta V_t = 2 \text{ mV}$$

$$V_{os} = \frac{0.3 \text{ m}}{0.3 \text{ m}} \times 2 \text{ m} = 2 \text{ mV}$$

8.112

(a) Referring to Fig. P8.112,

$$I_{E1} = I_{E2} = \frac{I}{2} = \frac{0.2 \text{ mA}}{2} = 0.1 \text{ mA}$$

$$I_{E3} \simeq I_{E4} = \frac{I}{2} = 0.1 \text{ mA}$$

$$I_{E5} = 0.5 \text{ mA}$$

since the output voltage is held at 0 V,

$$I_{E6} = 1 \text{ mA}$$

(b) considering the first stage,

$$G_{m1} = g_{m1} = \frac{|I_{C1}|}{V_T} = \frac{0.1 \text{ mA}}{25 \text{ mV}} = 4 \text{ mA/V}$$

since all $r_{os} = \infty$, the load of the differential stage is just the input of Q_5 .

$$r_{e5} = \frac{V_T}{|I_{E5}|} = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega$$

$$R_{o1} = (\beta + 1)r_{e5} = (101)(50) = 5.05 \text{ k}\Omega$$

$$A_1 = G_{m1}R_{o1} = (4 \text{ mA/V})(5.05 \text{ k}) = 20.2 \text{ V/V}$$

For the common-emitter stage (Q_5),

$$g_{m5} = \frac{I_{C5}}{V_T} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 20 \text{ mA/V}$$

The load is essentially

$$(R_L + r_{e6})(\beta + 1) \simeq R_L(\beta + 1)$$

$$A_5 = -g_{m5}(R_L)(\beta + 1)$$

$$= -20 \text{ mA/V} (10 \text{ k})(101) = -20,200 \text{ V/V}$$

$A_6 \simeq 1$ so,

$$A_o = A_1 \cdot A_5 \cdot A_6 = (20.2)(-20,200)(1)$$

$$= -408,040 \text{ V/V}$$

or

$$-A_o(\text{dB}) = 20 \log_{10}(408,040) = 112 \text{ dB}$$

8.113

$$I_B = 225 \mu\text{A}$$

$$\mu_n C_{OX} = 180 \mu\text{A/V}^2$$

$$\mu_p C_{OX} = 60 \mu\text{A/V}^2$$

For Q_8 & Q_9 : $W/L = 60/0.5$

$$\Rightarrow |V_{ov}| = \sqrt{\frac{2I_D}{k_p(W/L)}}$$

$$|V_{ov}|_{8,9} = \sqrt{\frac{2 \times 225 \mu}{60 \mu \times 120}} = 0.25 \text{ V}$$

$$\text{then } g_{m8,9} = \frac{2I_D}{|V_{ov}|} = \frac{2 \times 225 \mu}{0.25 \text{ V}}$$

$$= 1.8 \text{ mA/V}$$

Since g_m of Q_{10} , Q_{11} & Q_{13} are identical to g_m of Q_8 & Q_9 then $V_{ov13} = 0.25 \text{ V}$

Thus for Q_{13}

$$(0.25)^2 = \frac{2 \times 225 \mu}{180 \mu \times (W/L)_{13}}$$

$$\rightarrow (W/L)_{13} = 40 \text{ i.e., } (20/0.5)$$

Since Q_{12} is 4 times as wide as Q_{13} , then

$$(W/L)_{12} = \frac{4 \times 20}{0.5} = 80/0.5$$

$$R_B = \frac{2}{\sqrt{2 k_n (W/L)_{12} I_B}} \cdot \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)$$

$$= \frac{2}{\sqrt{2 \times 180 \mu \times \frac{80}{0.5} \times 225 \mu}} \cdot \left(\frac{\sqrt{\frac{80/0.5}{20/0.5}} - 1}{\sqrt{4} - 1} \right)$$

$$\rightarrow R_B = 555.6 \Omega$$

The voltage drop on R_B is:

$$555.6 \times 225 \mu = 0.125 \text{ V}$$

To obtain the gate voltages: (assume $|V_{m1}| = |V_{p1}| = 0.7 \text{ V}$)