

$$10.80 \quad A(S) = \frac{10^5}{1 + S/100}$$

$$\text{Ang}(A) = -\tan^{-1} \frac{\omega}{100} - 2 \tan^{-1} \frac{\omega}{10^4}$$

at  $\omega_{180}$ :  $\text{Ang}(A) = -180^\circ$  for  $\omega_{180} \gg 100$

$$\Rightarrow 18^\circ = 90^\circ + 2 \tan^{-1} \left[ \frac{\omega_{180}}{10^4} \right]$$

$$\text{hence } \tan^{-1} \frac{\omega_{180}}{10^4} = \frac{90^\circ}{2}$$

$$\text{i.e. } \frac{\omega_{180}}{10^4} = \tan(45^\circ) = 1$$

$$\therefore \omega_{180} = 10^4 \text{ rad/s}$$

$$|A\beta| = \frac{10^5 \beta}{\sqrt{1 + (10^4/10^2)^2}} \cdot \frac{1}{(\sqrt{1 + 1})^2} = 1$$

$$\Rightarrow \beta = 0.002$$

$$A_f(0) = \frac{10^5}{1 + 10^5(0.002)} \approx 500 \text{ V/V}$$

$$10.83 \quad A(S) = \frac{1000}{(1 + S/10^4)(1 + S/10^5)^2}$$

and  $\beta$  is independent of frequency

$$\text{Ang}(A) = -\tan^{-1} \frac{\omega}{10^4} - 2 \tan^{-1} \frac{\omega}{10^5}$$

$$\text{try } \omega = 10^4: \theta = 5 \cdot 45^\circ + 2 \times 5.7 = 56.4^\circ$$

$$\text{try } \omega = 10^5: \theta = 5 \cdot 84.2^\circ + 2 \times 45 = 174.2^\circ$$

Iteration yields  $\omega \approx 1.1 \times 10^5 \text{ rad/s}$

For oscillations:  $|AB(\omega_{180})| \geq 1$

$$\frac{\beta \cdot 10^3}{(\sqrt{1 + 11^2})(\sqrt{1 + 1.1^2})} \geq 1$$

$$\Rightarrow \beta \geq 0.0244$$

$$10.88 \quad A(f) = \frac{-K}{1 + j_f/10^5}$$

$$\text{for } \beta = 1: A\beta = \frac{K^3}{\left(1 + \frac{j_f}{10^5}\right)^3}$$

For oscillations to occur:  $|A\beta| \geq 1$  at

$$\phi(A\beta) = 180^\circ$$

$$3 \tan^{-1}$$

$$\left(\frac{f_{180^\circ}}{10^5}\right) = 180^\circ \Rightarrow f_{180^\circ} = \sqrt{3} \times 10^5 \text{ Hz}$$

$$f_{180^\circ} = 173.2 \text{ KHz}$$

Amplifier is unstable if  $|A\beta| \geq 1$  at  $f_{180^\circ}$

$$\left[\frac{K}{\sqrt{1 + (\sqrt{3})^2}}\right]^3 \geq 1 \rightarrow K \geq 2$$

10.92

$$A(j_f) = \frac{10^5}{\left(1 + \frac{j_f}{10^5}\right) \left(1 + \frac{j_f}{3.16 \times 10^5}\right) \left(1 + \frac{j_f}{10^6}\right)}$$

Assume  $\beta$  independent of frequency

For  $45^\circ$  PM:  $\theta = 180 - 45$

$$\tan^{-1} \frac{f_1}{10^5} + \tan^{-1} \frac{f_1}{3.16 \times 10^5} + \tan^{-1} \frac{f_1}{10^6} = 135^\circ$$


$$\text{solve } \Rightarrow f_1 = 3.16 \times 10^5 \text{ Hz}$$

$$|A\beta(f_1)| = 1 = \frac{10^5 \beta}{\sqrt{1 + (3.16)^2} \cdot \sqrt{2} \cdot \sqrt{1 + (0.316)^2}}$$

$$\Rightarrow \beta = 49 \times 10^{-6}$$

$$Af(0) = \frac{10^5}{1 + 10^5(4.9 \times 10^{-6})} = 16.9 \times 10^3$$

10.95

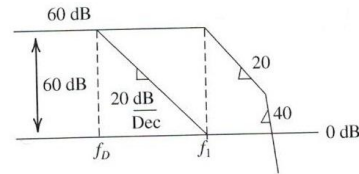


$$f_1 = 3 \text{ MHz}$$

$$A_o = 60 \text{ dB} \approx 1000$$

$$\frac{60 \text{ dB}}{20 \text{ dB/Dec}} = 3 \text{ Dec}$$

$$f_D = \frac{f_1}{10^3} = \frac{3 \text{ MHz}}{10^3} = 3 \text{ KHz}$$

10.96

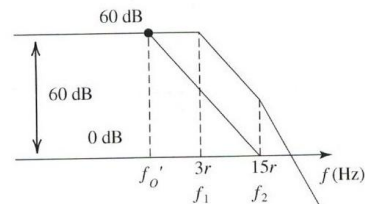

$$f_{p1} = 3 \text{ MHz}, f_{p2} = 15 \text{ MHz}$$

$$A_o = 60 \text{ dB}$$

$$\frac{60 \text{ dB}}{20 \text{ dB/Dec}} = 3 \text{ Dec}$$


$$f'_D = \frac{15 \mu}{10^3} = 15 \text{ KHz}$$

$$\text{if: } f_1 = \frac{1}{2\pi RC} \text{ and } f'_D = \frac{1}{2\pi RC_C}$$

$$\Rightarrow \frac{f_1}{f'_D} = \frac{3 \times 10^6}{15 \times 10^3} = \frac{C_C}{C} \Rightarrow 200 \times C = C_C$$

$C_C$  is increased by a factor of 200 to shift the dominant pole from 3 MHz to 15 KHz

10.98

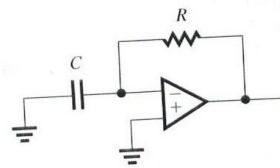

$$A_o = 10^4$$

Poles at  $10^6, 10^7, 10^8 \text{ Hz}$

For  $\beta = 1$ ,  $f_p$  must be kept  $10^4$  times

lower than the lowest pole at  $10^6 \text{ Hz}$

$$f_p = \frac{10^6}{10^4} = 100 \text{ Hz}$$

$$\text{Since: } f_p = \frac{1}{2\pi RC} \text{ and } R = 1 \text{ M}\Omega$$

$$\Rightarrow C = \frac{1}{2\pi \times 1 \text{ M} \times 100} = 1.59 \text{ nF}$$